

## **UNIT-IV**

# **Fundamentals of semiconductor devices and digital circuits**

Lecture 26

Prepared By:

Krishan Arora

Assistant Professor and Head

# Boolean Algebra

- Sometimes it is more economical to build a circuit using the complement of a function (and complementing its result) than it is to implement the function directly.
- DeMorgan's law provides an easy way of finding the complement of a Boolean function.
- Recall DeMorgan's law states:

$$\overline{(xy)} = \bar{x} + \bar{y} \quad \text{and} \quad \overline{(x+y)} = \bar{x}\bar{y}$$

# Boolean Algebra

- DeMorgan's law can be extended to any number of variables.
- Replace each variable by its complement and change all ANDs to ORs and all ORs to ANDs.
- Thus, we find the the complement of:

is:

$$F(X, Y, Z) = (XY) + (\bar{X}Z) + (Y\bar{Z})$$

$$\bar{F}(X, Y, Z) = \overline{(XY) + (\bar{X}Z) + (Y\bar{Z})}$$

$$= \overline{(XY)} \overline{(\bar{X}Z)} \overline{(Y\bar{Z})}$$

$$= (\bar{X} + \bar{Y})(X + \bar{Z})(\bar{Y} + Z)$$

# Boolean Algebra

- Through our exercises in simplifying Boolean expressions, we see that there are numerous ways of stating the same Boolean expression.
  - These “synonymous” forms are *logically equivalent*.
  - Logically equivalent expressions have identical truth tables.
- In order to eliminate as much confusion as possible, designers express Boolean functions in *standardized* or *canonical* form.

# Boolean Algebra

- There are two canonical forms for Boolean expressions: sum-of-products and product-of-sums.
  - Recall the Boolean product is the AND operation and the Boolean sum is the OR operation.
- In the sum-of-products form, ANDed variables are ORed together.
  - For example:  $F(x, y, z) = xy + xz + yz$
- In the product-of-sums form, ORed variables are ANDed together:
  - For example:  $F(x, y, z) = (x+y)(x+z)(y+z)$

# Boolean Algebra

- It is easy to convert a function to sum-of-products form using its truth table.
- We are interested in the values of the variables that make the function true (=1).
- Using the truth table, we list the values of the variables that result in a true function value.
- Each group of variables is then ORed together.

$$F(x, y, z) = x\bar{z} + y$$

x	y	z	$x\bar{z} + y$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

# Boolean Algebra

- The sum-of-products form for our function is:

$$F(x, y, z) = \bar{x}\bar{y}\bar{z} + \bar{x}y\bar{z} + x\bar{y}\bar{z} + x\bar{y}z$$

**We note that this function is not in simplest terms. Our aim is only to rewrite our function in canonical sum-of-products form.**

$$F(x, y, z) = x\bar{z} + y$$

x	y	z	$x\bar{z} + y$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1


# Logic Gates

- We have looked at Boolean functions in abstract terms.
- In this section, we see that Boolean functions are implemented in digital computer circuits called gates.
- A gate is an electronic device that produces a result based on two or more input values.
  - In reality, gates consist of one to six transistors, but digital designers think of them as a single unit.
  - Integrated circuits contain collections of gates suited to a particular purpose.


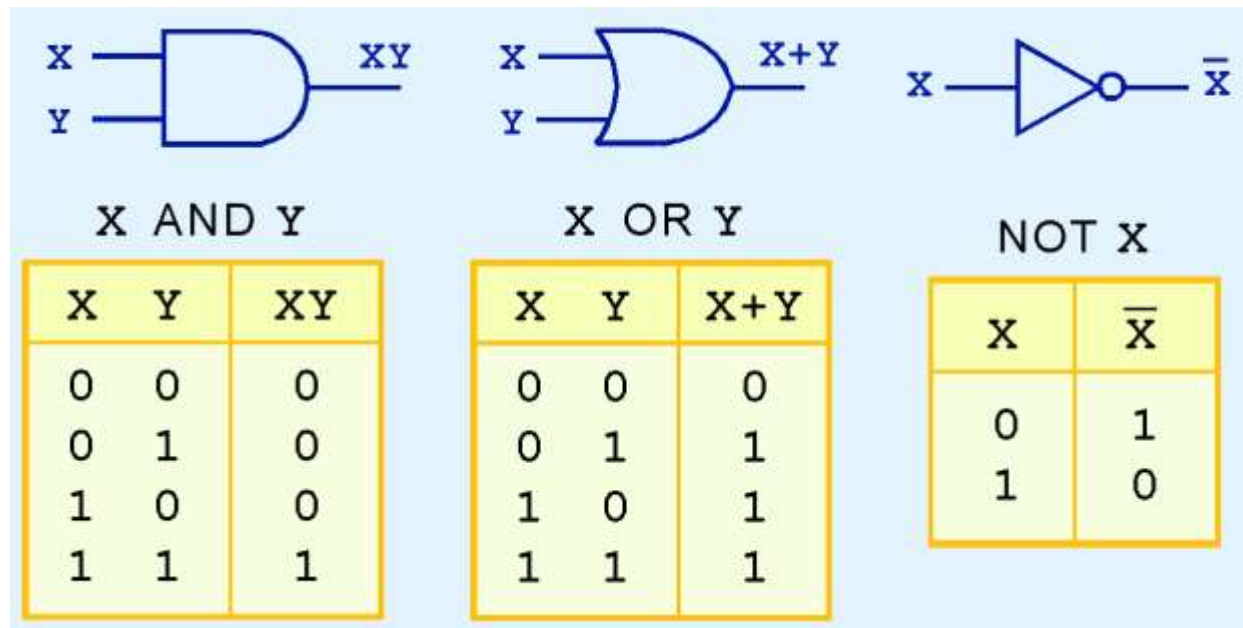
# Logic Gates

- The three simplest gates are the AND, OR, and NOT gates.




- They correspond directly to their respective Boolean operations, as you can see by their truth tables.

# Logic Gates

- Another very useful gate is the exclusive OR (XOR) gate.
- The output of the XOR operation is true only when the values of the inputs differ.

**X XOR Y**


X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

A logic diagram of an XOR gate. It has two inputs labeled 'X' and 'Y' on the left. The gate symbol is a D-shaped symbol with a curved front and a pointed back. The output is a single line on the right labeled 'X ⊕ Y'.

**Note the special symbol  $\oplus$  for the XOR operation.**

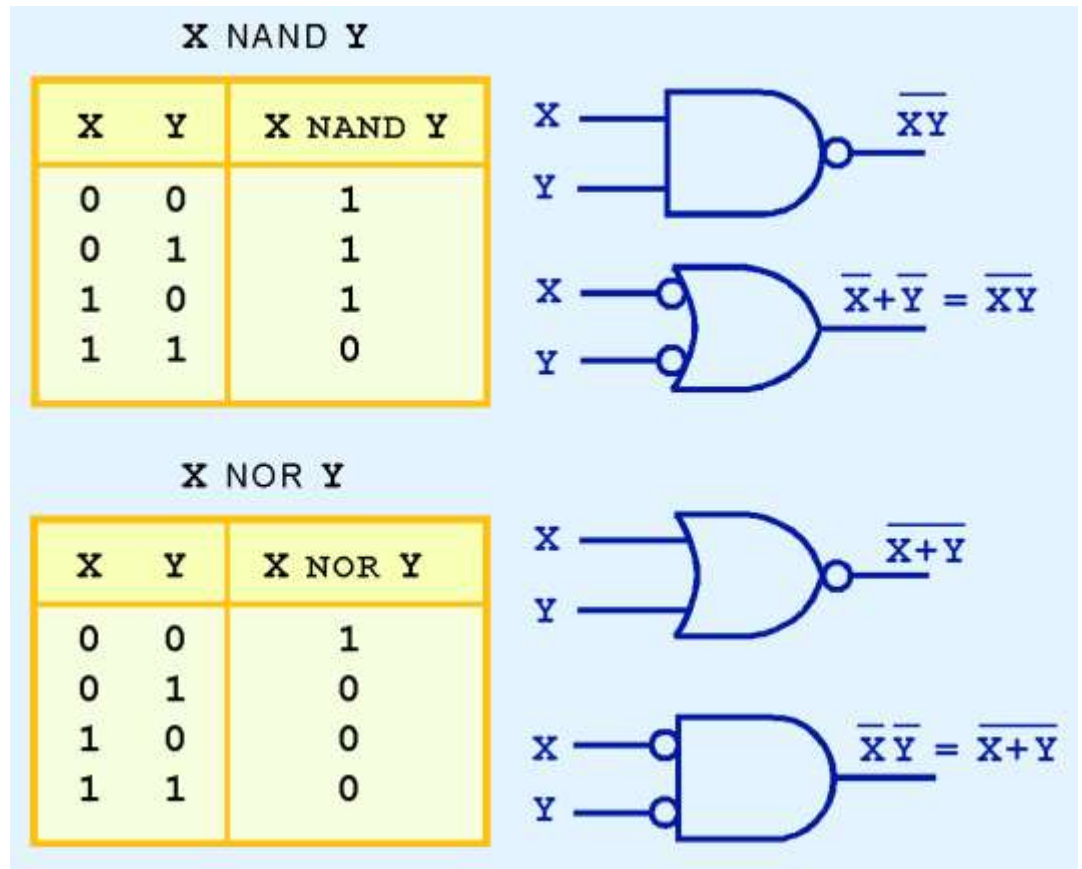
# Logic Gates

- NAND and NOR are two very important gates. Their symbols and truth tables are shown at the right.



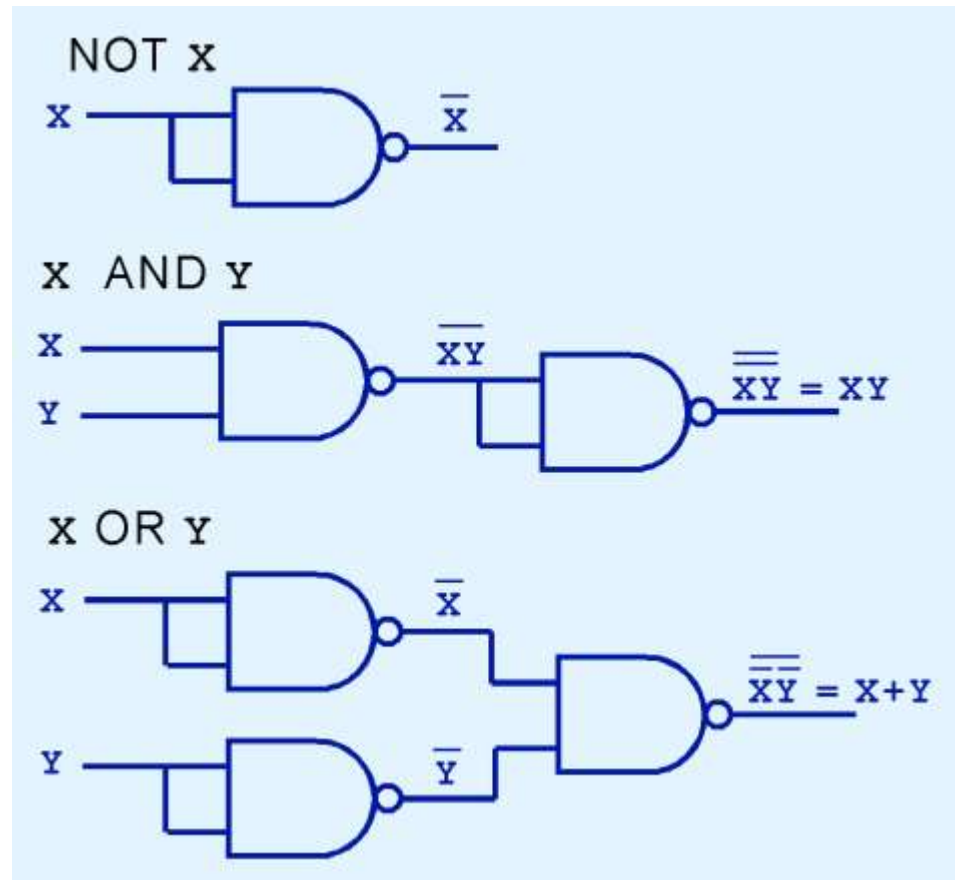
# Logic Gates

- NAND and NOR are known as *universal gates* because they are inexpensive to manufacture and any Boolean function can be constructed using only NAND or only NOR gates.


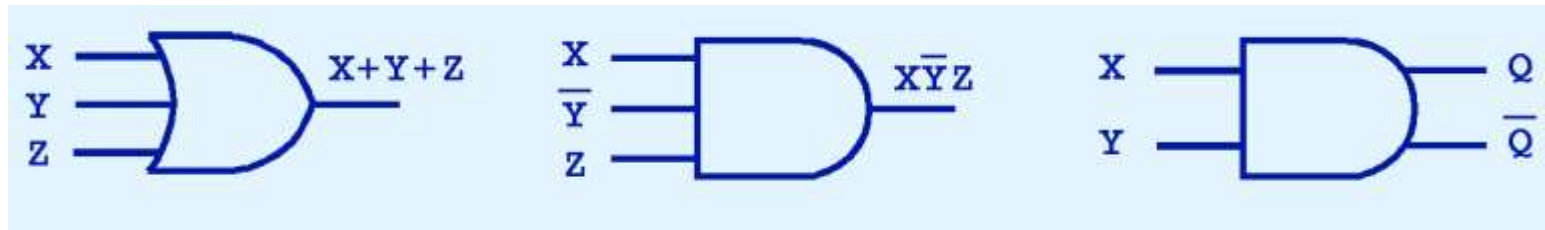
# Logic Gates

- Gates can have multiple inputs and more than one output.
  - A second output can be provided for the complement of the operation.
  - We'll see more of this later.



# Quick Quiz (Poll 1)


- Electronic circuits that operate on one or more input signals to produce standard output \_\_\_\_\_
  - a) Series circuits
  - b) Parallel Circuits
  - c) Logic Signals
  - d) Logic Gates

# Quick Quiz (Poll 2)

- A \_\_\_\_\_ gate gives the output as 1 only if all the inputs signals are 1.
  - a) AND
  - b) OR
  - c) EXOR
  - d) NOR
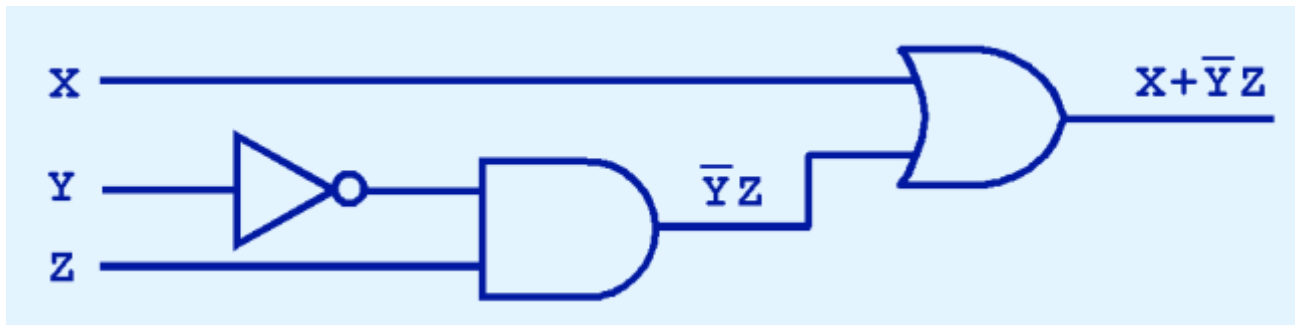
# Digital Components

- The main thing to remember is that combinations of gates implement Boolean functions.
- The circuit below implements the Boolean function:  $F(X, Y, Z) = X + \bar{Y}Z$




**We simplify our Boolean expressions so that we can create simpler circuits.**


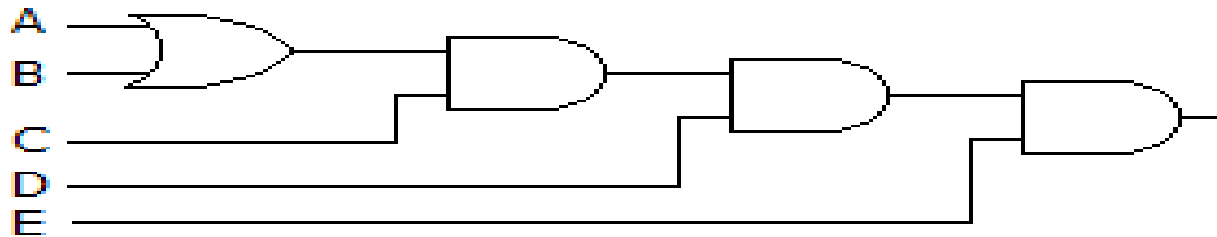
# Quick Quiz (Poll 3)

Derive the Boolean expression for the logic circuit shown below:



- A.  $C(A + B)DE$
- B.  $[C(A + B)D + \bar{E}]$
- C.  $[[C(A + B)D]\bar{E}]$
- D.  $ABCDE$

# Quick Quiz (Poll 4)

- The universal gate that can be used to implement any Boolean expression is

\_\_\_\_\_

- a) NAND
- b) EXOR
- c) OR
- d) AND