



DIGITAL ELECTRONICS

SUBTRACTOR



❖ Objectives

- Definition of Subtractor
- Types of subtractor
- Explaining different subtractors with
 - Truth table
 - Boolean Expression
 - Logic circuit
- Parallel binary subtractor
- Applications




❖ What is Subtractor ?

Subtractor is an electronic logic circuit for calculating the difference between two binary numbers which provides the **difference** and **borrow** as output.



❖ Types of Subtractor

- Half Subtractor
- Full Subtractor

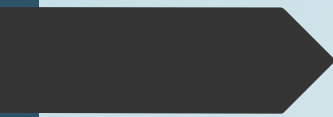

➤ Half subtractor

Half Subtractor is used for subtracting one single bit binary number from another single bit binary number.

It has two inputs; Minuend (A) and Subtrahend (B) and two outputs; Difference (D) and Borrow (B_{out}).

Truth Table

Input		Output	
A	B	Difference (D)	Borrow (B_{out})
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

□ Solving truth table using K-map

B \ A	0	1
	0	1
0	0	0
1	1	0

For Borrow
 $\text{Borrow} = \bar{A}.B$

B \ A	0	1
	0	1
0	0	1
1	1	0

For Difference
 $\text{Difference} = A \oplus B$




□ Boolean Expression

From the truth table and K-map, the Boolean Expression can be derived as:

$$\text{Difference (D)} = \bar{A}.B + A.\bar{B} = A \oplus B$$

$$\text{Borrow (B}_{\text{out}}) = \bar{A}.B$$

□ Logical Circuit

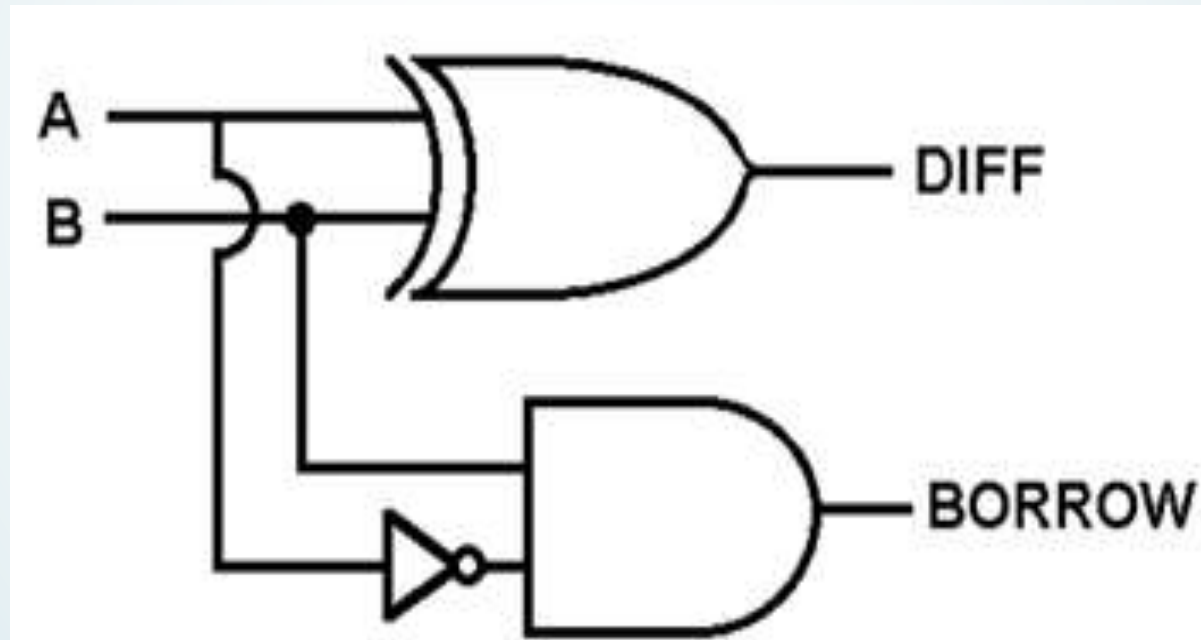



➤ *full subtractor*

A logic Circuit Which is used for subtracting three single bit binary numbers is known as Full Subtractor.

It has three inputs; Minuend (A), Subtrahend (B) and following Subtrahend (C) and two outputs; Difference (D) and Borrow (B_{out}).

Truth Table

Input			Output	
A	B	C	D	B _(out)
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

□ Solving Truth Table using K-Map

BC		00	01	11	10
A	0	0	1	1	1
	1	0	0	1	0

For Borrow

BC		00	01	11	10
A	0	0	1	0	1
	1	1	0	1	0

For Difference

□ K-Map Minimization

From the Truth Table The Difference and Borrow will be written as,

$$\text{Difference} = A'B'C + A'BC' + AB'C' + ABC$$

Reducing it we get,

$$\text{Difference} = A \oplus B \oplus C$$

$$\text{Borrow} = A'B'C + A'BC' + A'BC + ABC$$

$$= A'B'C + A'BC' + A'BC + A'BC + A'BC + ABC$$

$$= A'C(B' + B) + A'B(C' + C) + BC(A' + A)$$

$$\text{Borrow} = A'C + A'B + BC$$




□ Boolean Expression

From the truth table and k-map minimization, the Boolean Expression can be derived as:


$$\mathbf{D} = \mathbf{A} \oplus \mathbf{B} \oplus \mathbf{C}$$

$$\mathbf{B_{(out)}} = \mathbf{BC} + (\mathbf{B} \oplus \mathbf{C}) \mathbf{A}$$

□ Logical Circuit

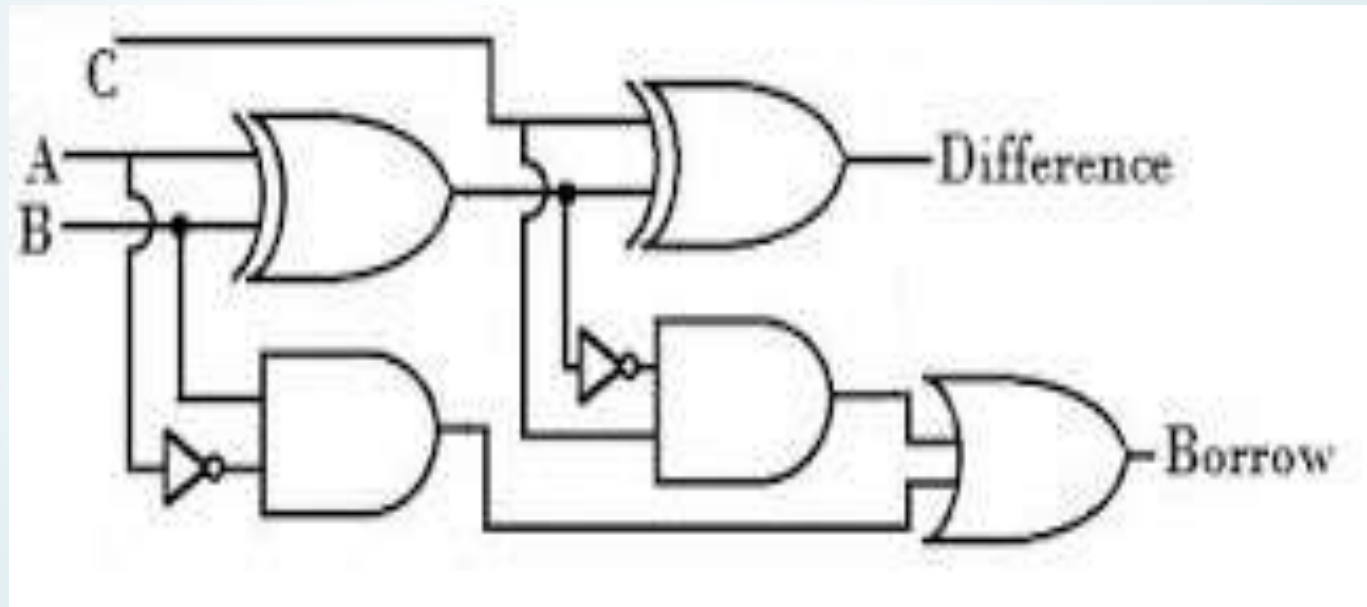

Diagram

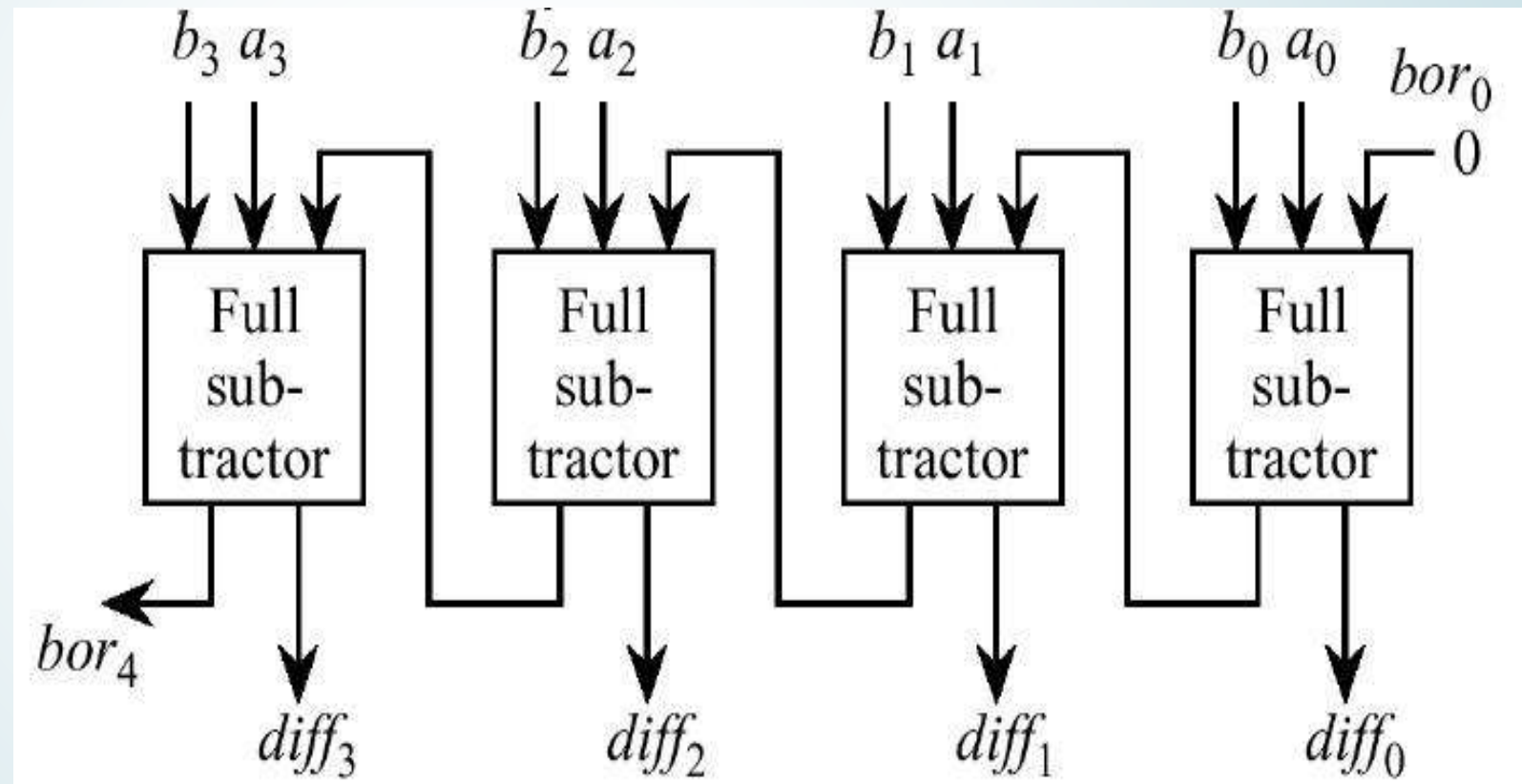



❖ Applications

- To attenuate the radio/audio signal
- In amplifier to reduce sound distortion
- In arithmetic logic unit of processors
- Increment and decrement operators
- Calculate addresses



Any question ?