

ECE213

computer science

illuminated

Logic Gates_{2x}

Dr. Krishan Arora

**Assistant Professor and Head
Lovely Professional University**



Logic Gates

- Logic gates are the fundamental building blocks of digital systems. The name logic gate is derived from the ability of such a device to make a decision, in the sense that it produces one output level when some combinations of input level are present, and a different output level when other combinations of input levels are present.



Computers

- There are three different, but equally powerful, notational methods for describing the behavior of gates and circuits
 - Boolean expressions
 - logic diagrams
 - truth tables



Truth Table

- **Logic diagram:** a graphical representation of a circuit
 - Each type of gate is represented by a specific graphical symbol
- **Truth table:** defines the function of a gate by listing all possible input combinations that the gate could encounter, and the corresponding output



Gates


- Let's examine the processing of the following six types of gates

- NOT
- AND
- OR
- XOR
- NAND
- NOR

Truth table.

- Systematic method to describe Boolean function.
- One row for each possible input combination.
- N inputs $\Rightarrow 2^N$ rows.

AND Truth Table		
x	y	AND
0	0	0
0	1	0
1	0	0
1	1	1

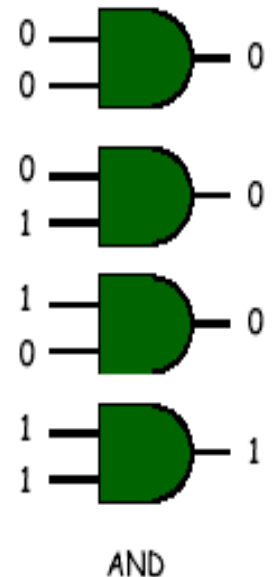



NOT Gate

- A NOT gate accepts one input value and produces one output value


Boolean Expression	Logic Diagram Symbol	Truth Table						
$X = A'$		<table><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	X	0	1	1	0
A	X							
0	1							
1	0							

Figure 4.1 Various representations of a NOT gate



NOT Gate

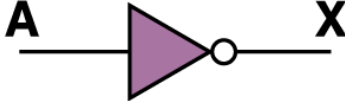- By definition, if the input value for a NOT gate is 0, the output value is 1, and if the input value is 1, the output is 0
- A NOT gate is sometimes referred to as an *inverter* because it inverts the input value



AND Gate

- An AND gate accepts two input signals
- If the two input values for an AND gate are both 1, the output is 1; otherwise, the output is 0

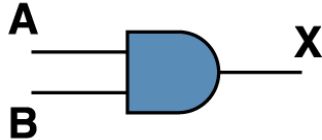
Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = A \cdot B$		<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1
A	B	X															
0	0	0															
0	1	0															
1	0	0															
1	1	1															

Figure 4.2 Various representations of an AND gate



OR Gate

- If the two input values are both 0, the output value is 0; otherwise, the output is 1


Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = A + B$		<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1
A	B	X															
0	0	0															
0	1	1															
1	0	1															
1	1	1															

Figure 4.3 Various representations of a OR gate



XOR Gate

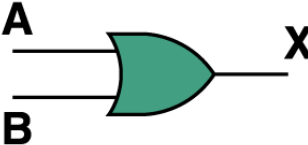- XOR, or *exclusive* OR, gate
 - An XOR gate produces 0 if its two inputs are the same, and a 1 otherwise
 - Note the difference between the XOR gate and the OR gate; they differ only in one input situation
 - When both input signals are 1, the OR gate produces a 1 and the XOR produces a 0




XOR Gate

Boolean Expression

$$X = A \oplus B$$

Logic Diagram Symbol

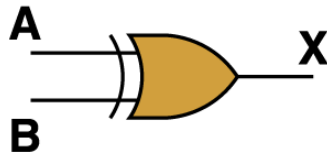

Truth Table

A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

Figure 4.4 Various representations of an XOR gate



NAND and NOR Gates

- The NAND and NOR gates are essentially the opposite of the AND and OR gates, respectively


Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = (A \cdot B)'$		<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0
A	B	X															
0	0	1															
0	1	1															
1	0	1															
1	1	0															

Figure 4.5 Various representations of a NAND gate



Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = (A + B)'$		<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0
A	B	X															
0	0	1															
0	1	0															
1	0	0															
1	1	0															

Figure 4.6 Various representations of a NOR gate

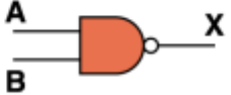

3-Input And gate

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

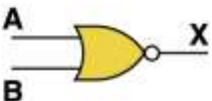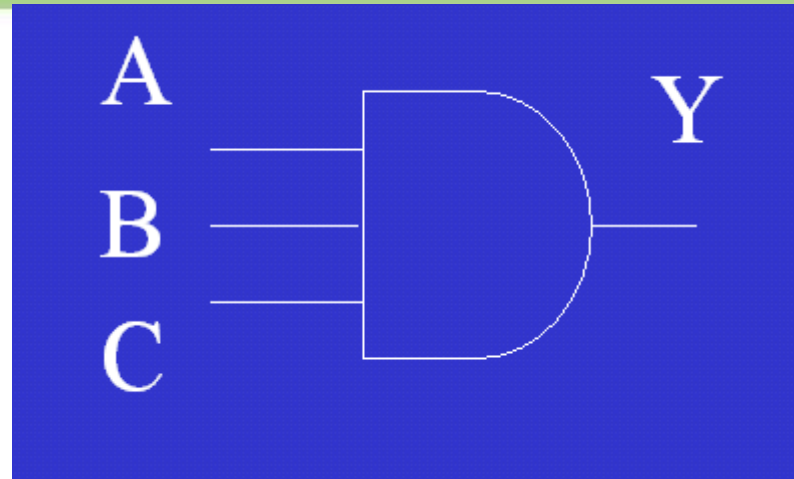

$$Y = A \cdot B \cdot C$$




Circuits

- Two general categories
 - In a **combinational circuit**, the input values explicitly determine the output
 - In a **sequential circuit**, the output is a function of the input values as well as the existing state of the circuit
- As with gates, we can describe the operations of entire circuits using three notations
 - Boolean expressions
 - logic diagrams
 - truth tables



Universal Gates

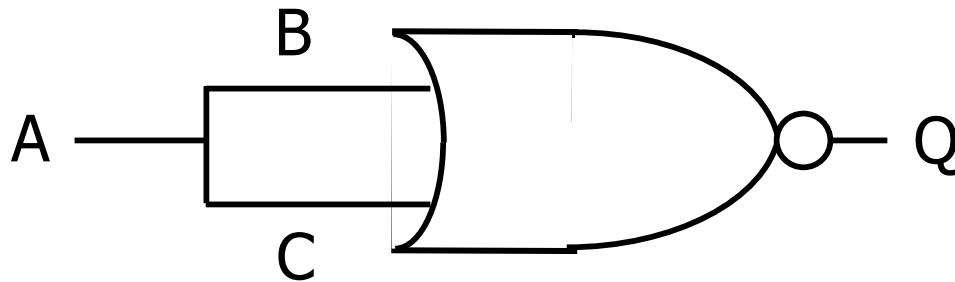How to use **NOR** gate to build a **NOT** gate?



Truth Table

A	B	C	Q
0	0	0	1
1	1	1	0

Hint!

Link inputs B & C together (to a same source).

When $A = 0$, $B = C = A = 0$


When $A = 1$, $B = C = A = 1$





Universal Gates

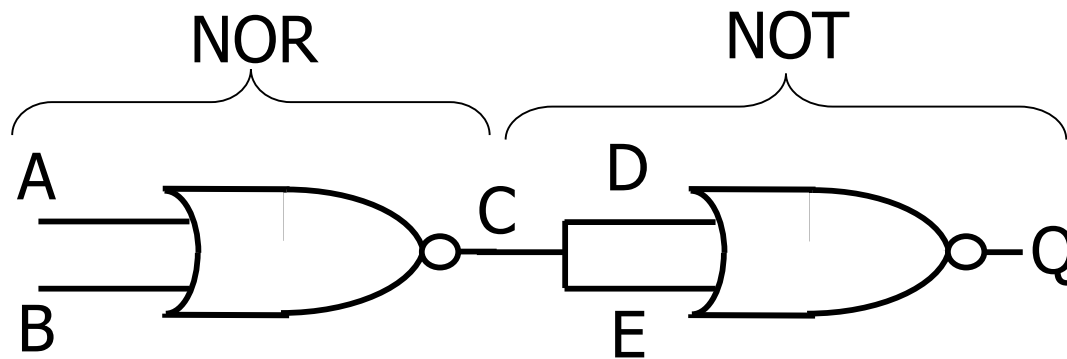*How to use **NOR** gates to build an OR gate?*



Truth Table

A	B	C	D	E	Q
0	0	1	1	1	0
0	1	0	0	0	1
1	0	0	0	0	1
1	1	0	0	0	1

Hint 1 : Use 2 NOR gates


Hint 2 : From a NOR gate, build a NOT gate

Hint 3 : Put this "NOT" gate after a NOR gate



Universal Gates

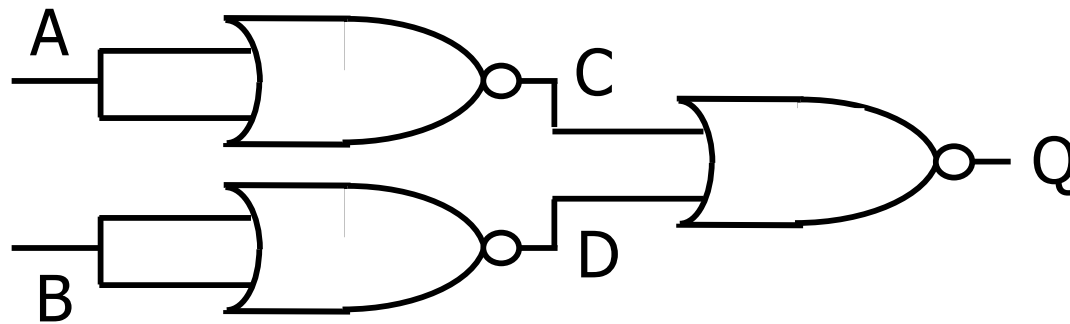*How to use **NOR** gates to build an **AND** gate?*



Truth Table

A	B	C	D	Q
0	0	1	1	0
0	1	1	0	0
1	0	0	1	0
1	1	0	0	1

Hint 1 : Use 3 NOR gates


Hint 2 : From 2 NOR gates, build 2 NOT gates

**Hint 3 : Each "NOT" gate
is an input to the 3rd NOR gate**



Universal Gates

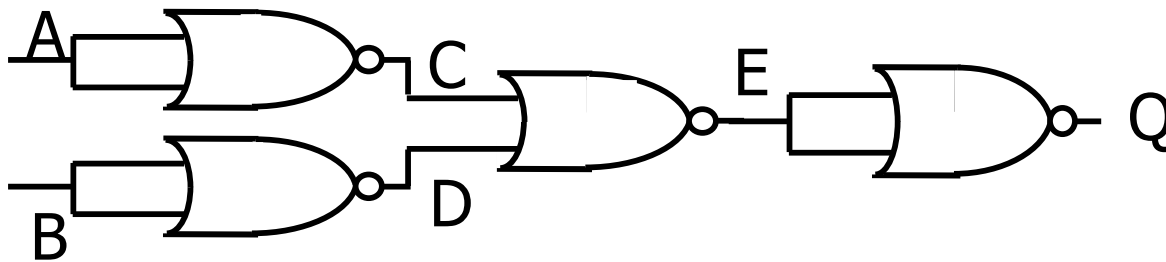*How to use **NOR** gates to build a **NAND** gate?*



Truth Table

A	B	C	D	E	Q
0	0	1	1	0	1
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	1	0

Hint 1 : Use 4 NOR gates

Hint 2 : Use 3 NOR gates to build a NAND gate

(previous lesson)

Hint 3 : Use the 4th NOR gate to build a NOT gate


Hint 4 : Insert "NOT" gate after "NAND" gate

Hint 5 : NOT-NAND = AND



Universal Gates

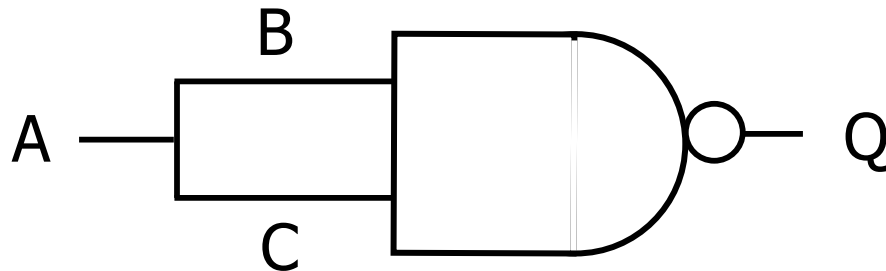How to use **NAND** gates to build a **NOT** gate?



Truth Table

A	B	C	Q
0	0	0	1
1	1	1	0

Hint!

Link inputs B & C together (to a same source).

When $A = 0$, $B = C = A = 0$


When $A = 1$, $B = C = A = 1$





Universal Gates

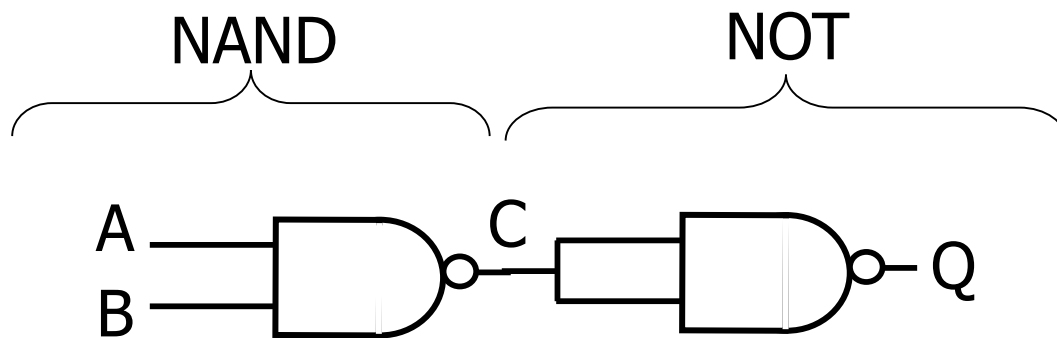*How to use **NAND** gates to build an AND gate?*



Truth Table

A	B	C	Q
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

Hint 1 : Use 2 NAND gates

Hint 2 : From a NAND gate, build a NOT gate

Hint 3 : Put this "NOT" gate after a NAND gate


Hint 4 : NOT-NAND = AND





Universal Gates

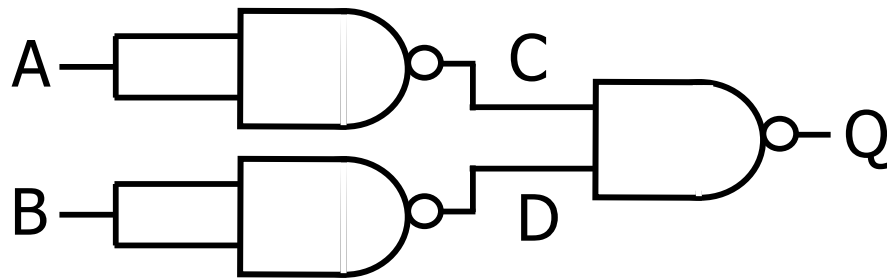*How to use **NAND** gates to build an **OR** gate?*



Truth Table

A	B	C	D	Q
0	0	1	1	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	1

Hint 1 : Use 3 NAND gates

Hint 2 : Use 2 NAND gates to build 2 NOT gates

**Hint 3 : Put the 3rd NAND gate
after the 2 "NOT" gates**






Universal Gates

*How to use **NAND** gates to build a **NOR** gate?*

Truth Table

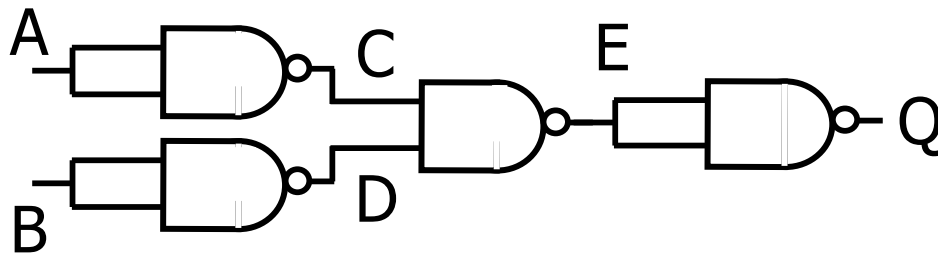


A	B	C	D	E	Q
0	0	1	1	0	1
0	1	1	0	1	0
1	0	0	1	1	0
1	1	0	0	1	0

Hint 1 : Use 4 NAND gates

Hint 2 : Use 3 NAND gates to build an OR gate

Hint 3 : Use a NOR gate to build a NOT gate

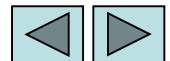
Hint 4 : Put the "NOT" gate after "OR" gate





Converting between circuits and equations

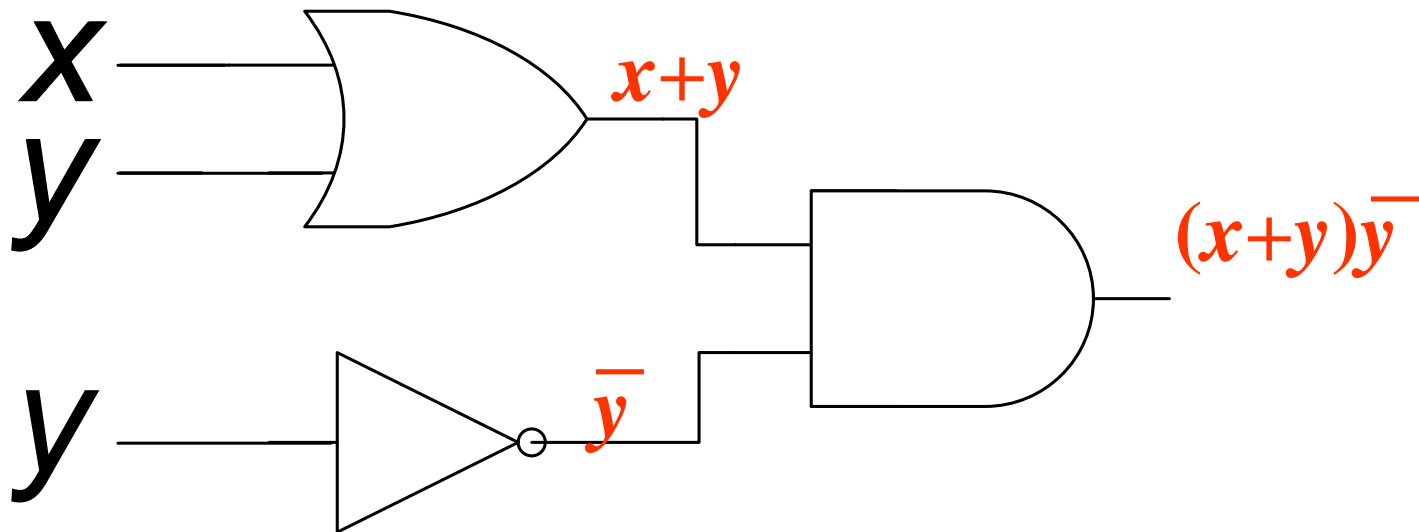- Find the output of the following circuit




- Answer: $(x+y)\bar{y}$



Converting between circuits and equations

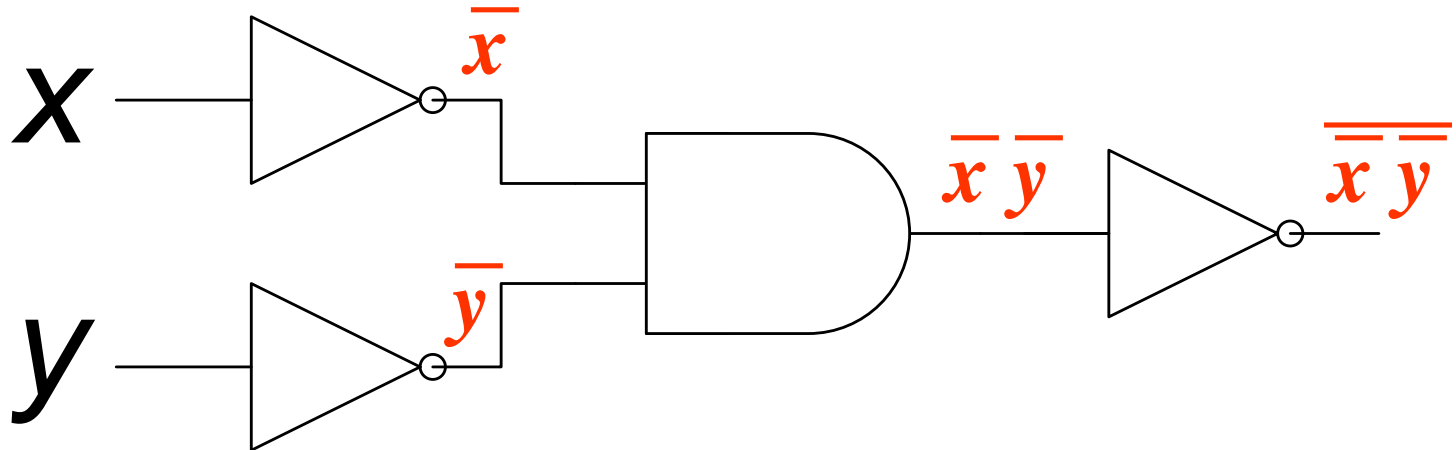- Find the output of the following circuit




- Answer: xy



Converting between circuits and equations

- Write the circuits for the following Boolean algebraic expressions

a) $\overline{x+y}$

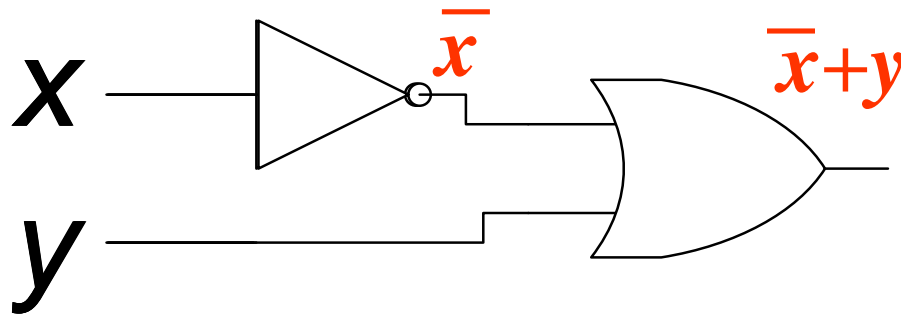




Converting between circuits and equations

- Write the circuits for the following Boolean algebraic expressions

b) $(x+y)x$

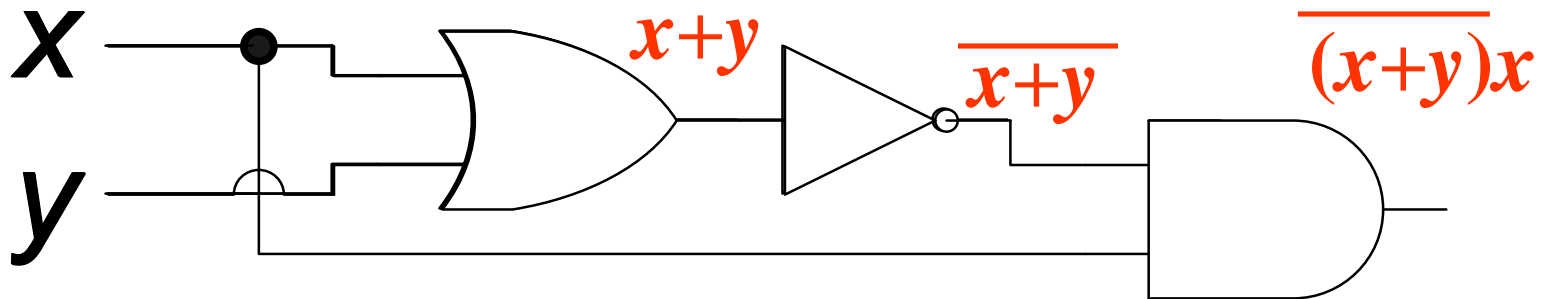



Writing X-OR using AND/OR/NOT

- $x \oplus y \equiv (x + y) \overline{(xy)}$

x	y	$x \oplus y$
1	1	0
1	0	1
0	1	1
0	0	0

