

ECE131

1. Given two numbers $X=1010100$ and $Y=1000011$, perform subtraction $X-Y$ by using 2's complement.
2. Do the BCD addition $(248)_{10} + (876)_{10}$
0001 0001 0010 0100
0001 0001 0110 0100
0001 0001 0010 0111
0001 0001 0010 1011
3. Do hexadecimal addition $(F57A)_{16} + (C85E)_{16}$
 $(1BDD8)_{16}$
 $(1BDD)_{16}$
 $(1BDE8)_{16}$
 $(BDD8)_{16}$
4. Find the duals of the function $F=AB+(AC)'+AB'C$
 $(A+B)(A'C)(A+B'+C)$
 $(A+B)(A+C)(A+B'+C)$
 $(A+B)(A+C)'(A+B'+C)$
 $(A+B)(A+C)(A+B'+C)$
5. Simplify the Boolean Expression $F=(X+Y)(X+Y')$
 Y'
 X
 X'
 $X+Y$
6. Minimize the following Boolean function- $F(A, B, C, D) = \sum m(3, 5, 7, 11, 13, 15)$
 $F(A, B, C, D) = B'C' + D$
 $F(A, B, C, D) = D$
 $F(A, B, C, D) = D'$
 $F(A, B, C, D) = AC' + D$
7. The binary numbers $A = 1101$ and $B = 1011$ are applied to the inputs of a comparator. What are the output levels?
 $A > B = 1, A < B = 0, A = B = 1$
 $A > B = 0, A < B = 1, A = B = 1$
 $A > B = 1, A < B = 0, A = B = 1$
 $A > B = 1, A < B = 0, A = B = 0$
8. Write the expression for the minterms $F(ABC) = m(1,2,4,7)$
 A or B
 A and B
 A xor B xor C
 A bar only
9. What are the input of 4:1 MUX for implementing the $F(A,B,C) = m(1,5,6,7)$ Where A,B are select lines
 $C, C, C, 1$

C,0,C,1

C,C,0,1

0,C,C,1

10. what would be the data stored in the register after the 4th clock pulse, if the group of bits 11011 is serially shifted (right-most bit first) into a 6-bit parallel output shift register with an initial state 101110.

1 101110

2


3 101111

4

5 111110

6

7 101010

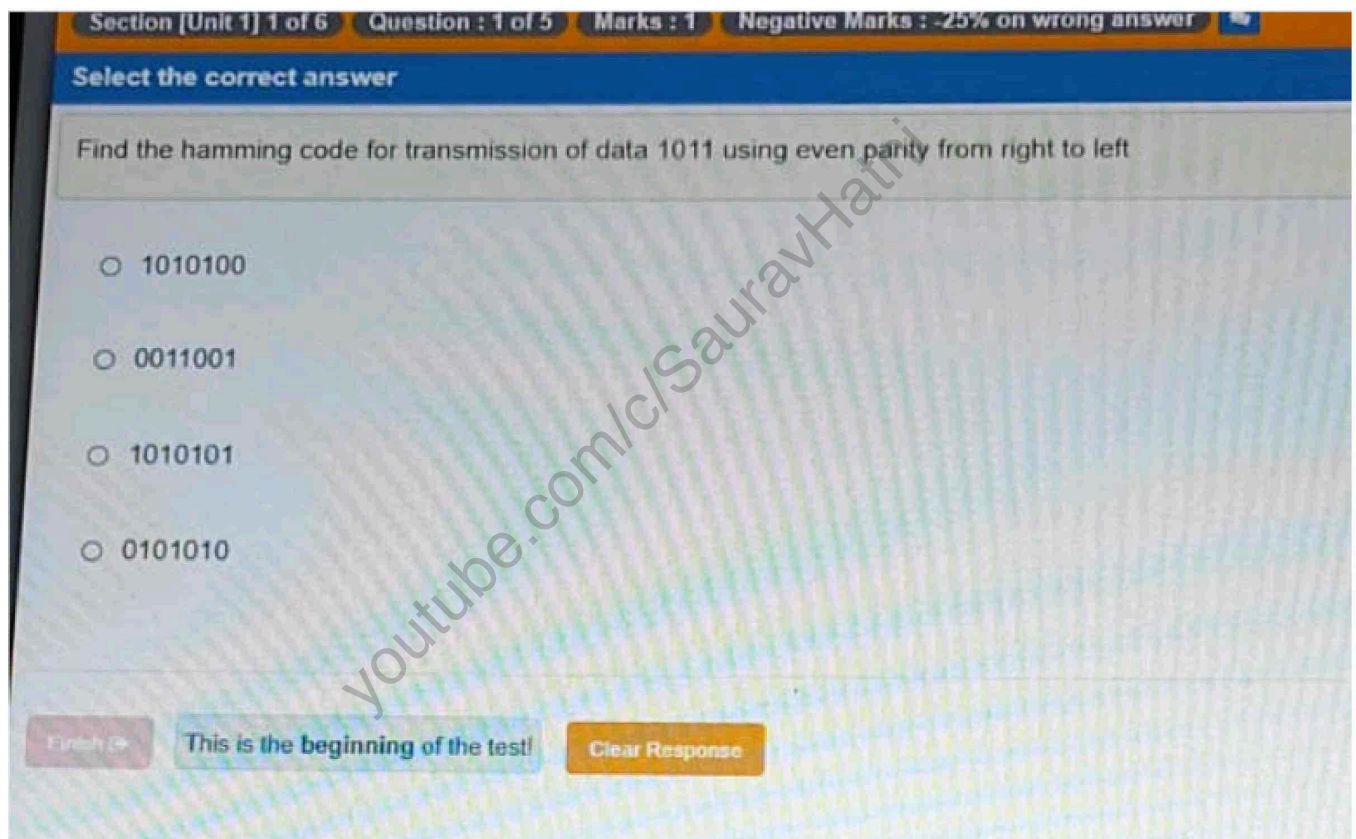


11.

\

Select the correct answer

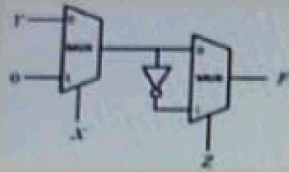Consider the circuit shown in the figure. The Boolean expression F implemented by the circuit is if $X=0, Y=0, Z=1$.



- ☐ $XYZ+XY+XZ$
- ☐ $X'YZ'+XZ+Y'Z$ or 1
- ☐ $XYZ+XY+X$
- ☐ $Z+XY+XZ$