

# Unit IV

## Introduction to Sequential Logic Circuits

*by*

**Dr. Krishan Arora**  
**Associate Professor and Head**  
**Lovely Professional University**

# Sequential Circuits

## ◆ Combinational

- The outputs depend only on the current input values
- It uses only logic gates

## ◆ Sequential

- The outputs depend on the current and past input values
- It uses logic gates and storage elements
- Example
  - ✓ Vending machine
- They are referred as finite state machines since they have a finite number of states

# Block Diagram

- ◆ **Memory elements can store binary information**
  - **This information at any given time determines the state of the circuit at that time**

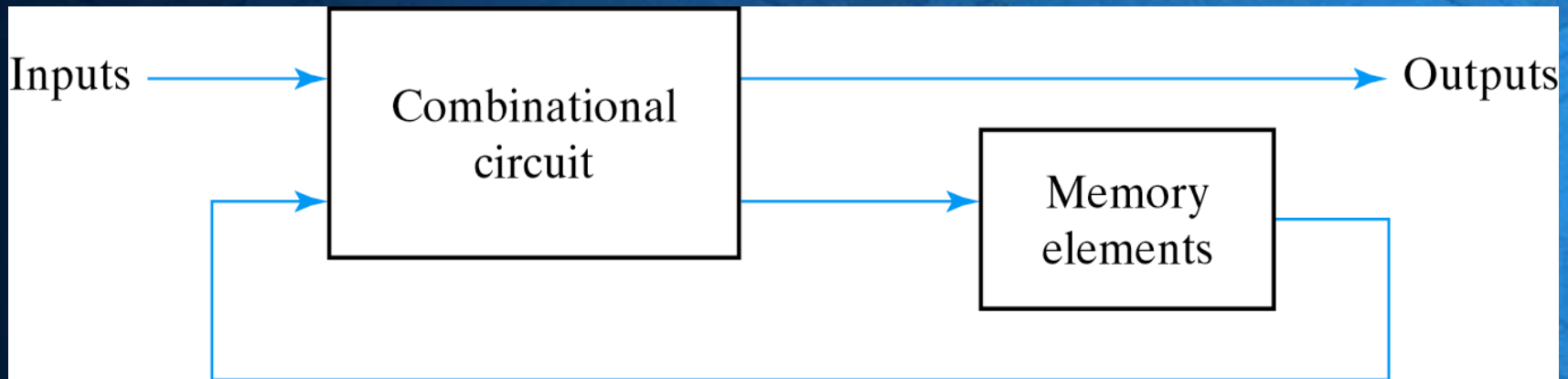


Fig. 5-1 Block Diagram of Sequential Circuit



# Sequential Circuit Types

## ◆ Synchronous

- The circuit behavior is determined by the signals at discrete instants of time
- The memory elements are affected only at discrete instants of time
- A clock is used for synchronization
  - ✓ Memory elements are affected only with the arrival of a clock pulse
  - ✓ If memory elements use clock pulses in their inputs, the circuit is called
    - Clocked sequential circuit

# Sequential Circuit Types

## ◆ ASynchronous


- The circuit behavior is determined by the signals at any instant of time
- It is also affected by the order the inputs change

# Clock


- ◆ It emits a series of pulses with a precise pulse width and precise interval between consecutive pulses
- ◆ Timing interval between the corresponding edges of two consecutive pulses is known as the clock cycle time, or period
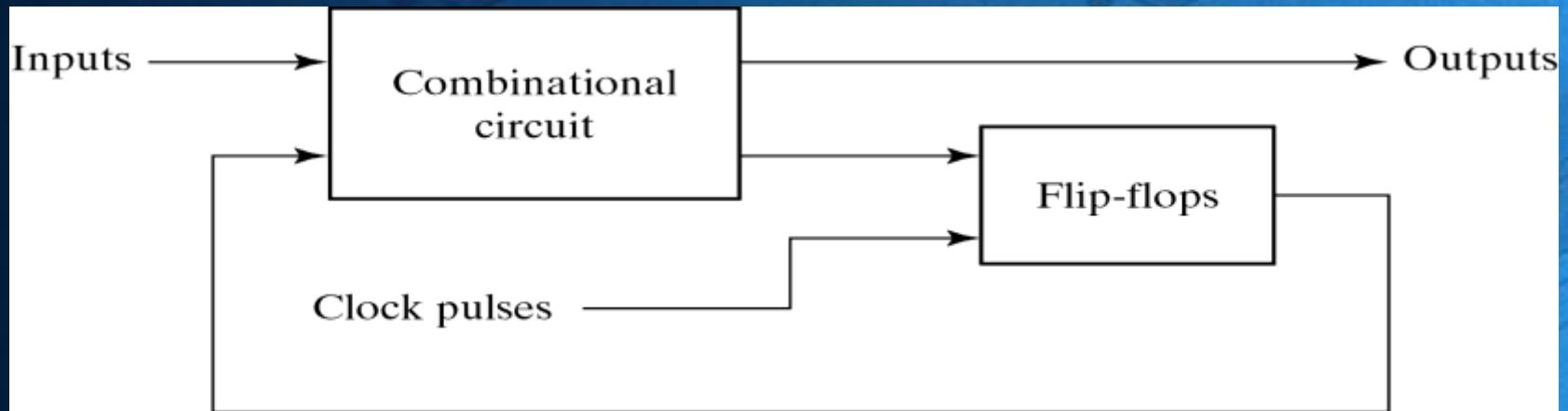
# Flip-Flops

- ◆ They are memory elements
- ◆ They can store binary information



(a) Block diagram

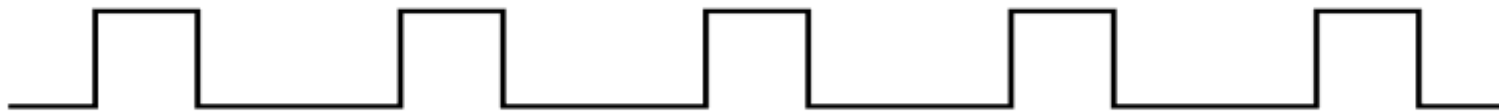

(b) Timing diagram of clock pulses

Fig. 5-2 Synchronous Clocked Sequential Circuit



# Flip-Flops

- ◆ Can keep a binary state until an input signal to switch the state is received
- ◆ There are different types of flip-flops depending on the number of inputs and how the inputs affect the binary state




# Latches

- ◆ The most basic flip-flops
  - They operate with signal levels
- ◆ The flip-flops are constructed from latches
- ◆ They are not useful for **synchronous** sequential circuits
- ◆ They are useful for **asynchronous** sequential circuits

- ◆ The difference between a latch and a flip-flop is that a latch is level-triggered (outputs can change as soon as the inputs changes) and Flip-Flop is edge-triggered (only changes state when a control signal goes from high to low or low to high).


# SR Latch with NOR

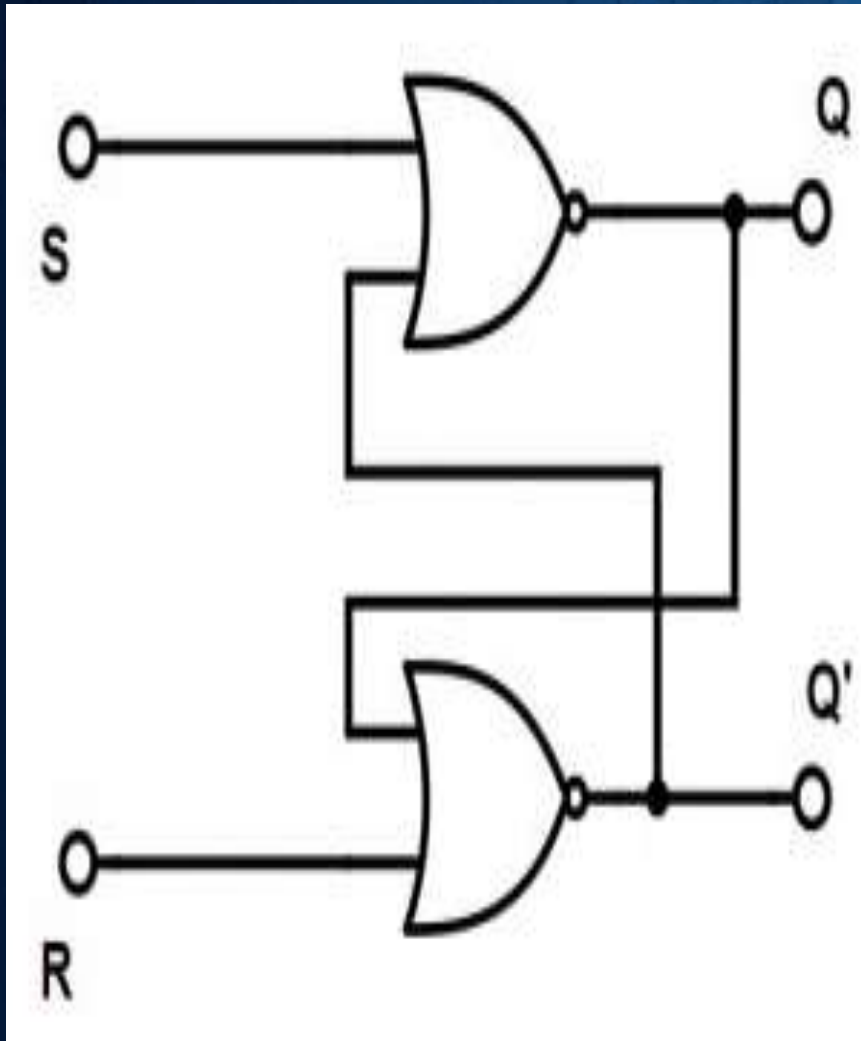

Input		Output
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

S	R	Q	State
0	0	Previous State	No change
0	1	0	Reset
1	0	1	Set
1	1	?	Forbidden

# SR Latch with NAND

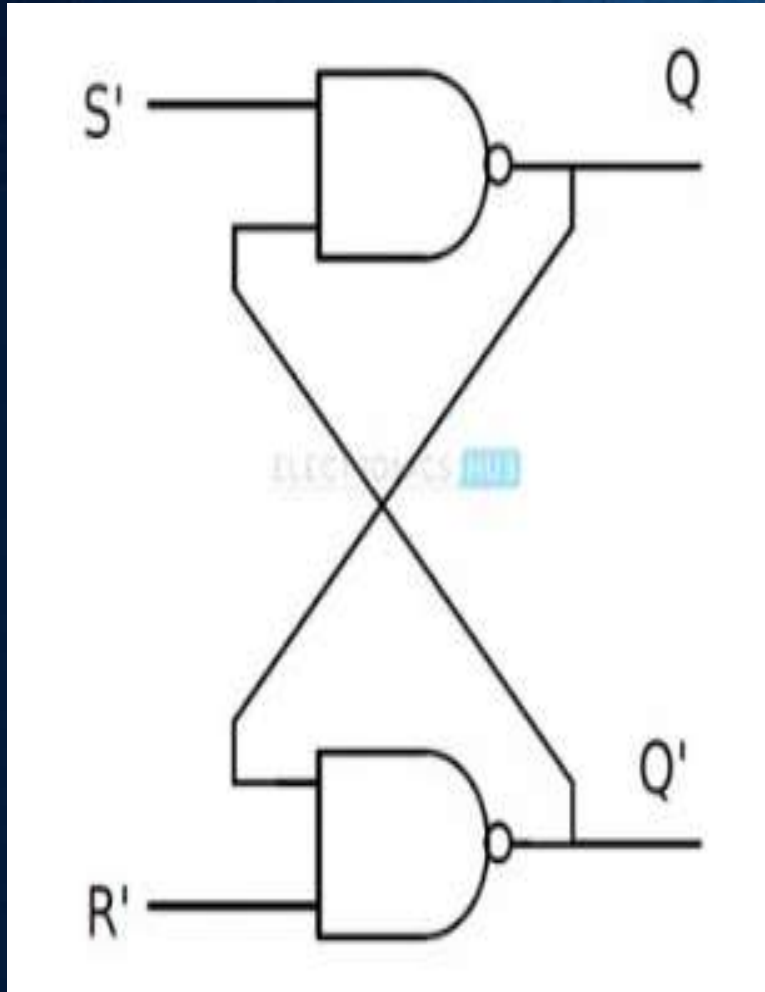

Inputs		output
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


$\bar{S}$	$\bar{R}$	Q	State
1	1	Previous State	No change
1	0	0	Reset
0	1	1	Set
0	0	?	Forbidden



# Link

- ◆ <https://www.youtube.com/watch?v=kt8d3CYWGH4>

# SR Latch with Control Input

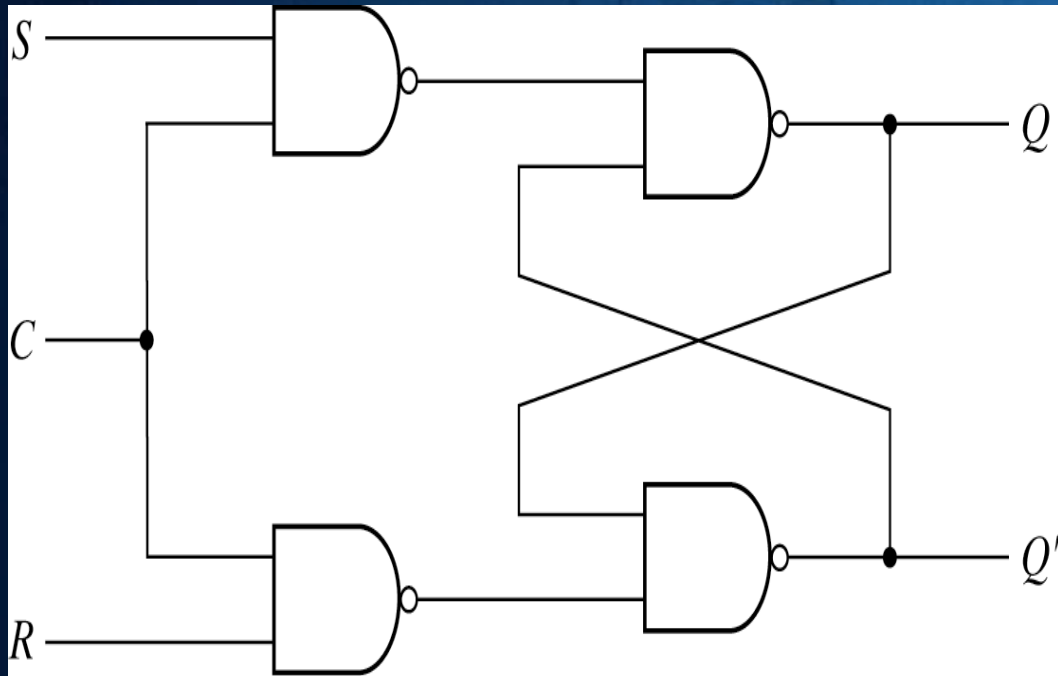


(a) Logic diagram

C	S	R	Next state of $Q$
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; Reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate

(b) Function table

Fig. 5-5 SR Latch with Control Input

# D Latch

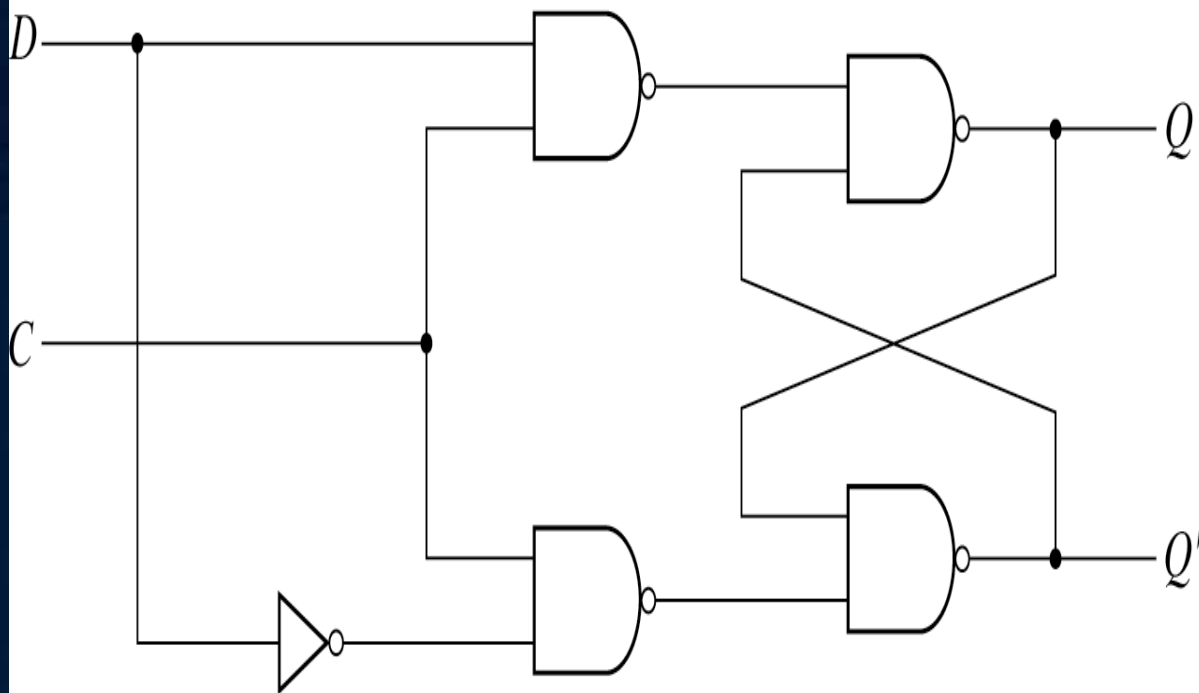

(a) Logic diagram

$C$	$D$	Next state of $Q$
0	X	No change
1	0	$Q = 0$ ; Reset state
1	1	$Q = 1$ ; Set state

(b) Function table

Fig. 5-6 D Latch

# Symbols for Latches

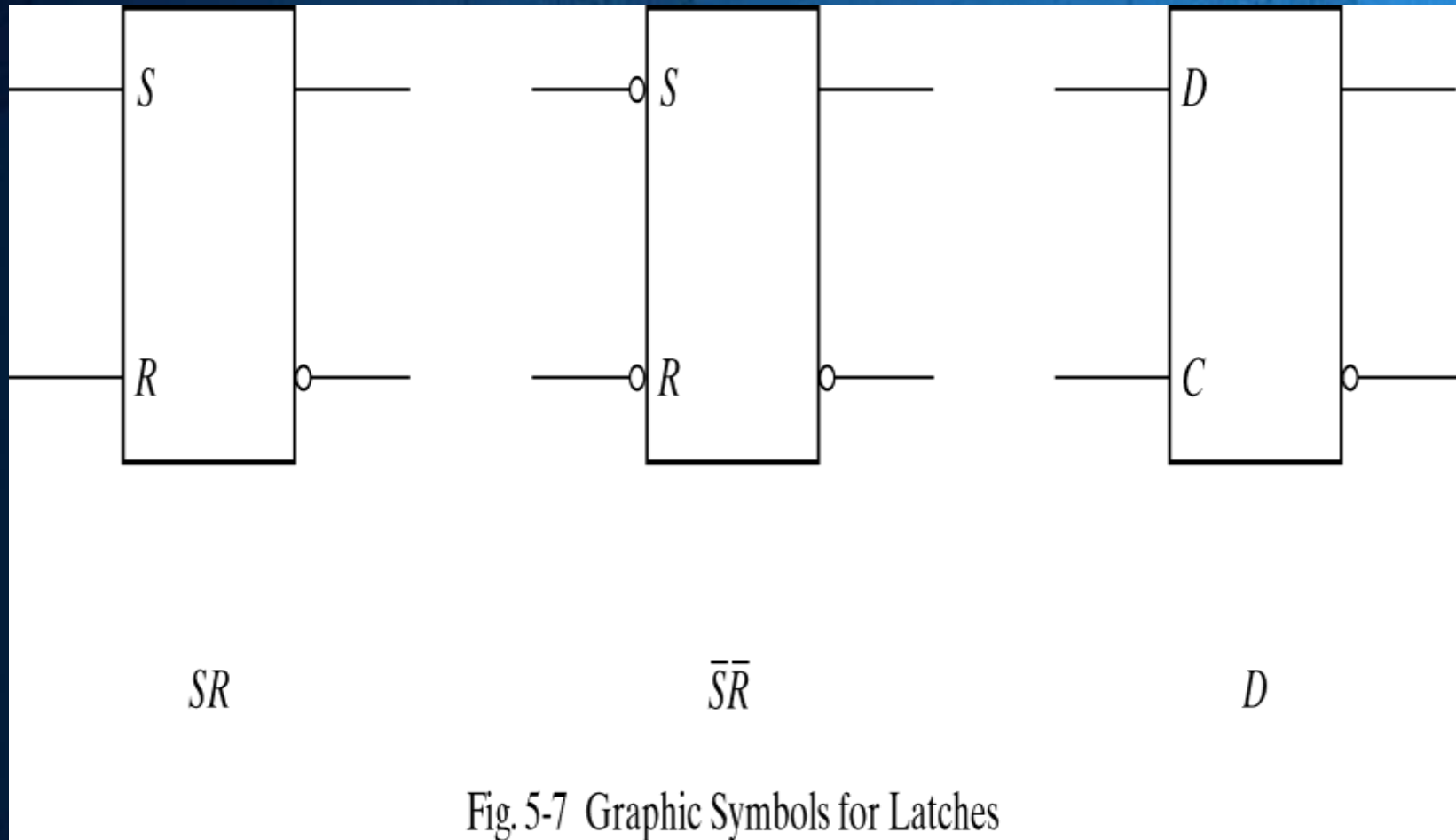


Fig. 5-7 Graphic Symbols for Latches



# Questions



# Quick Quiz (Poll 1)

- ◆ Why latches are called memory devices?
  - a) It has capability to store 8 bits of data
  - b) It has internal memory of 4 bit
  - c) It can store one bit of data
  - d) It can store infinite amount of data

# Quick Quiz (Poll 2)

◆ The full form of SR is \_\_\_\_\_

- a) System rated
- b) Set reset
- c) Set ready
- d) Set Rated