

DIGITAL ELECTRONICS

Presented by


Dr. Krishan Arora
Associate Professor and Head
Lovely Professional University

Presentation Topic

- What is synchronous counter
- A three-bit synchronous “UP” counter
- A three-bit synchronous “down” counter
- How to design synchronous counter

Synchronous counter

 - ▶ A *synchronous counter*, in contrast to an *asynchronous counter*, is one whose output bits change state simultaneously, with no ripple. The only way we can build such a counter circuit from J-K flip-flops is to connect all the clock inputs together, so that each and every flip-flop receives the exact same clock pulse at the exact same time:




Synchronous counter

- ▶ In synchronous binary counter, clock pulses are applied to the CP inputs of all flip-flops and triggered simultaneously.
- ▶ If $J = K = 0$, the flip-flop remains unchanged. If $J = K = 1$, the flip-flop Complements.

Truth table for JK flip-flop

J	K	Q
0	0	No change
0	1	0
1	0	1
1	1	Toggle

 

3 – Bit Synchronous Up Counter

State diagram of a 3-bit binary up counter.

The next step is to obtain the state table, which is derived from the state diagram

State table

Present State $Q_2 Q_1 Q_0$	Next State $Q_2 Q_1 Q_0$
0 0 0	0 0 1
0 0 1	0 1 0
0 1 0	0 1 1
0 1 1	1 0 0
1 0 0	1 0 1
1 0 1	1 1 0
1 1 0	1 1 1
1 1 1	0 0 0

Truth Table for JK Flip-Flop

Inputs		Outputs	
J	K	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Excitation Table for JK Flip-Flop

Outputs		Inputs	
Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Excitation table

Output State Transitions				Flip-flop inputs		
Present State		Next State				
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	
0	0	0	0	0	1	0 X 0 X 1 X
0	0	1	0	1	0	0 X 1 X X 1
0	1	0	0	1	1	0 X X 0 1 X
0	1	1	1	0	0	1 X X 1 X 1
1	0	0	1	0	1	X 0 0 X 1 X
1	0	1	1	1	0	X 0 1 X X 1
1	1	0	1	1	1	X 0 X 0 1 X
1	1	1	0	0	0	X 1 X 1 X 1

Q2Q1 \ Q0	0	1
	00	01
00	0	0
01	0	1
11	X	X
10	X	X

J2 map

Q2Q1 \ Q0	0	1
	00	01
00	0	1
01	X	X
11	X	X
10	0	1

J1 map

Q2Q1 \ Q0	0	1
	00	01
00	1	X
01	1	X
11	1	X
10	1	X

J0 map

Q2Q1 \ Q0	0	1
	00	01
00	X	X
01	X	X
11	0	1
10	0	0

K2 map

Q2Q1 \ Q0	0	1
	00	01
00	X	X
01	0	1
11	0	1
10	X	X

K1 map

Q2Q1 \ Q0	0	1
	00	01
00	X	1
01	X	1
11	X	1
10	X	1


K0 map



The 1s in the Karnaugh maps are grouped with "don't cares" and the following expressions for the J and K inputs of each flip-flop are obtained:

$$J_0 = K_0 = 1$$

$$J_1 = K_1 = Q_0$$

$$J_2 = K_2 = Q_1 * Q_0$$

 

  

CP	Q_C	Q_B	Q_A
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

3-bit Synchronous down counter with JK flip-flops

Present State	Next State
1 1 1	1 1 0
1 1 0	1 0 1
1 0 1	1 0 0
1 0 0	0 1 1
0 1 1	0 1 0
0 1 0	0 0 1
0 0 1	0 0 0
0 0 0	1 1 1

Present State	Next State	J_2K_2	J_1K_1	J_0K_0
111	110	d 0	d 0	d 1
110	101	d 0	d 1	1 d
101	100	d 0	0 d	d 1
100	011	d 1	1 d	1 d
011	010	0 d	d 0	d 1
010	001	0 d	d 1	1 d
001	000	0 d	0 d	d 1
000	111	1 d	1 d	1 d

K-map for each JK inputs:

$Q_2 \setminus Q_1 Q_0$	00	01	11	10
0	1	0	0	0
1	d	d	d	d

$$J_2 = \overline{Q_1} \overline{Q_0}$$

$Q_2 \setminus Q_1 Q_0$	00	01	11	10
0	d	d	d	d
1	1	0	0	0

$$K_2 = \overline{Q_1} \overline{Q_0}$$

$Q_2 \setminus Q_1 Q_0$	00	01	11	10
0	1	0	d	d
1	1	0	d	d

$$J_1 = \overline{Q_0}$$

$Q_2 \setminus Q_1 Q_0$	00	01	11	10
0	1	d	0	d
1	1	d	0	d


$$K_1 = \overline{Q_0}$$

$Q_2 \setminus Q_1 Q_0$	00	01	11	10
0	1	d	d	1
1	1	d	d	1

$$J_0 = 1$$

$Q_2 \setminus Q_1 Q_0$	00	01	11	10
0	d	1	1	d
1	d	1	1	d

$$K_0 = 1$$

 


How to design synchronous counter

- ▶ For synchronous counters, all the flip-flops are using the same CLOCK signal. Thus, the output would change synchronously.
- ▶ Procedure to design synchronous counter are as follows:-
- ▶ **STEP 1:** Obtain the State Diagram.
- ▶ **STEP 2:** Obtain the Excitation Table using state transition table for any particular FF (JK or D). Determine number of FF used.
- ▶ **STEP 3:** Obtain and simplify the function of each FF input using K-Map.
- ▶ **STEP 4:** Draw the circuit.

How to design synchronous counter

 - ▶ Design a MOD-4 synchronous up-counter, using JK FF.
- ▶ **STEP 1:** Obtain the State transition Diagram



How to design synchronous counter

STEP 2: Obtain the Excitation table. Two JK FF are used.

OUTPUT TRANSITION		FF INPUT	
Q_N	Q_{N+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Excitation table

Present State	Next State	Input, J K	
B A	B A	$J_B K_B$	$J_A K_A$
0 0	0 1	0 X	1 X
0 1	1 0	1 X	X 1
1 0	1 1	X 0	1 X
1 1	0 0	X 1	X 1

How to design synchronous counter

STEP 3: Obtain the simplified function using K-Map

		B		
		0	1	
A	0	0	1	$J_B = A$
	1	X	X	


		B		
		0	1	
A	0	X	X	$K_B = A$
	1	0	1	

		B		
		0	1	
A	0	1	X	$J_A = 1$
	1	1	X	

		B		
		0	1	
A	0	X	1	$K_A = 1$
	1	X	1	

How to design synchronous counter

STEP 4: Draw the circuit diagram.

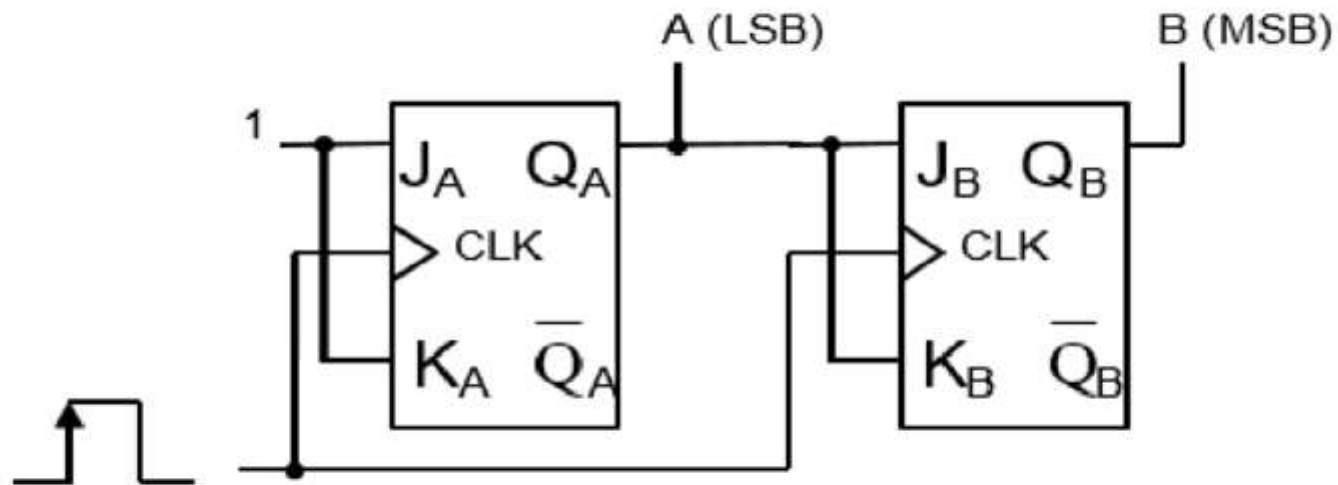

(MOD-4 synchronous up-counter)

Quick Quiz

Ripple counters are also called _____

- a) SSI counters
- b) Asynchronous counters
- c) Synchronous counters
- d) VLSI counters