

# UNIT VI



Analog to digital converter  
And  
Digital to analog converter

# Part One



## Analog to Digital converter

# Outline




- ❖ Definition
- ❖ Why we need ADC
- ❖ Types ADC and each basic operation
- ❖ Applications of analog to digital converter

# Definition

- ❖ An electronic integrated circuit which transforms a signal from analog(continues) to digital(discrete) form
- ❖ Analog signals are directly measurable quantities
- ❖ Digital signals only have two states for digital computer we refer to binary states, 0 and 1
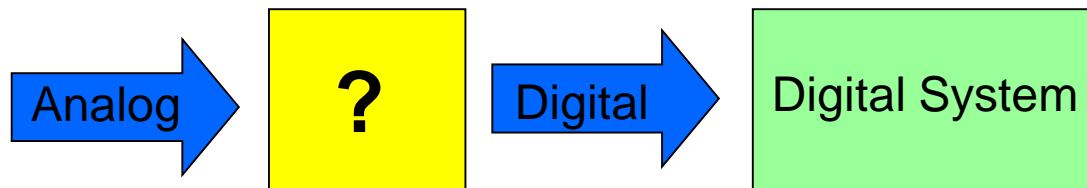
# Continue

- ❖ The heart of computer-based data acquisition is usually the analog to digital converter
- ❖ Basically this device is digital volt meter
- ❖ Digital Systems require discrete digital data




# Continue


- ❖ Digital computers require signals to be in digital form whereas most instrumentation transducers have an output signal in analogue form.
- ❖ ADC conversion is therefore required at the interface between analogue transducers and the digital computer

# Examples of use

- Voltmeter

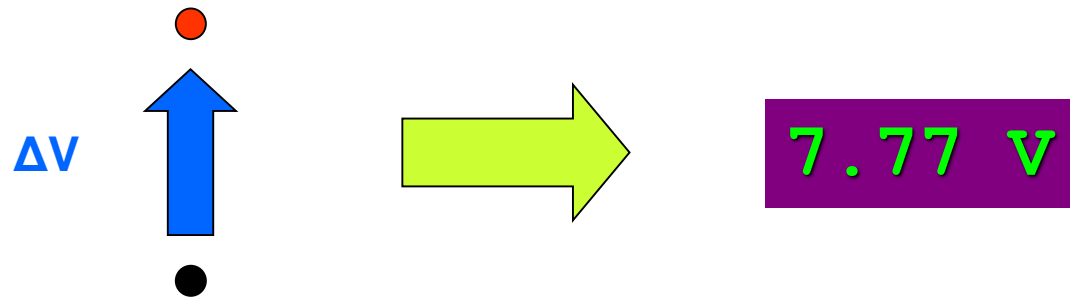

- Cell phone (microphone)

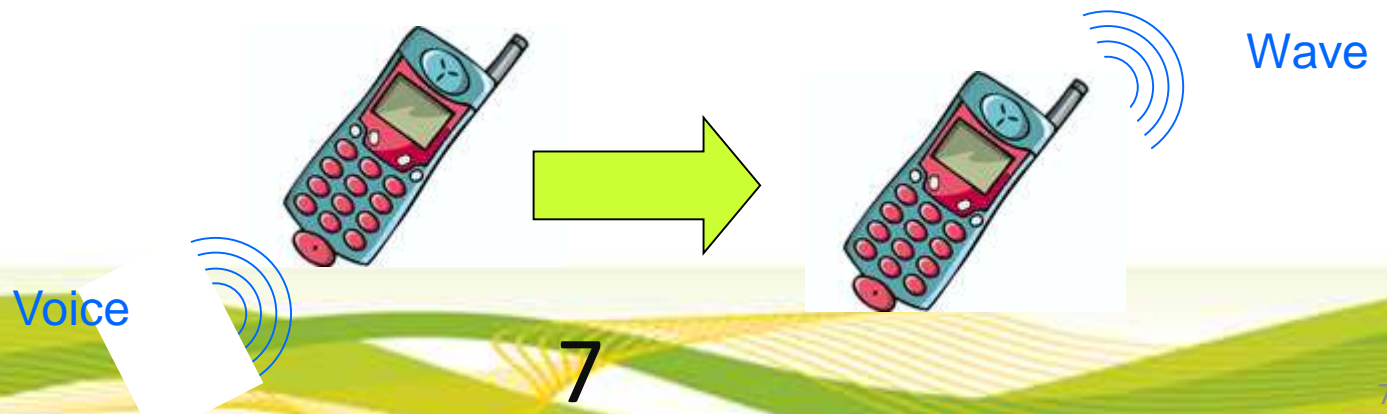

# Why we need ADC

- ❖ Microprocessors can only perform complex processing on digitized signals
- ❖ When signals are in digital form they are less susceptible to the deleterious effects of additive noise
- ❖ ADC Provides a link between the analog world of transducers and the digital world of signal processing and data handling.



# Types of analog to digital converter



- ❖ There are many different types of analog to digital converters
- ❖ Each offers something in the way of
  - ✓ Speed
  - ✓ Cost
  - ✓ Power dissipation
  - ✓ complexity

# Types of analog to digital converter

- ❖ Counter type
- ❖ Successive approximation
- ❖ There are many types such as flash type and sigma-delta but we will cover these two types

# Counter type

- ❖ One of the simplest types of analog to digital converter is counter type ADC
- ❖ The input signal of ADC is connected to the signal input of its internal comparator
- ❖ The ADC then systematically increases the voltage of the reference input of the comparator until the reference becomes larger than the signal

# Continue

- ❖ And the comparator output goes to 0
- ❖ Ex: consider an input signal is 4.78 volts. The initial comparator's input would be 2.5 volts
- ❖ The comparator compares the two value then the result this is less than 4.78 then the next higher voltage (5.00 volts) is applied
- ❖ The comparator compares the two value and says this is greater than 4.78 and switches 0

# Continue

- ❖ The digital output of the ADC is the number of times the ADC increase the voltage after starting at the initial 2.5 volts
- ❖ This scheme is relatively simple , but as the number of ADC increases the time it takes to scan through all possible values lower than input will grow quickly


# Components of counter type

- ❖ This type of converter uses some type of counter as part of its operation
- ❖ Counter type contains the following elements:
  - Digital to analog converter
  - Some type of counting mechanism
  - Comparator
  - clock

# Features of counter type


- ❖ Use a clock to index the counter
- ❖ Use DAC to generate analog signal to compare against input
- ❖ Comparator is used to compare  $V_{IN}$  and  $V_{DAC}$  where  $V_{IN}$  is the signal to be digitized
- ❖ The input to the DAC is from the counter

# Operation of counter type

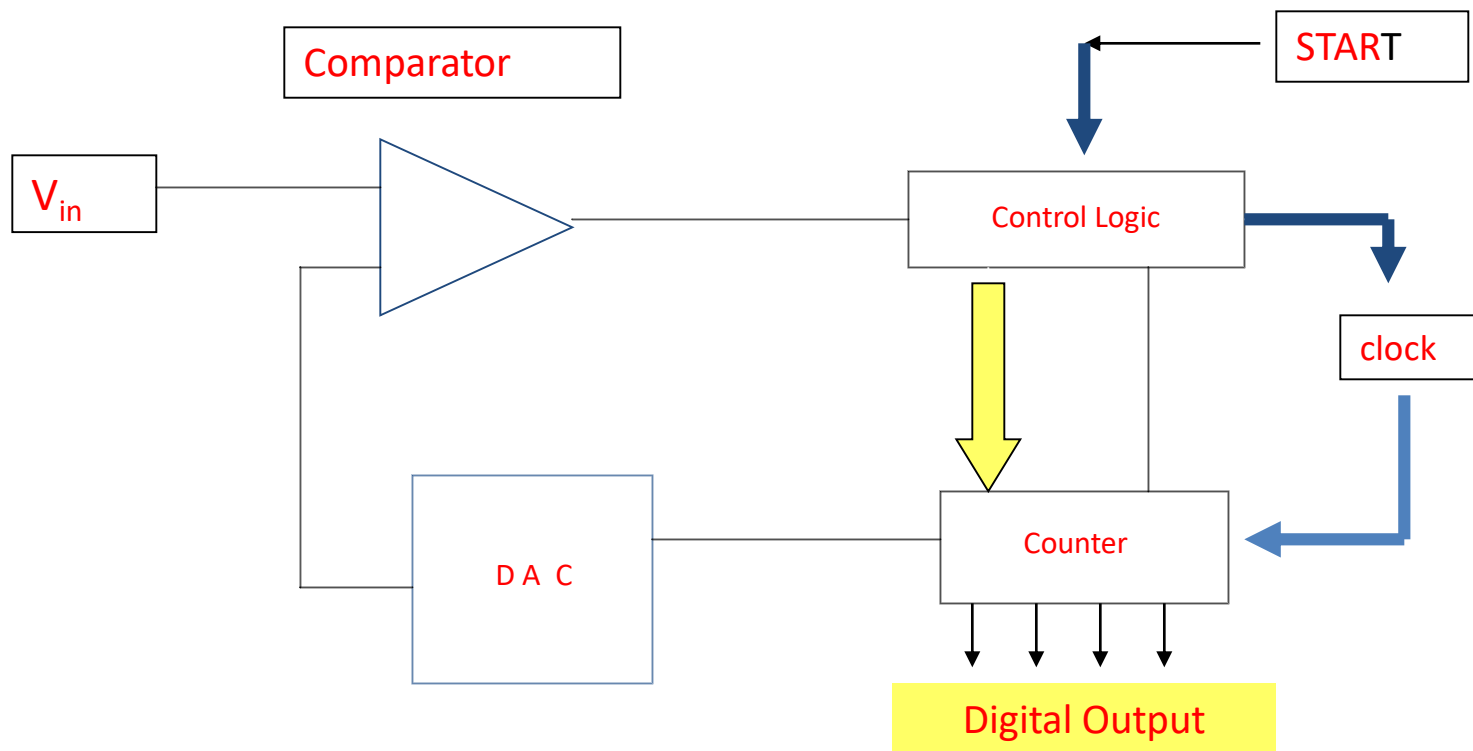



# Operation of counter type

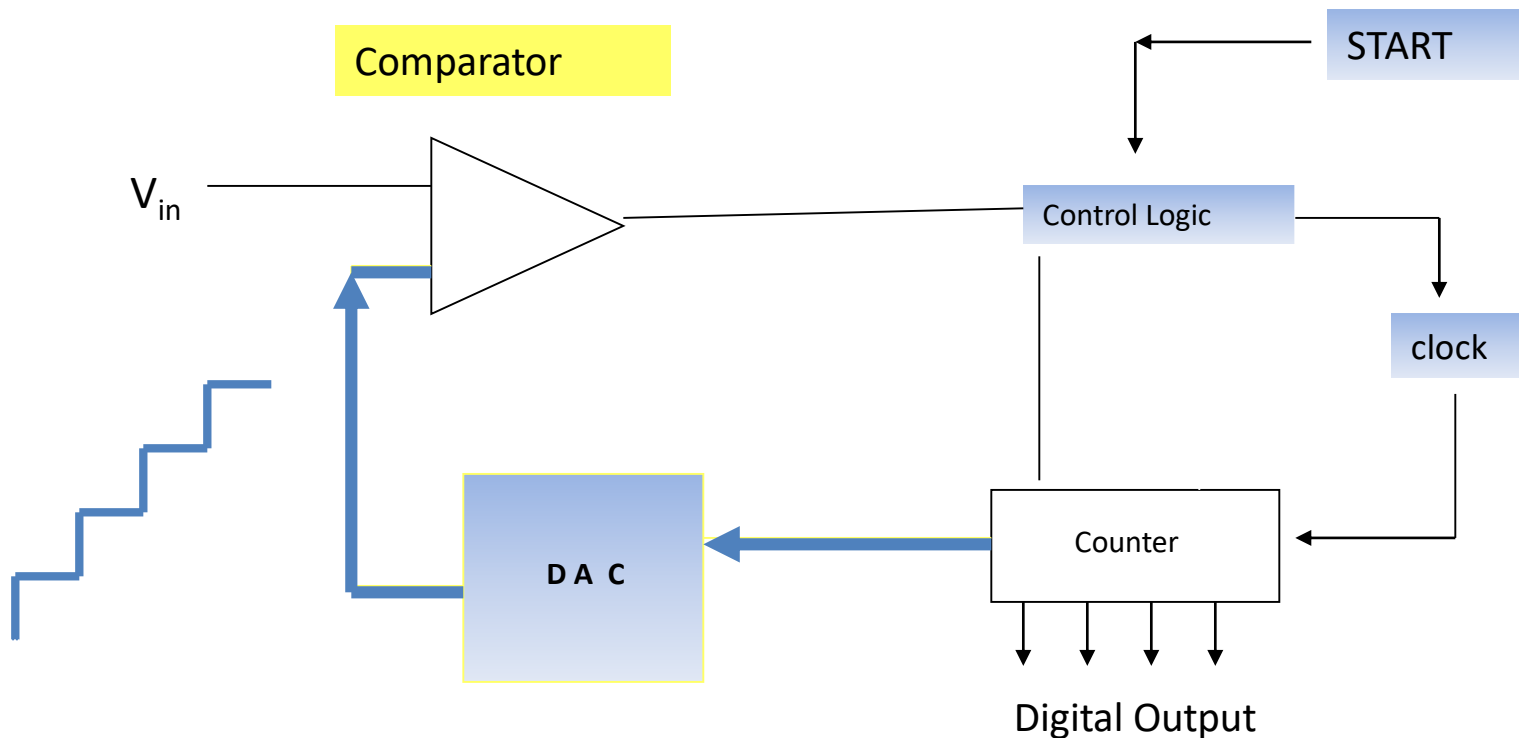

# Quick Quiz

- **Which of following is not a type of ADC?**
  - (a) Flash ADC
  - (b) Dual slope ADC
  - (c) Recessive approximation ADC
  - (d) sigma-delta ADC

# Quick Quiz



- **A DAC is a**
  - (a) digital-to-analog computer
  - (b) digital analysis calculator
  - (c) data accumulation converter
  - (d) digital-to-analog converter