

Unit V

Synchronous Counters

by

Dr. Krishan Arora
Associate Professor and Head
Lovely Professional University

Lock Out condition in Synchronous Counters

- Sometimes a counter may find itself in some **unused states**.
- It happens when the next state of some unused state is again some unused one and if by chance the counter happens to find itself in some unused state and **never arrives** at in used state then this condition is called “Lock Out”.

- **Solution:**

An **additional circuit** is required to ensure that “lock out” does not occur. The counter should be designed using the next state to be initial state from the unused state.


EXAMPLE : Synchronous Counter Design Problem:

Design a MOD-5, 3-bit synchronous counter to count in the following sequence: 2, 3, 5, 1, 7. The counter must be self-starting with the count states of 0, 4, and 6 leading directly to 2.

Solution

- Follow these procedures:
- 1. Create a state transition diagram.
- 2. Create a counter excitation table by listing the present state and next state sequence.
- 3. Expand the table by adding the J and K input states for each flip
- 4. Determine the logic functions for the J and K inputs as a function of the present states.
- 5. Analyze the counter to verify the design.
- 6. Construct and test the counter

 - The state transition diagram for the counter is shown in Figure



J-K Excitation Table

Present State Q_N	Next State Q_N	Inputs		Condition
		J	K	
0	0	0	x	No Change, Reset
0	1	1	x	Toggle, Set
1	0	x	1	Toggle, Reset
1	1	x	0	No Change, Set

Present State-Next State Table

Present State			Next State		
Q_C	Q_B	Q_A	Q_C	Q_B	Q_A
0	0	0	0	1	0
1	0	0	0	1	0
1	1	0	0	1	0
0	1	0	0	1	1
0	1	1	1	0	1
1	0	1	0	0	1
0	0	1	1	1	1
1	1	1	0	1	0

Counter Excitation Table

Present State			Next State			Present Input					
Q _C	Q _B	Q _A	Q _C	Q _B	Q _A	J _C	K _C	J _B	K _B	J _A	K _A
0	0	0	0	1	0	0	X	1	X	0	X
1	0	0	0	1	0	X	1	1	X	0	X
1	1	0	0	1	0	X	1	X	0	0	X
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	1	1	X	X	1	X	0
1	0	1	0	0	1	X	1	0	X	X	0
0	0	1	1	1	1	1	X	1	X	X	0
1	1	1	0	1	0	X	1	X	0	X	1

- The above Table do not follow counting order, so be careful when filling in the K-maps. The K-maps and resulting logic functions for the J and K inputs are shown in Figure

K-maps

$Q_C Q_B \backslash Q_A$		0	1
0	0	0	1
0	1	0	1
1	1	x	x
1	0	x	x

$$J_C = Q_A$$

$K_C = 1$ by inspection of table

(a)

Q_A	0	1
$Q_C Q_B$		
0 0	1	1
0 1	x	x
1 1	x	x
1 0	1	0

$$J_B = \overline{Q_C} Q_A$$

Q_A	0	1
$Q_C Q_B$		
0 0	x	x
0 1	0	1
1 1	0	0
1 0	x	x

$$K_B = \overline{Q_C} Q_A$$

(b)

$Q_A \backslash Q_C Q_B$	0	1
0 0	0 ₀	x ₁
0 1	1 ₂	x ₃
1 1	0 ₆	x ₇
1 0	0 ₄	x ₅


$$J_A = \overline{Q_C} Q_B$$

$Q_A \backslash Q_C Q_B$	0	1
0 0	x	0
0 1	x	0
1 1	x	1
1 0	x	0

$$K_A = Q_C Q_B$$

(c)

Synchronous Counter

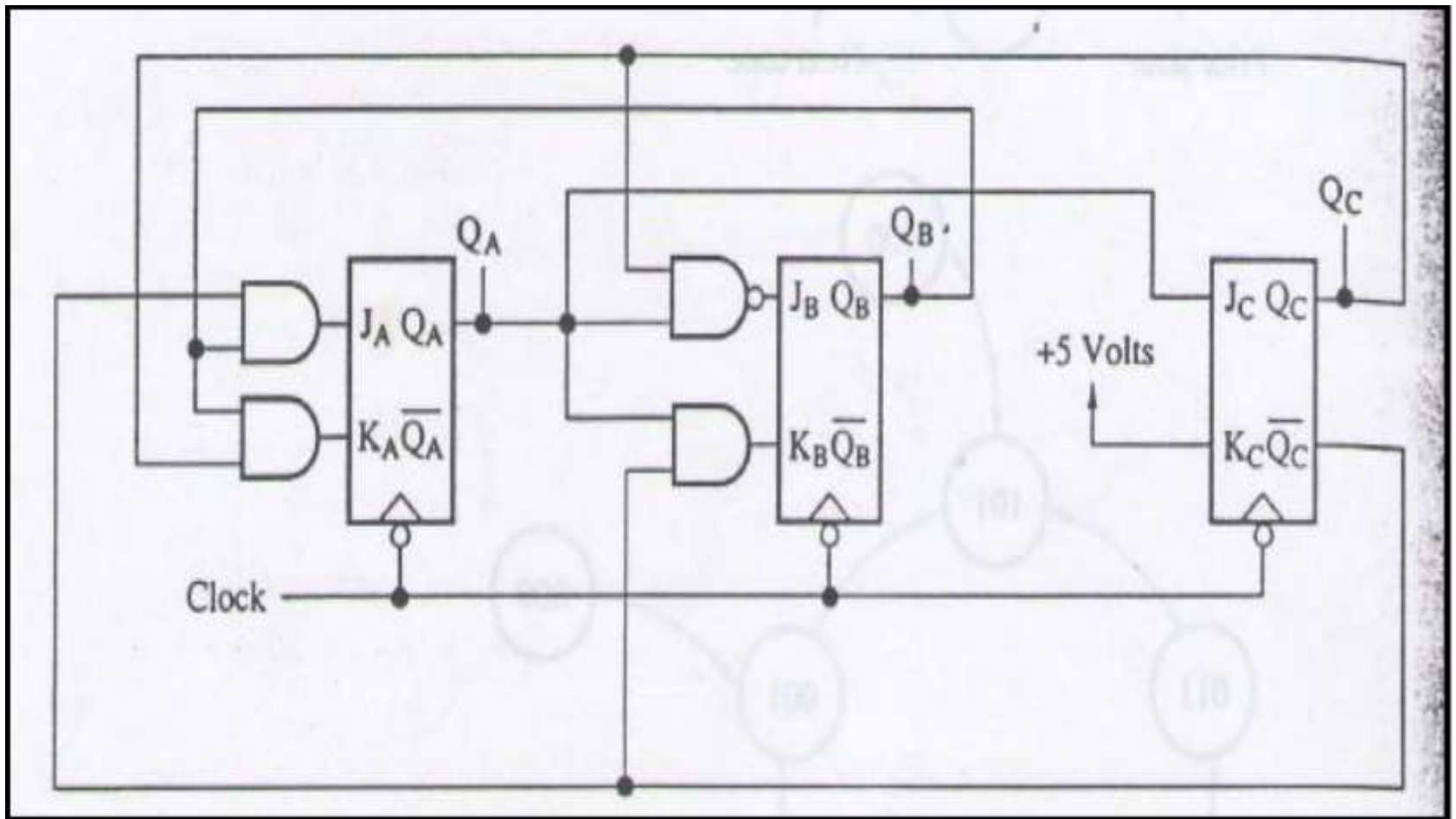

Synchronous Counter with Random Sequence

- Example: Design a counter with a sequence 4,7,3,0,2,4,..... Using JK FlipFlop?

Synchronous Counter with Random Sequence

3 bits = 3 F/F.

- Example: Design a counter with a sequence 4, 7, 3, 0, 2, 4, Using JK FlipFlop?

State Table:

Q_2	Q_1	Q_0	Q_2^+	Q_1^+	Q_0^+	J_2	K_2	J_1	K_1	J_0	K_0
4	1	0	0	1	1	X	0	1	X	1	X
7	1	1	1	0	1	X	1	X	0	X	0
3	0	1	1	0	0	0	X	X	1	X	1
0	0	0	0	1	0	0	X	1	X	0	X
2	0	1	0	1	0	1	X	X	1	0	X

Unused state \rightarrow 1, 5, 6.
Used state \rightarrow ✓

- 1) State Table
- 2) K-maps:
- 3) Design.

K-map:

Q_2	$\bar{Q}_1\bar{Q}_0$	\bar{Q}_1Q_0	$Q_1\bar{Q}_0$	Q_1Q_0
Q_2	0	X ¹		1
Q_2	X ⁴	X ⁵	X ⁷	X ⁶

$$J_2 = Q_1\bar{Q}_0$$

— Yourself!

E-T

	I	K
00	0	X
01	1	X
10	X	1
11	X	0

QUICK QUIZ (POLL)

The counter with sequence 0,3,1,7,4, can be designed with

- a) Three bit ripple counter
- b) Two bit synchronous counter
- c) Three bit synchronous counter
- d) All of the above

Practice Example

- Design a MOD-5, 3-bit synchronous counter to count in the following sequence: 2, 3, 5, 1, 7. To modify the design and minimize the additional gates required for the J and K inputs, route the unused states to their next natural count state.
- In other words, route 0 to 1, 4 to 5, and 6 to 7.