
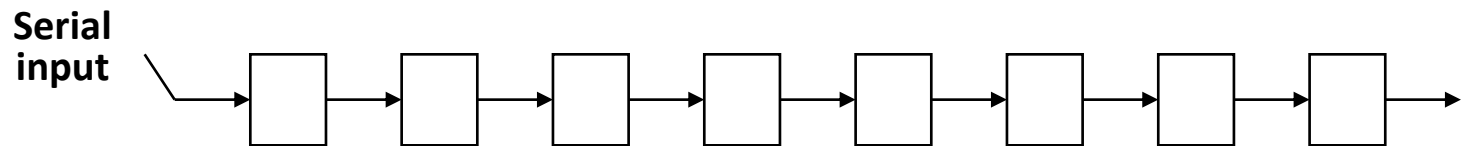


Shift Microoperations

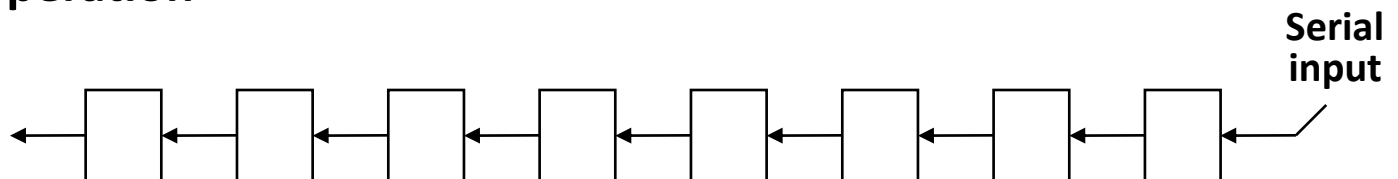- There are three types of shifts
 - *Logical shift*
 - *Circular shift*
 - *Arithmetic shift*
- What differentiates them is the information that goes into the serial input
- A right shift operation




- A left shift operation




Logical Shift

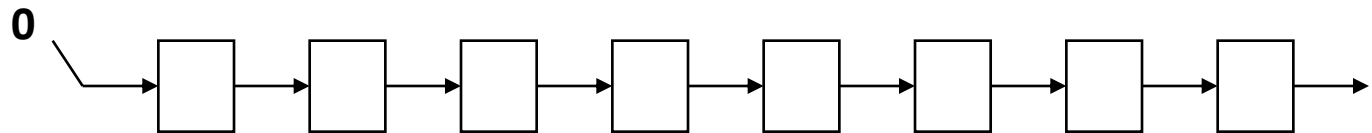- In a logical shift the serial input to the shift is a 0.
- A right logical shift operation:




- A left logical shift operation:

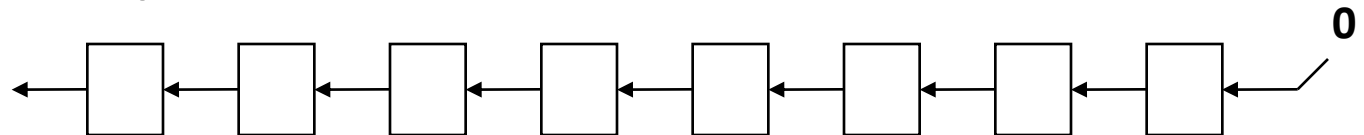


- In a Register Transfer Language, the following notation is used
 - *shl* for a logical shift left
 - *shr* for a logical shift right
 - Examples:
 - $R2 \leftarrow shr\ R2$
 - $R3 \leftarrow shl\ R3$

Circular Shift

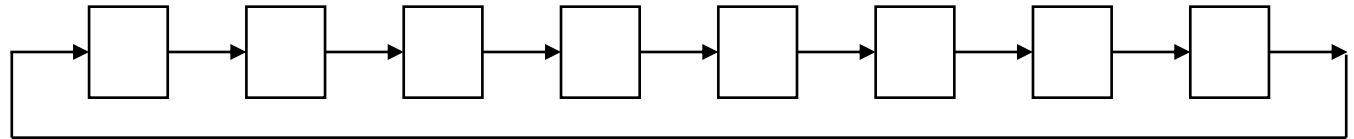- In a circular shift the serial input is the bit that is shifted out of the other end of the register.
- A right circular shift operation:




- A left circular shift operation:

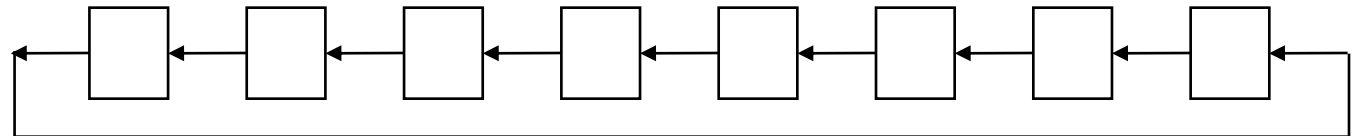


- In a RTL, the following notation is used
 - *cil* for a circular shift left
 - *cir* for a circular shift right
 - Examples:
 - $R2 \leftarrow cir\ R2$
 - $R3 \leftarrow cil\ R3$

Arithmetic Shift

- An arithmetic shift is meant for signed binary numbers (integer)
- An arithmetic left shift **multiplies** a signed number **by two**
- An arithmetic right shift **divides** a signed number **by two**
- Sign bit : 0 for positive and 1 for negative
- The main distinction of an arithmetic shift is that it must keep the sign of the number the same as it performs the multiplication or division
- A right arithmetic shift operation:

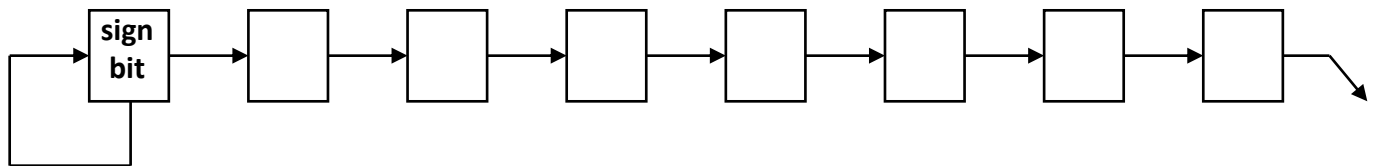


- A left arithmetic shift operation:

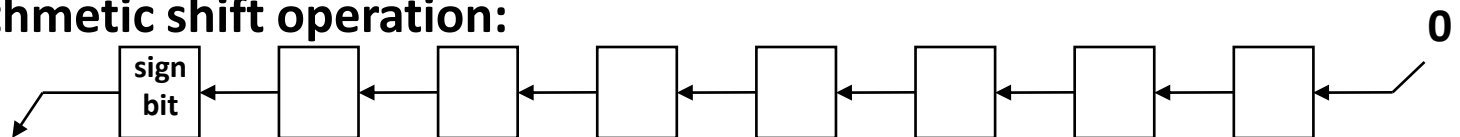

Arithmetic Shift

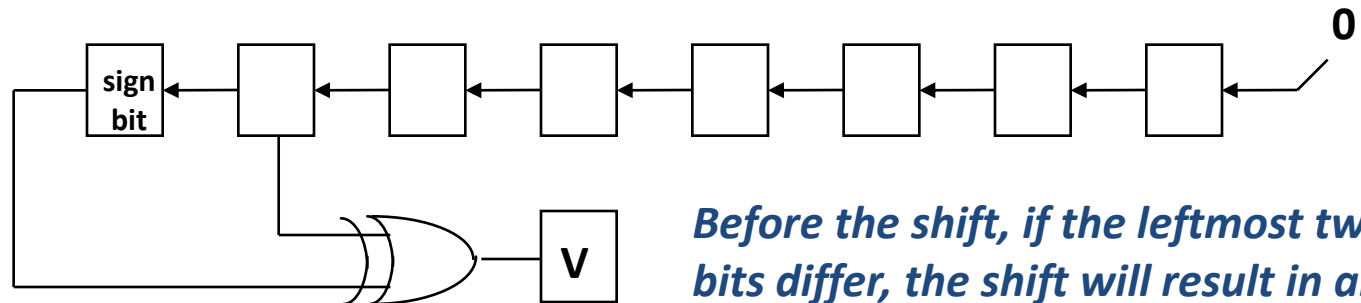- An left arithmetic shift operation must be checked for the overflow



Before the shift, if the leftmost two bits differ, the shift will result in an overflow

- In a RTL, the following notation is used
 - *ashl* for an arithmetic shift left
 - *ashr* for an arithmetic shift right
 - Examples:
 - » $R2 \leftarrow ashr R2$
 - » $R3 \leftarrow ashl R3$

- An arithmetic left shift **multiplies** a signed number by

A) 4


B) 8

C) 2

D) 16


Hardware Implementation of Shift Microoperation

◆ Hardware Implementation(Shifter) :

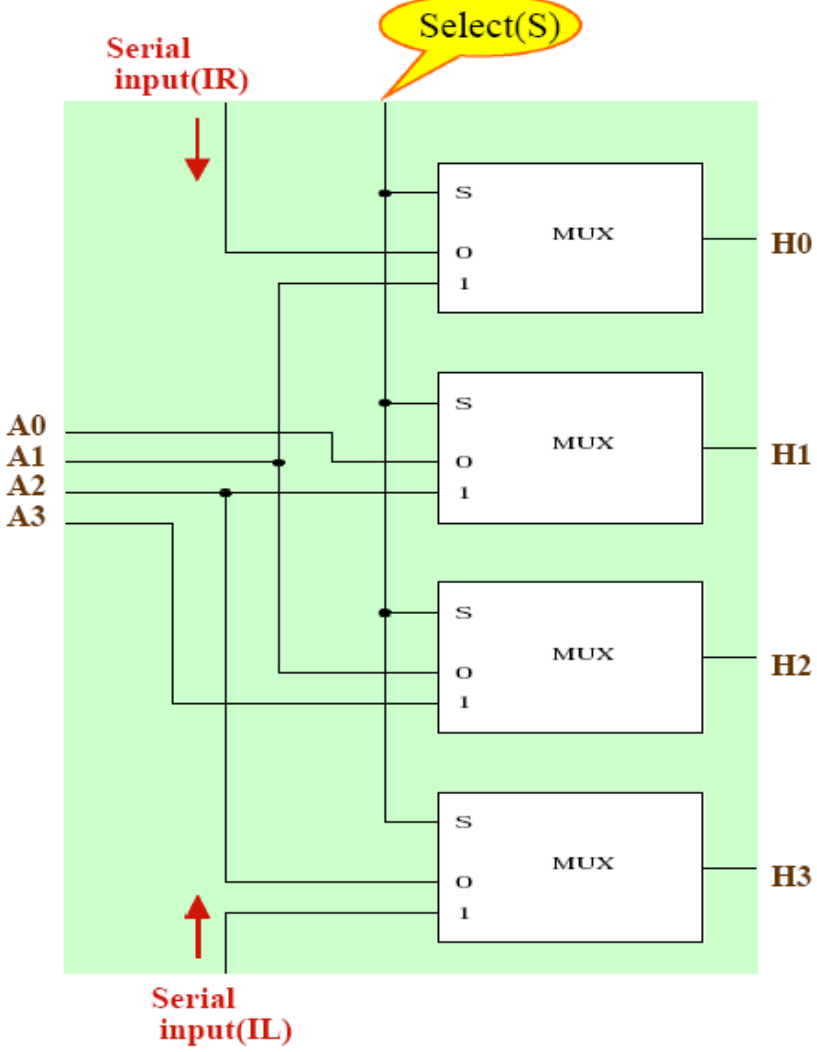


Function Table				
Select	output			
	H0	H1	H2	H3
0	IR	A0	A1	A2
1	A1	A2	A3	IL

Arithmetic Circuits

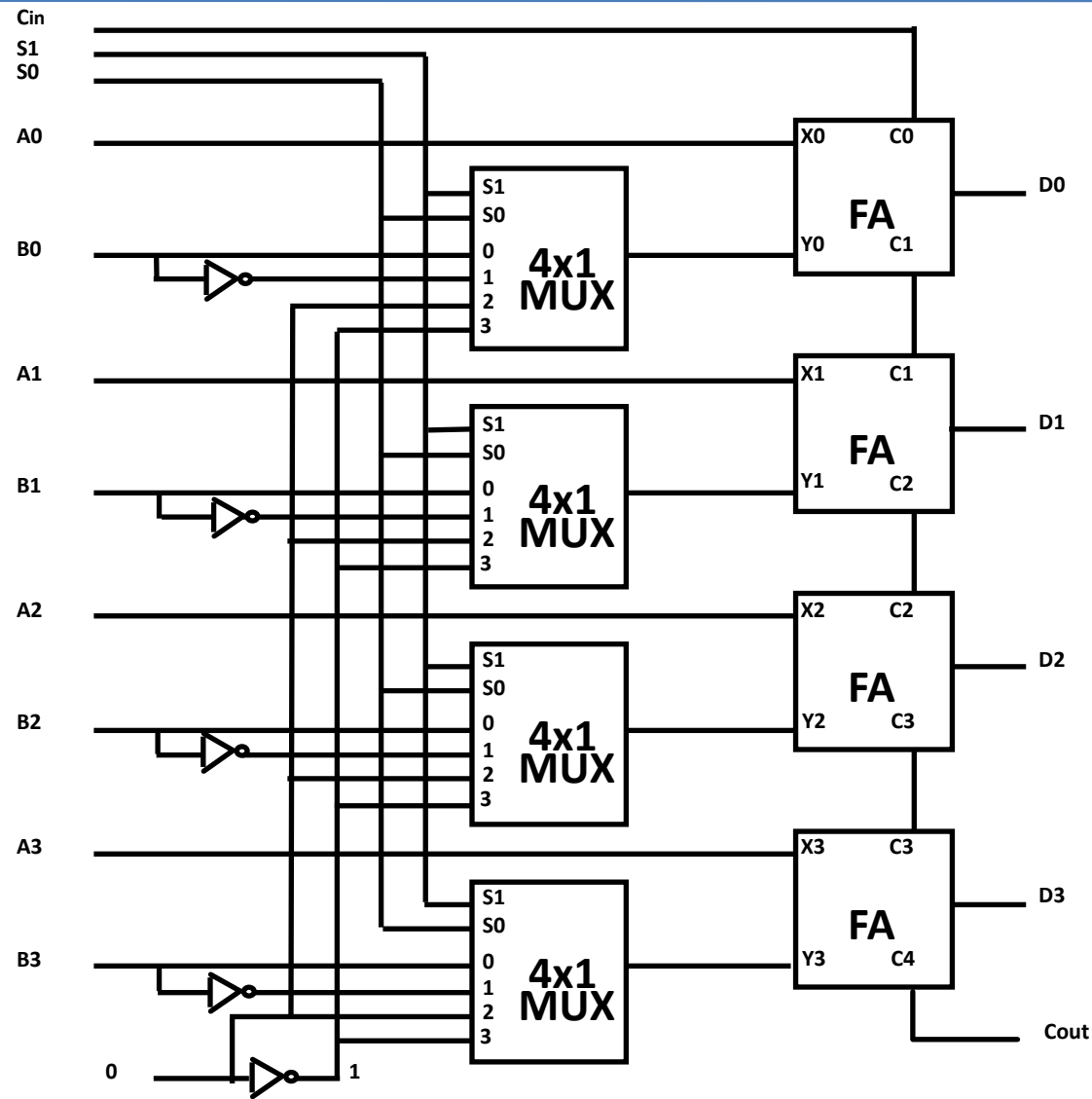

Select			Input	Output
S1	S0	C _{in}	Y	D=A+Y+C _{in}
0	0	0	B	D=A+B
0	0	1	B	D=A+B+1
0	1	0	B'	D=A+B'
0	1	1	B'	D=A+B'+1
1	0	0	0	D=A
1	0	1	0	D=A+1
1	1	0	1	D=A-1
1	1	1	1	D=A


Hardware Implementation

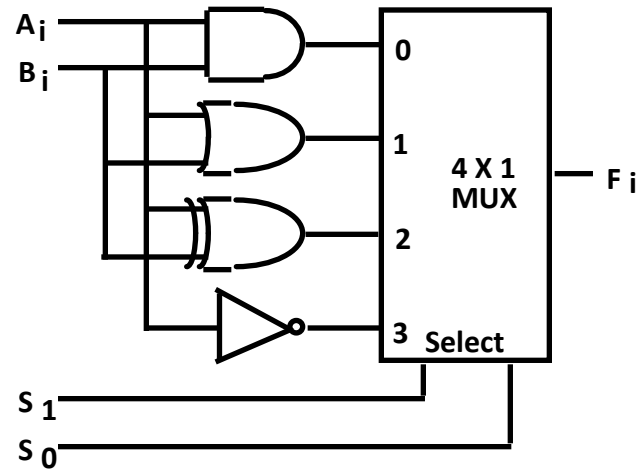


Function table

S_1	S_0	Output	μ -operation
0	0	$F = A \wedge B$	AND
0	1	$F = A \vee B$	OR
1	0	$F = A \oplus B$	XOR
1	1	$F = A'$	Complement

Arithmetic Logic and Shift Unit

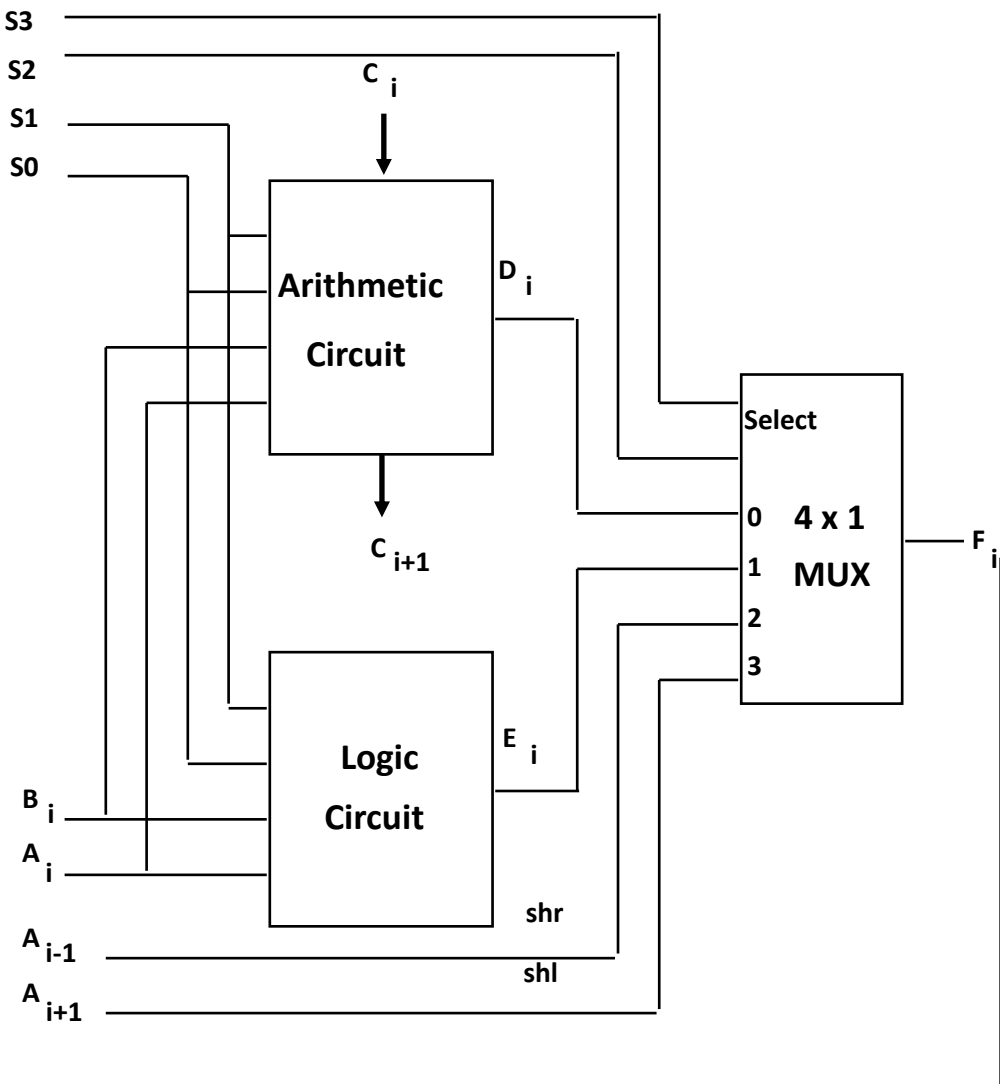

S3	S2	S1	S0	Cin	Operation
0	0	0	0	0	$F = A$
0	0	0	0	1	$F = A + 1$
0	0	0	1	0	$F = A + B$
0	0	0	1	1	$F = A + B + 1$
0	0	1	0	0	$F = A + B'$
0	0	1	0	1	$F = A + B' + 1$
0	0	1	1	0	$F = A - 1$
0	0	1	1	1	$F = A$
0	1	0	0	X	$F = A \wedge B$
0	1	0	1	X	$F = A \vee B$
0	1	1	0	X	$F = A \oplus B$
0	1	1	1	X	$F = A'$
1	0	X	X	X	$F = shr\ A$
1	1	X	X	X	$F = shl\ A$

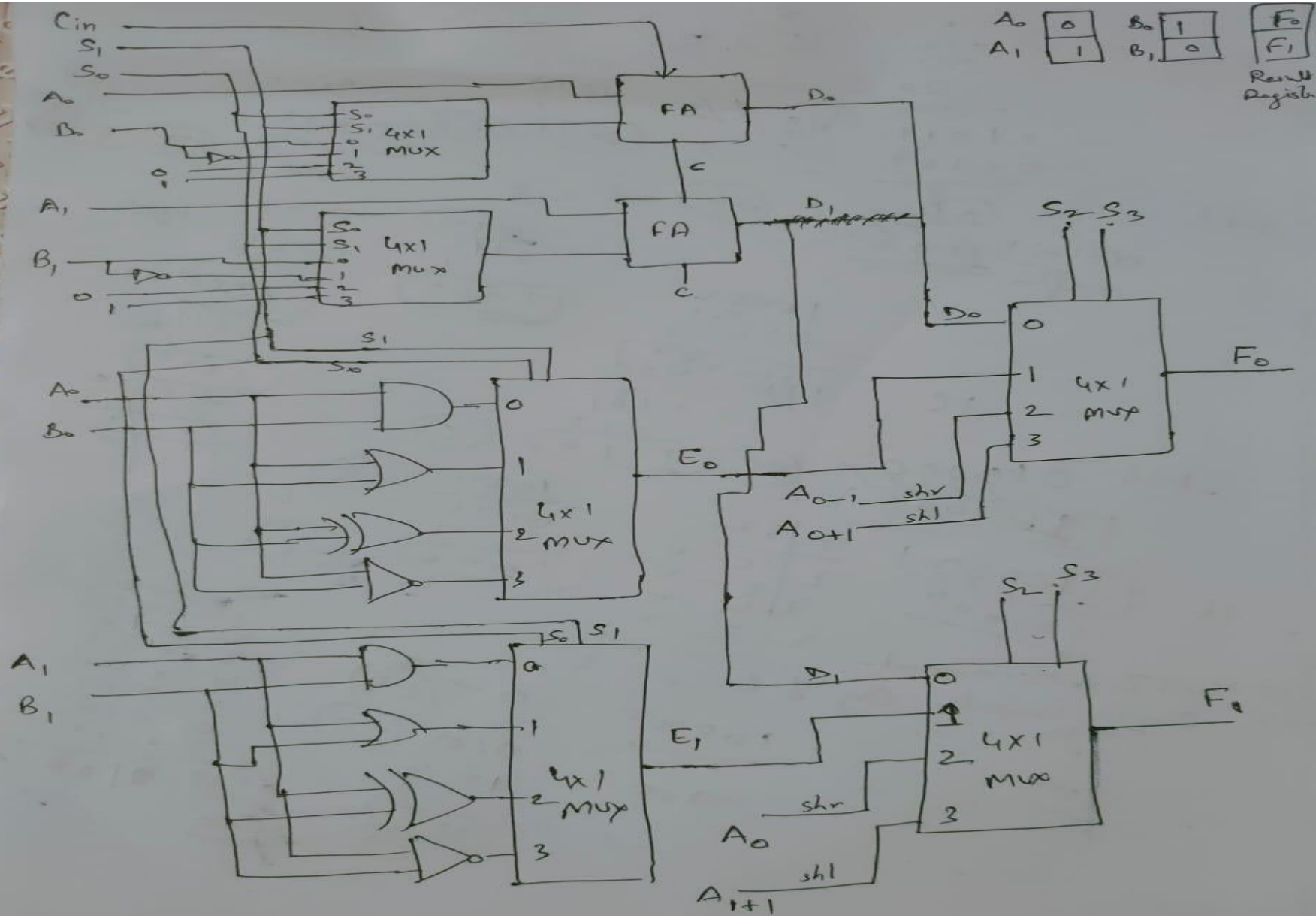

2-Bit Arithmetic Logic Shift Unit

- In context of arithmetic shift left operation, which of the following Gate is used to check the overflow?

A) OR

B) XOR

C) XNOR

D) NOR