

UNIT-II

Combinational Logic System

Lecture 14

Prepared By:

Dr.Krishan Arora

Assistant Professor and Head

KMAP

Karnaugh map is a tool for simplification of Boolean algebra

K-Map diagram is made up of squares

K-map is a graphical representation of SOP (Minterm)

K-Map extensively reduce the calculation and provides best minimized solution

K-map solve the expression with grouping of neighbor cells

Y \ X	0	1
0		
1		

2 variable

Y Z \ X	0	1
00		
01		
11		
10		

3 variable

Z \ XY	00	01	11	10
0				
1				

3 variable

Y Z \ WX	00	01	11	10
00				
01				
11				
10				

4 variable

Kmap Simplification Rule

- 1) Construct kmap and place 1's in the squares according to the truth table.
- 2) Groupings can contain only 1s
- 3) Groups can be formed only at right angles; diagonal groups are not allowed.
- 4) The number of 1's in a group must be a power of 2
- 5) The groups must **be made as large** as possible.
- 6) Groups can overlap and wrap around the sides of the Kmap.
- 7) Every group puts a term in the solution

Optimized Solution

Minimum number of group

Each group covers maximum possible squares

$$\text{Out} = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C$$

A \ BC				
	00	01	11	10
0	1	1		
1				

$$\text{Out} = \overline{A}\overline{B}$$

$$\text{Out} = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}BC + \overline{A}B\overline{C}$$

A \ BC				
	00	01	11	10
0	1	1	1	1
1				

$$\text{Out} = \overline{A}$$

$$\text{Output} = AB + BC + AC$$


A \ BC				
	00	01	11	10
0			1	
1		1	1	1

$$\text{Out} = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}BC + ABC + AB\overline{C}$$


A \ BC	BC			
	00	01	11	10
0	1	1	1	1
1			1	1

$$\text{Out} = \overline{A} + B$$
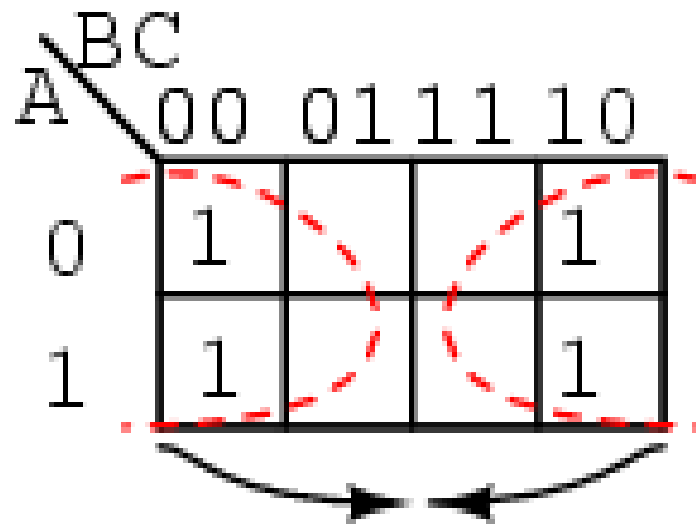
$$\text{Out} = \overline{A}\overline{B}\overline{C} + A\overline{B}\overline{C} + \overline{A}B\overline{C} + AB\overline{C}$$



$$\text{Out} = \overline{C}$$

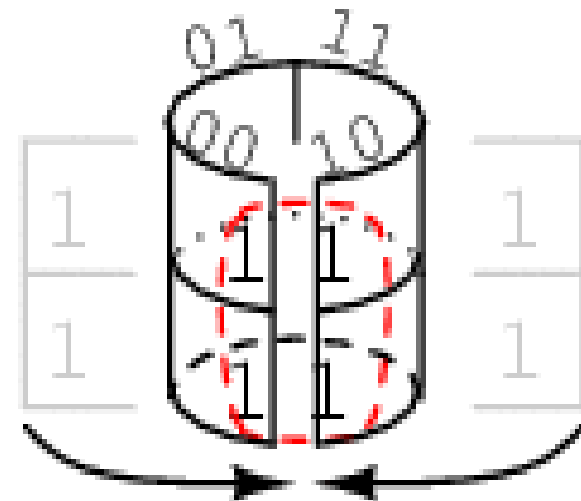

$$\text{Out} = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + A\overline{B}C$$

A \ BC	BC			
	00	01	11	10
0	1	1	1	1
1	1			1


$$\text{Out} = \overline{A} + \overline{C}$$

$$\text{Out} = \bar{A}\bar{B}CD + \bar{A}BCD + ABCD + A\bar{B}CD + AB\bar{C}\bar{D} + AB\bar{C}D + ABC\bar{D}$$

		CD			
		00	01	11	10
A \ B	00			1	
	01			1	
	11	1	1	1	1
	10			1	

$\text{Out} = AB + CD$
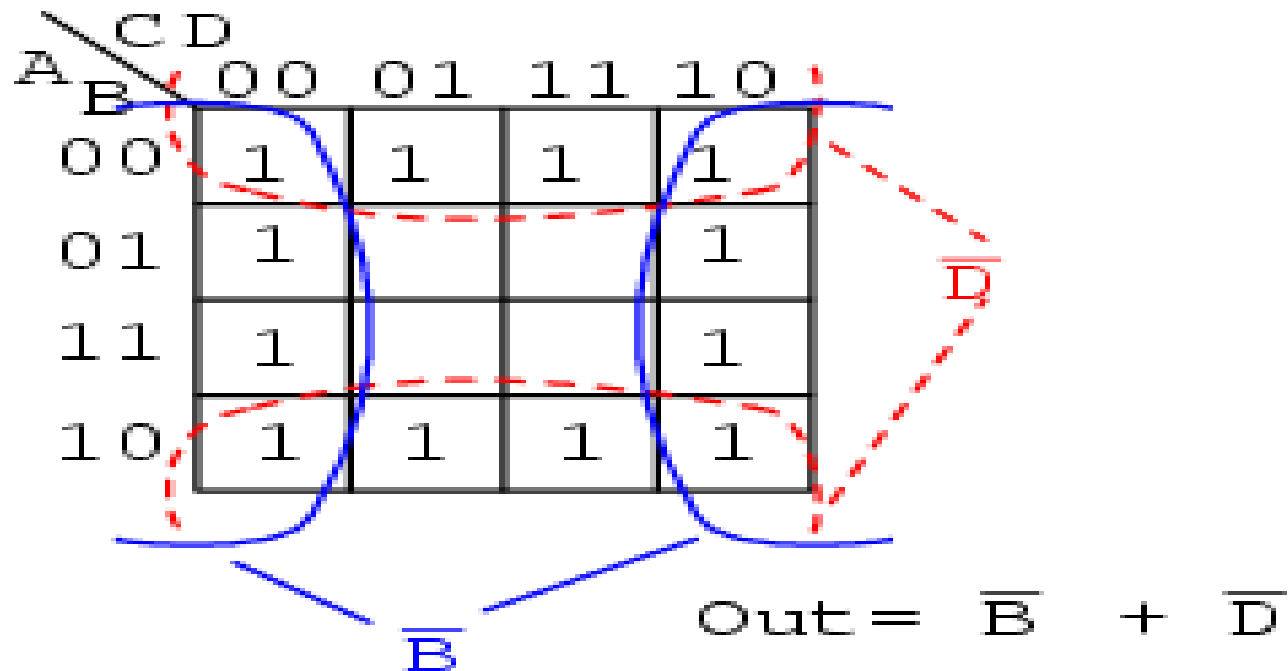
$$\text{Out} = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}CD + \overline{B}\overline{C}\overline{D} + B\overline{C}\overline{D} + A\overline{B}\overline{C}\overline{D} + A\overline{B}D + A\overline{B}C\overline{D}$$



$$\text{Out} = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D} + \overline{A}BC\overline{D} + A\overline{B}\overline{C}\overline{D} \\ + A\overline{B}C\overline{D} + ABC\overline{D} + A\overline{B}C\overline{D} + A\overline{B}CD$$

A \ B		CD			
		00	01	11	10
00	1			1	
01	1			1	
11	1	1		1	
10	1			1	

$$\text{Out} = \overline{C}\overline{D} + CD + AB\overline{C}$$

A \ B		CD			
		00	01	11	10
00	1			1	
01	1			1	
11	1	1	1		
10	1			1	

$$\text{Out} = \overline{C}\overline{D} + CD + ABD$$

Practice Question

WX \ YZ	YZ			
	00	01	11	10
00	1		1	
01	1		1	1
11	1			
10	1			

WX \ YZ	YZ			
	00	01	11	10
00	1		1	
01	1		1	1
11	1			
10	1			

Quick Quiz (Poll 1)

- There are _____ cells in a 4-variable K-map.
 - a) 12
 - b) 16
 - c) 18
 - d) 8

Quick Quiz (Poll 2)

- These logic gates are widely used in _____ design and therefore are available in IC form.
 - a) Sampling
 - b) Digital
 - c) Analog
 - d) Systems