

Unit 1: DC Circuits

TUTORIAL : Week 3

Prepared By: Irfan Ahmad Pindoo

Recap: POLL

Nodal Analysis is applicable to_____ network.


- A. Planar only
- B. Non Planar
- C. Both planar and non planar
- D. Only meshes

Delta to Star Conversion

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$


$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

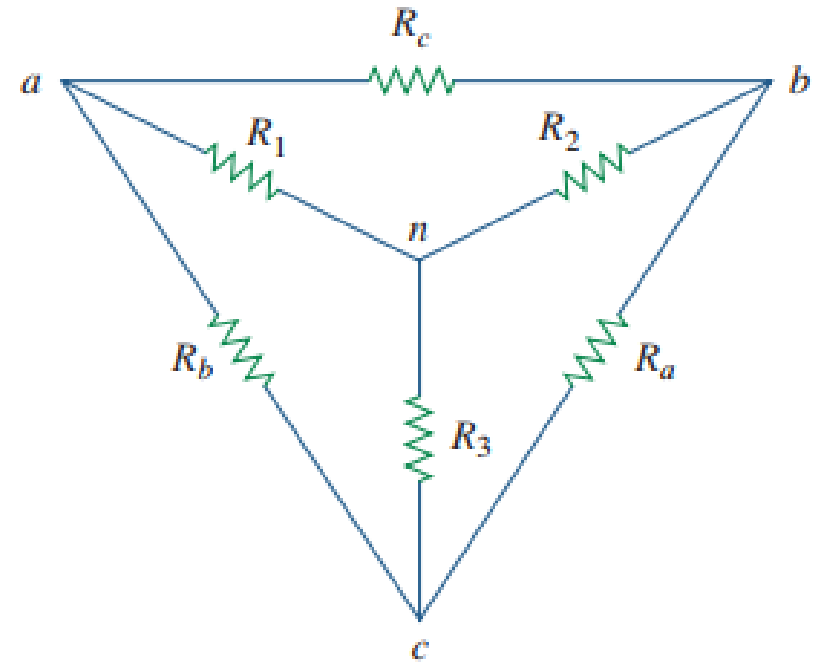

Problem 1


Q: Convert Δ network into a Y network?

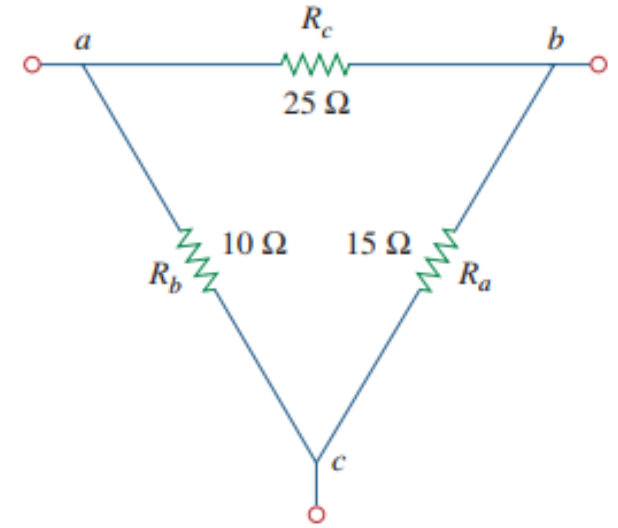

POLL

While converting Δ network into a Y, the equivalent values of the resistor would be?

- A. 12
- B. 4
- C. 36
- D. 40

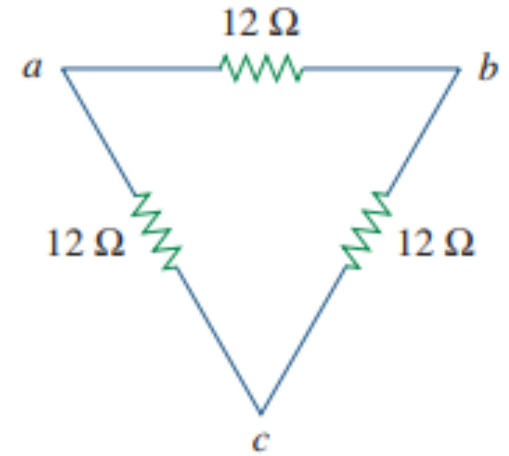


Star to Delta Conversion


$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$
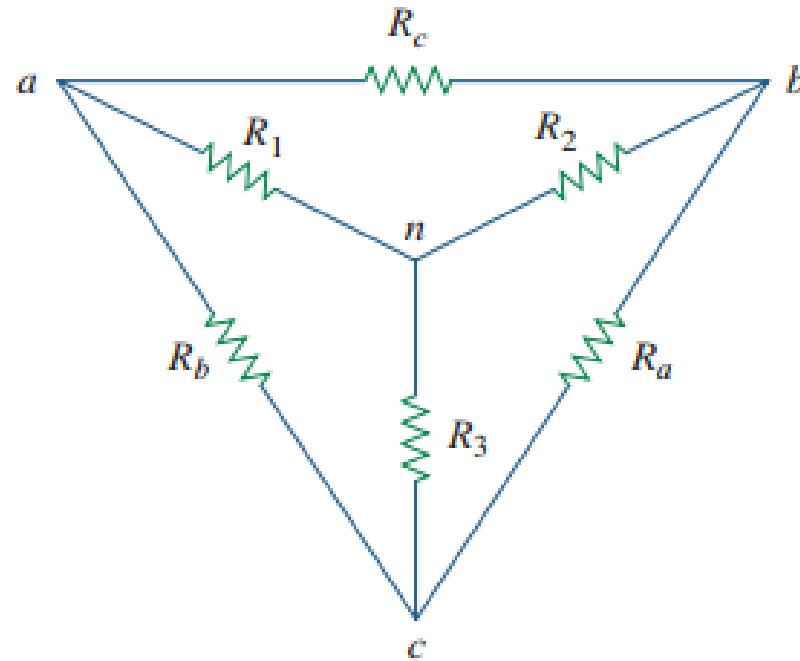
$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$




Example

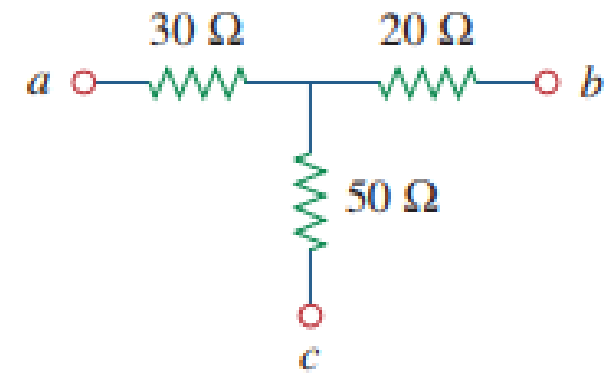


QUICK QUIZ (Poll)

Resistance R_{bc} for the Δ network of the corresponding Figure is:


- A. 140
- B. 70
- C. 35
- D. 100

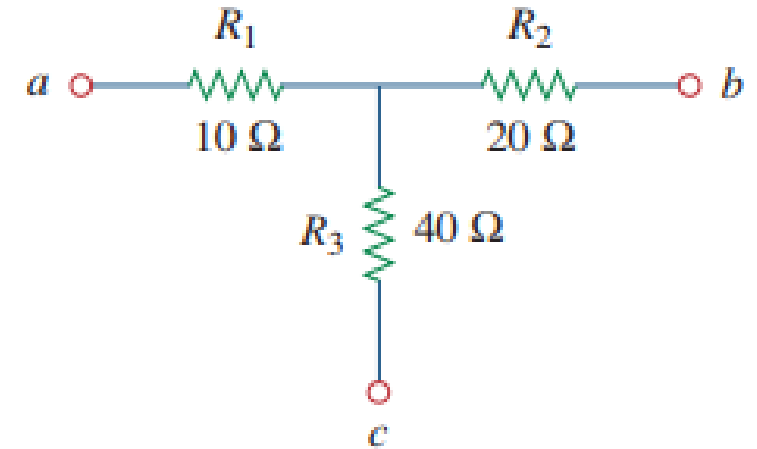

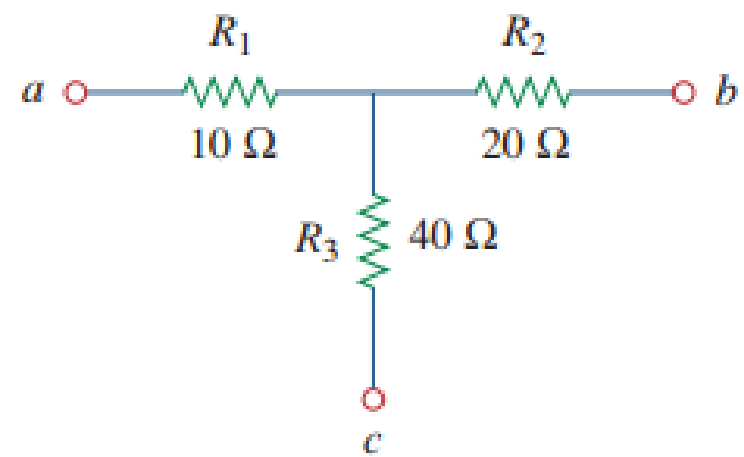


Problem 2

Find Mesh Currents?

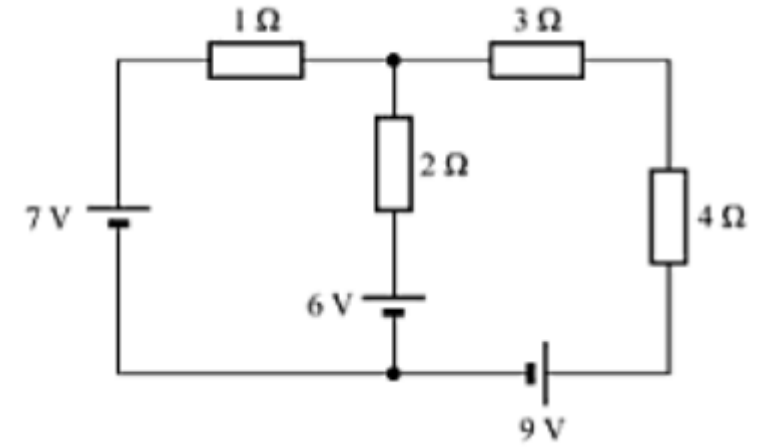


Problem 3

Find current through 5ohm using Nodal Analysis?

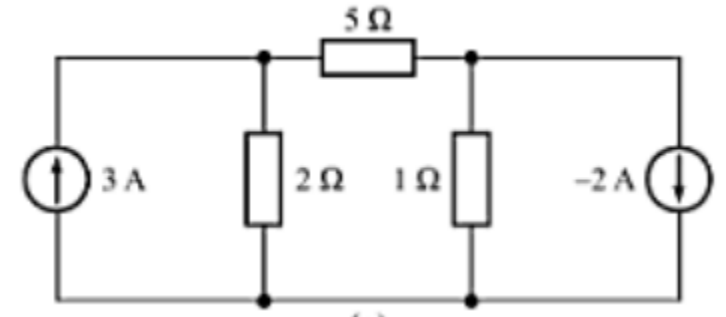

Problem 4


Find I using Superposition?

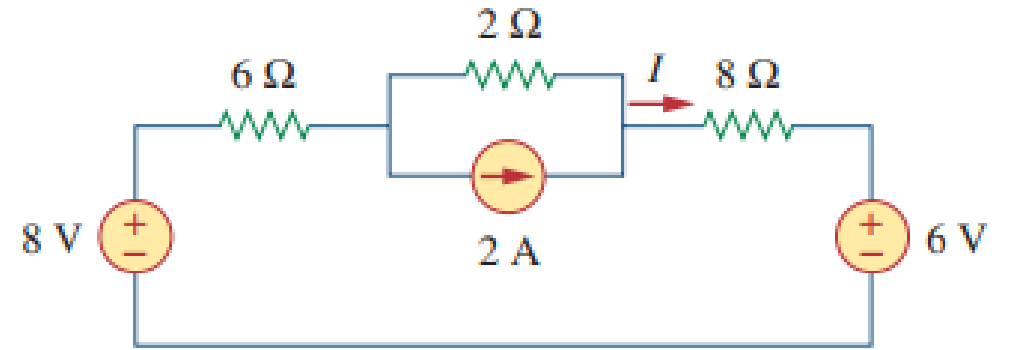

QUICK QUIZ (POLL)

Find node voltages?


- A. 6V
- B. 7V
- C. 8V
- D. 9V

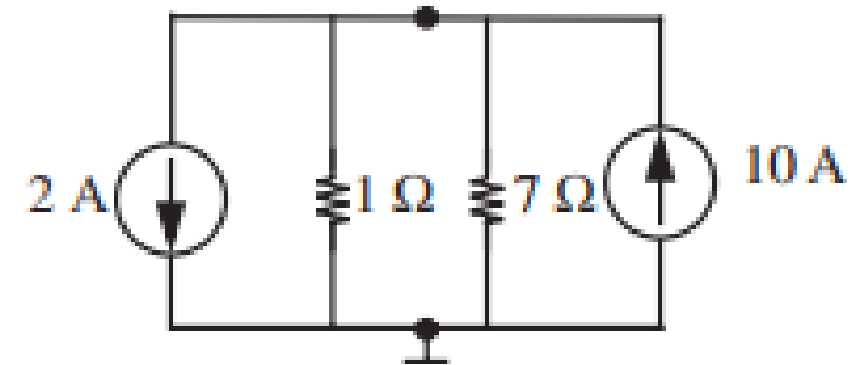

Dependent Sources:


Problem 5

Find V_x in the circuit using Nodal Analysis?

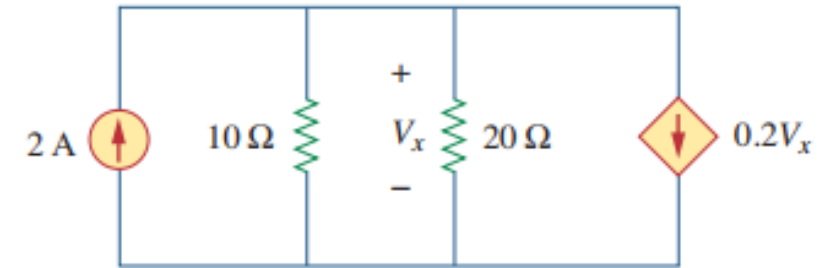


Problem 6

Use Mesh Analysis to find I_o ?

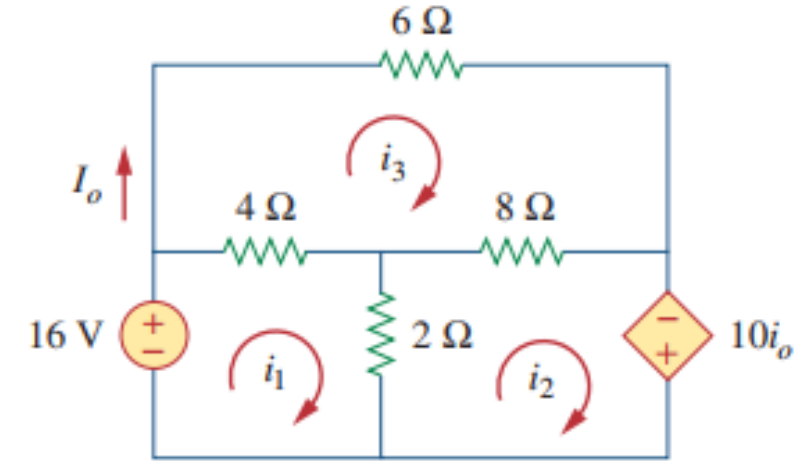


Problem 7

Find V_x using Superposition?

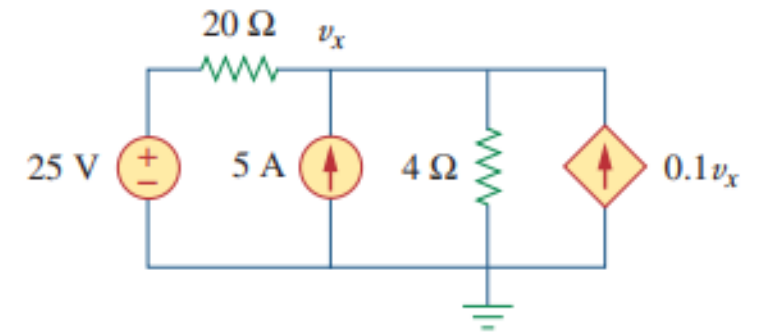


Source Transformation

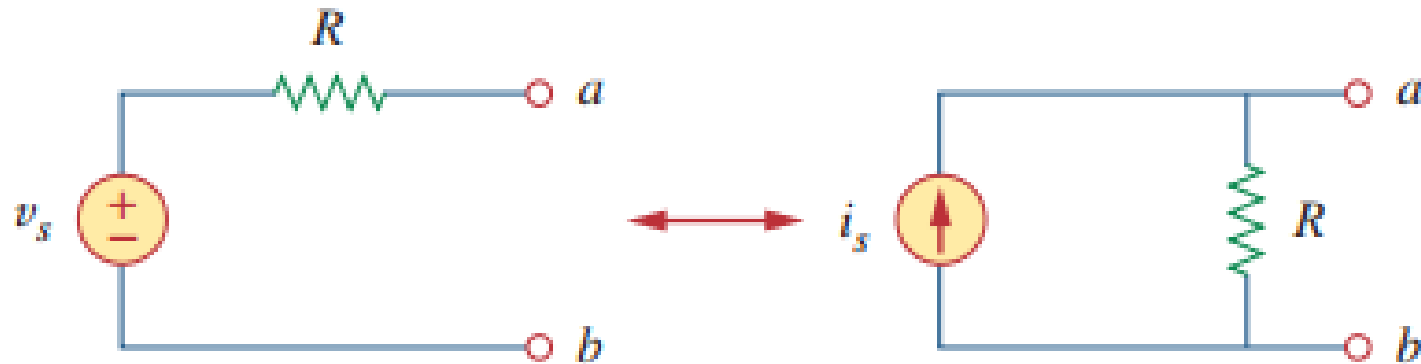- We have noticed that series-parallel combination and wye-delta transformation help simplify circuits.
- *Source transformation* is another tool for simplifying circuits. Basic to these tools is the concept of *equivalence*.




PRACTICE PROBLEM


Using Source Transformation, find V_o ?

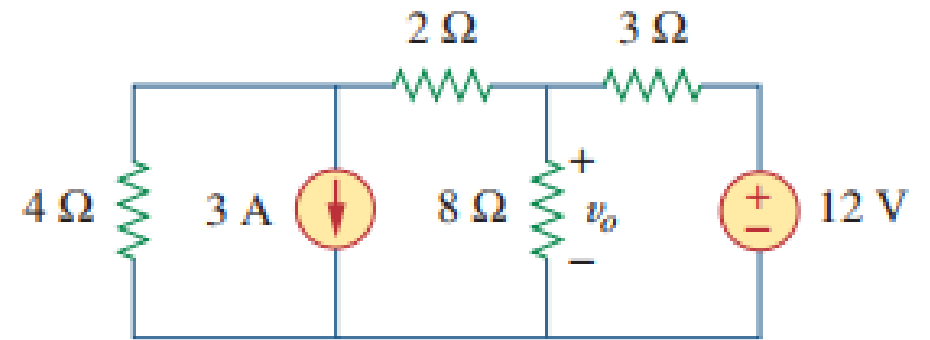


Problem 8

- Find R_{ab} and i in the given circuit:

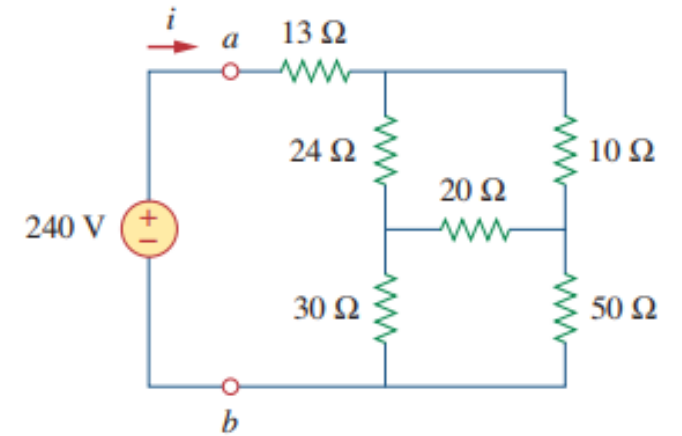

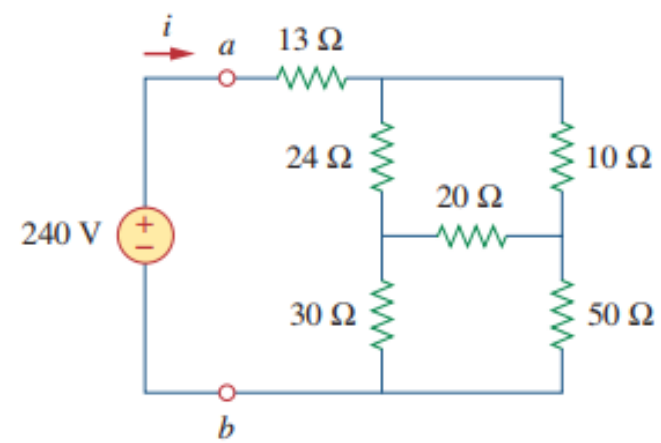

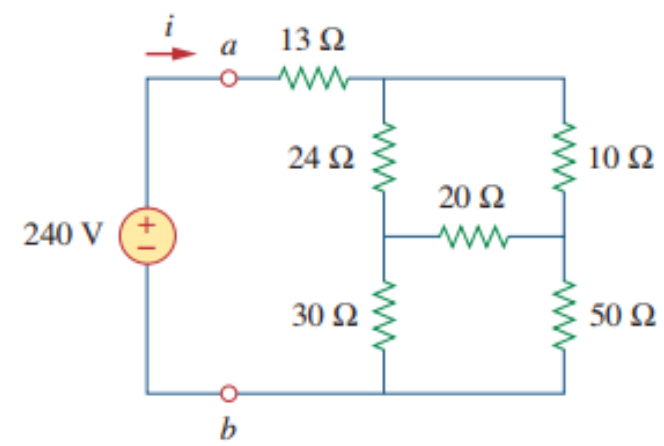

Problem 9

Find i_o in the circuit?

