

Unit IV

Introduction to Sequential Logic Circuits

by

Dr. Krishan Arora

Associate Professor and Head
Lovely Professional University

FLIP FLOP CONVERSIONS

- SR to D
- SR to JK
- SR to T
- JK to T
- JK to D
- JK to SR
- D to T
- D to SR
- T to D

PROCEDURE FOR CONVERSION

1. Draw the block diagram of the target flip flop from the given problem.
2. Write truth table for the target flip-flop.
3. Write excitation table for the available flipflop.
4. Draw k-map for target flip-flop.
5. Draw the block diagram.

SR to D Flip flop Conversion

Conversion Table

Input	Present state	Next state	Flip flop Inputs	
D	Q_n	Q_{n+1}	S	R
0	0	0	0	X
0	1	0	0	1
1	0	1	1	0
1	1	1	X	0

K-MAP SIMPLIFICATION

D \ Q_p	0	1
0	0 ⁰	0 ¹
1	1 ²	X ³

$$S = D$$

D \ Q_p	0	1
0	X ⁰	1 ¹
1	0 ²	0 ³

$$R = \overline{D}$$


D



CP



S

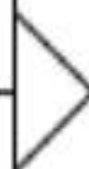

R

Qn

Qn'

Truth Table

CLK	S	R	Q	\bar{Q}
0	x	x	Memory state	
1	0	0	Memory state	
1	0	1	0	1
1	1	0	1	0
1	1	1	Invalid	

Characteristics Table

S	R	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	×
1	1	1	×

Excitation Table

Q_n	Q_{n+1}	S	R
0	0	0	x
0	1	1	0
1	0	0	1
1	1	x	0

SR(Available) to JK(Target) Flip-

Conversion Table Flop

Input		Present State	Next State	Flip-Flop Inputs	
J	K	Q n	Qn+1	S	R
0	0	0	0	0	X
0	0	1	1	X	0
0	1	0	0	0	X
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	1	X	0
1	1	0	1	1	0
1	1	1	0	0	1

SR to JK

- K-map Simplification


J	KQ _p			
	00	01	11	10
0	0 ⁰	X ¹	0 ³	0 ²
1	1 ⁴	X ⁵	0 ⁷	1 ⁶

$$S = \bar{J}Q_p$$

J	KQ _p			
	00	01	11	10
0	X ⁰	0 ¹	1 ³	X ²
1	0 ⁴	0 ⁵	1 ⁷	0 ⁶

$$R = KQ_p$$



Logic Diagram (SR to JK)

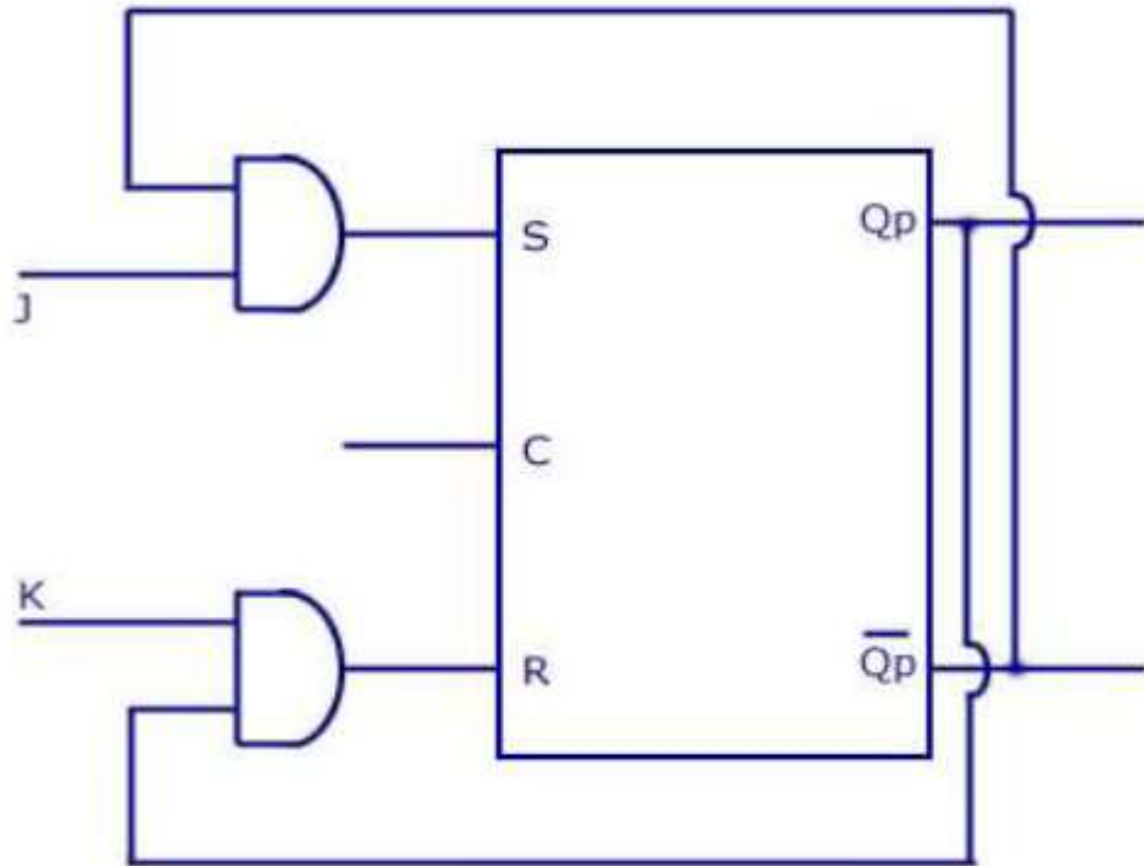


SR(Available) to T(Target) Conversion Table

Input	Present state	Next state	Flip flop Inputs	
T	Q_n	Q_{n+1}	S	R
0	0	0	0	X
0	1	1	X	0
1	0	1	1	0
1	1	0	0	1

K- MAP SIMPLIFICATION

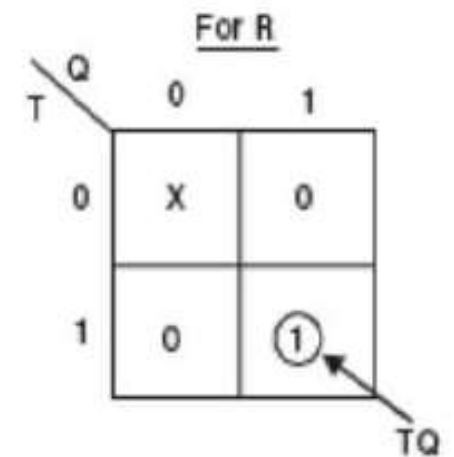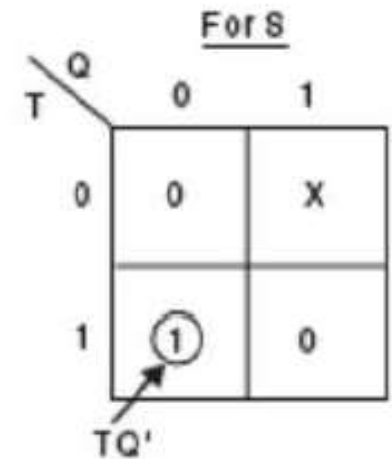

Logic Diagram (SR to T)

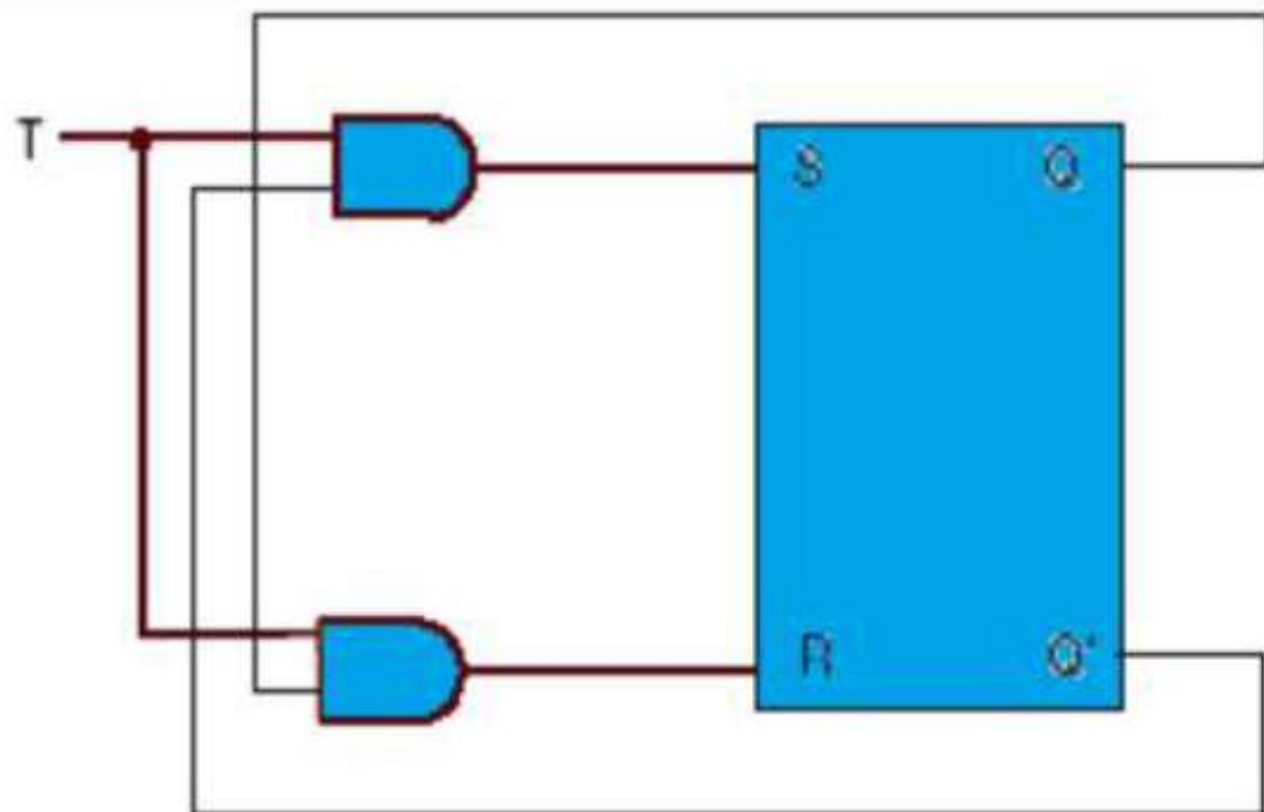

A T flip-flop using S-R flip-flop.

Quick Quiz

- Whose operations are more faster among the following?
 - a) Combinational circuits
 - b) Sequential circuits
 - c) Latches
 - d) Flip-flops

Quick Quiz

- In S-R flip-flop, if $Q = 0$ the output is said to be

- a) Set
- b) Reset
- c) Previous state
- d) Current state

Quick Quiz

- What does the triangle on the clock input of a J-K flip-flop mean?
 - a) Level enabled
 - b) Edge triggered
 - c) Both Level enabled & Edge triggered
 - d) Level triggered