

Tutorial 7

Example 1

- A transformer has a primary coil and a secondary coil with the number of loops are 500 and 5000. Input voltage is 220 V. What is the output voltage?

Solution

- Primary coil (N_p) = 500 loops
- Secondary coil (N_s) = 5000 loops
- Primary voltage (V_p) = 220 Volt
- Secondary voltage (V_s) = ?

- Solution :

- $V_s / N_s = V_p / N_p$
- $V_s / 5000 = 220 / 500$
- $V_s / 5000 = 0.44$
- $V_s = (0.44)(5000)$
- $V_s = 2200$ Volt

Example 2

- A transformer has primary coil with 1200 loops and secondary coil with 1000 loops. If the current in the primary coil is 4 Ampere, then what is the the current in the secondary coil.

Solution

- Solution :
- $I_S/I_P = N_P/N_S$
- The current in the secondary coil :
- $I_S/4 = 1200/1000$
- $I_S/4 = 1.2$
- $I_S = 1.2 (4)$
- $I_S = 4.8$ Ampere

Example 3

- The secondary voltage is 220 Volt and primary voltage is 110 volt, then a comparison of the secondary coil and primary coil is...

Solution

Given :


- Secondary voltage (V_s) = 220 Volt
- Primary voltage (V_p) = 110 Volt

Required N_s/N_p

- Solution :
- $V_s/V_p = N_s/N_p$
- $220/110 = N_s/N_p$
- $22/11 = N_s/N_p$
- $2/1 = N_s/N_p$
- $12/6 = N_s/N_p$

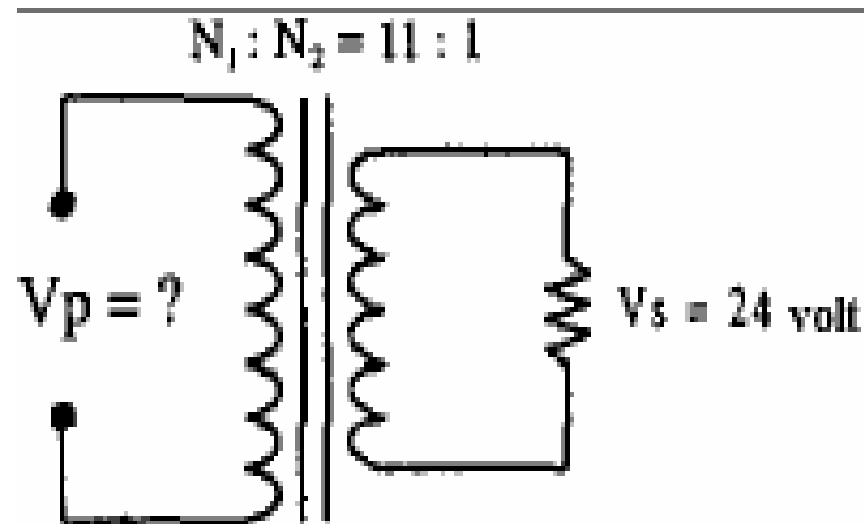Example 4

- Based on figure below, what is the primary voltage of the transformer.



Solution

Given :


- Secondary voltage (V_s) = 24 Volt
- Primary loops (N_p or N_1) = 11 N
- Secondary loops (N_s or N_2) = 1 N = N
- Primary voltage (V_p) = ?

Solution :

- $V_s / N_s = V_p / N_p$
- $24 / 1 = V_p / 11$
- $24 = V_p / 11$
- $V_p = (24)(11)$
- $V_p = 264$ Volt

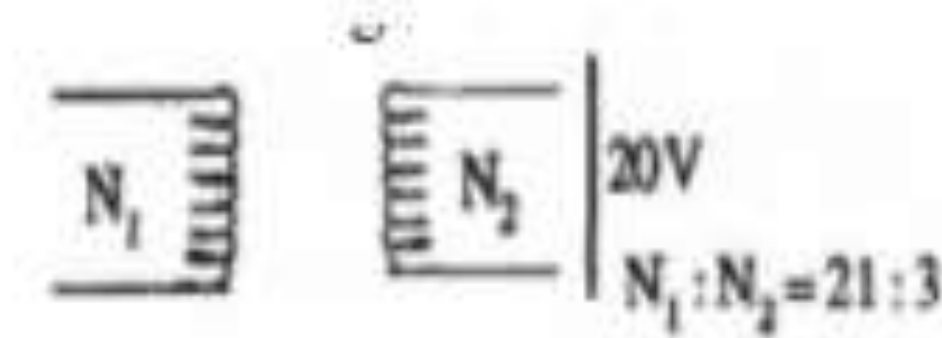Example 5

- Based on figure below, what is the input voltage of the transformer



Solution

Given :


- Primary coil (N_1) = 21 N
- Secondary coil (N_2) = 3 N
- Secondary voltage (V_2) = 20 Volt
- Primary voltage (V_1) = ?

Solution :

- $V_2 / N_2 = V_1 / N_1$
- $20 / 3 \text{ N} = V_1 / 21 \text{ N}$
- $20 / 1 = V_1 / 7$
- $20 = V_1 / 7$
- $V_1 = (7)(20)$
- $V_1 = 140 \text{ Volt}$

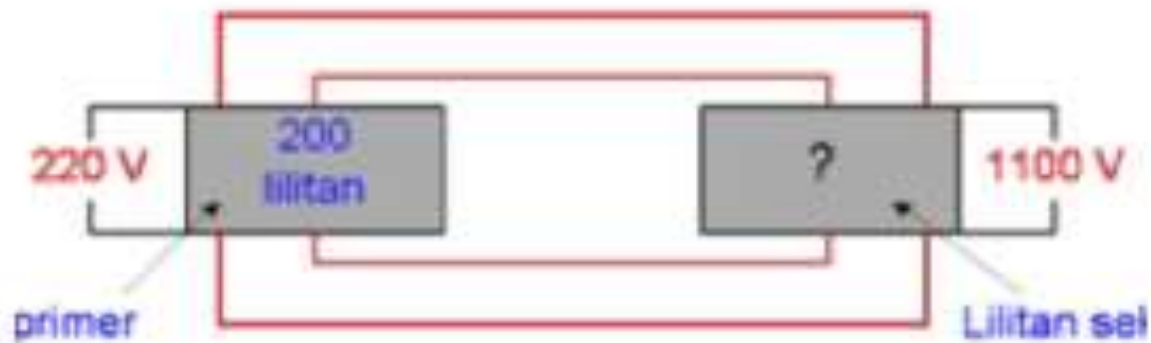Example 6

- According to figure below, what is the amount of the secondary loops of the transformer.




Solution

- $V_s / N_s = V_p / N_p$
- $1100 \text{ Volt} / N_s = 220 \text{ Volt} / 200 \text{ loops}$
- $1100 / N_s = 220 / 200$
- $1100 / N_s = 1.1$
- $N_s = 1100 / 1.1$
- $N_s = 1000 \text{ loops}$

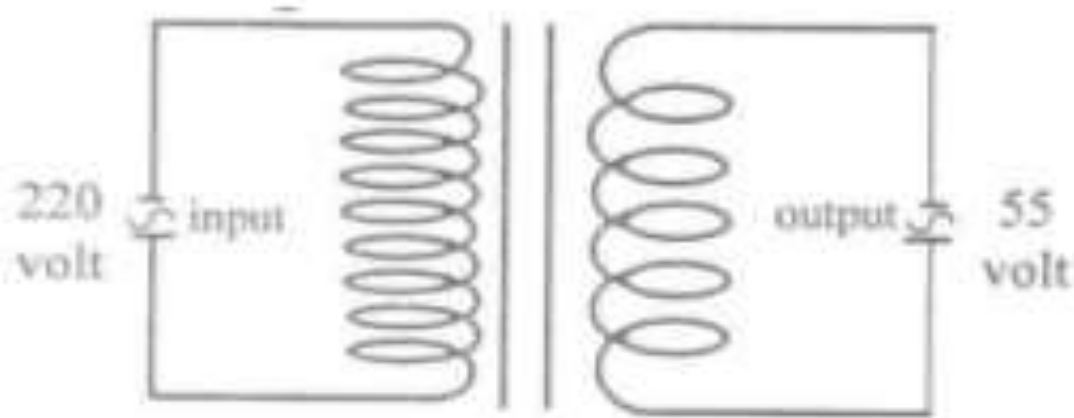Example 7


- If the primary coil has 800 loops, then determine the secondary coil.



Solution

- $V_s / N_s = V_p / N_p$
- $55 / N_s = 220 / 800$
- $55 / N_s = 22 / 80$
- $N_s = (80)(55) / 22$
- $N_s = 4400 / 22$
- $N_s = 200$ loops

Quick Quiz 1

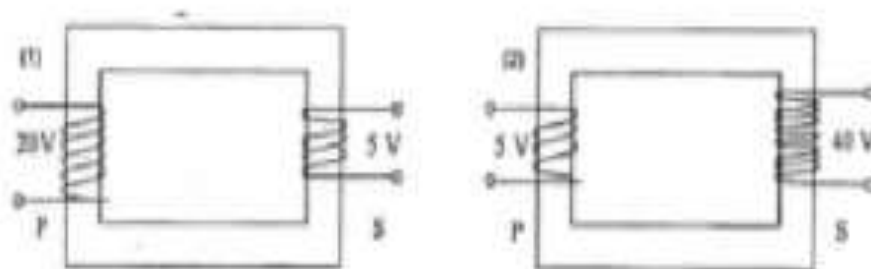

Based on the above figure, which of the following statements about the figure above is correct.

- A. Figure 1 is a step-up transformer and figure 2 is a step-down transformer
- B. Figure 1 is a step-down transformer and figure 2 is a step-up transformer
- C. Figure 1 and 2 are a step-down transformer
- D. Figure 1 and 2 are a step-up transformer

Quick Quiz 2

Quantities	Transformers	
	P	Q
Primary voltage	110 V	220 V
Secondary voltage	200 V	110 V
Primary current	4 A	1 A
Secondary current	2 A	2 A
Power	400 W	220 W

The correct statement about transformer P and Q is...

- A. P is a step-down transformer because of $I_s < I_p$
- B. P is a step-up transformer because of $V_p < V_s$
- C. Q is a step-up transformer because of $V_p > V_s$
- D. Q is a step-up transformer because $I_s > I_p$

Quick Quiz 3

- Turns ratio of the transformer is directly proportional to _____
 - a) Resistance ratio
 - b) Currents ratio
 - c) Voltage ratio
 - d) Not proportional to any terms

Quick Quiz 4

- Which of the following statement is correct regarding turns ratio?
 - a) Current ratio and turns ratio are inverse of each other
 - b) Current ratio is exactly same to the voltage ratio
 - c) Currents ratio is exactly same to the turns ratio
 - d) Voltage ratio and turns ratio are inverse of each other