

## 2-2 Decoder/Encoder


### ■ NAND Gate Decoder

- ◆ Constructed with NAND instead of AND gates
- ◆ Logic Diagram/Truth Table : *Fig. 2-2*

*Fig. 2-2 2-to-4 Decoder with NAND gates*

Enable Input		Output			
E	A1 A0	D0	D1	D2	D3
0	0 0	0	1	1	1
0	0 1	1	0	1	1
0	1 0	1	1	0	1
0	1 1	1	1	1	0
1	x x	1	1	1	1

(a) Truth Table

 

(b) Logic Diagram

### ■ Decoder Expansion

- ◆ Constructed decoder : *Fig. 2-3*
- ◆ 3 X 8 Decoder constructed with two 2 X 4 Decoder

### ■ Encoder


- ◆ Inverse Operation of a decoder
- ◆  $2^n$  input, n output
- ◆ Truth Table : *Tab. 2-2*

#### ● 3 OR Gates Implementation

- »  $A0 = D1 + D3 + D5 + D7$
- »  $A1 = D2 + D3 + D6 + D7$
- »  $A2 = D4 + D5 + D6 + D7$

*Tab. 2-2 Truth Table for Encoder*

Inputs								Outputs		
D7	D6	D5	D4	D3	D2	D1	D0	A2	A1	A0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

 

*Fig. 2-3 A 3-to-8 Decoder constructed with two 2-to-4 Decoder*

## 2-2 Decoder/Encoder


### Octal to Binary Encoder

D <sub>7</sub>	D <sub>6</sub>	D <sub>5</sub>	D <sub>4</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

 


## 2-3 Multiplexers

### ■ Multiplexer(Mux)

- ◆ A combinational circuit that receives binary information from one of  $2^n$  input data lines and directs it to a single output line
- ◆ A  $2^n$ -to 1 multiplexer has  $2^n$  input data lines and  $n$  input selection lines(Data Selector)
- ◆ 4-to-1 multiplexer Diagram : *Fig. 2-4*
- ◆ 4-to-1 multiplexer Function Table : *Tab. 2-3*

*Tab. 2-3 Function Table for  
4-to-1 line Multiplexer*

Select		Output
S1	S0	Y
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

 

*Fig. 2-4 4-to-1 Line Multiplexer*


### ■ Quadruple 2-to-1 Multiplexer

- ◆ Quadruple 2-to-1 Multiplexer : *Fig. 2-5*

*Fig. 2-5 Quadruple 2-to-1  
line Multiplexer*


Select		Output
E	S	Y
0	0	All 0's
1	0	A
1	1	B

*(a) Function Table*

 


*(b) Block Diagram*

## 2-3 Multiplexers

 

*Fig A. Combinational logic diagram with four  $2 \times 1$  multiplexer*

 

$E \rightarrow$  Data input  
 $S_0, S_1 \rightarrow$  Select Data

*Fig B. Demultiplexer*

A **Demultiplexer**, sometimes abbreviated **DMUX** is a circuit that has one input and more than one output. It is used when a circuit wishes to send a signal to one of many devices

- Suppose a MUX is having 16 input lines. How many selection input lines are required?

A) 2

B) 3

C) 4

D) 5



## 2-4 Registers

### ■ Register


- ◆ A group of flip-flops with each flip-flop capable of storing one bit of information
- ◆ An n-bit register has a group of n flip-flops and is capable of storing any binary information of n bits
- ◆ The simplest register consists only of flip-flops, with no external gate :

*Fig. 2-6*

- ◆ A clock input C will load all four inputs in parallel
  - The clock must be *inhibited* if the content of the register must be left unchanged

### ■ Register with Parallel Load


- ◆ A 4-bit register with a load control input : *Fig. 2-7*
- ◆ The clock inputs receive clock pulses at all times
- ◆ The buffer gate in the clock input will increase “fan-out”
- ◆ Load Input
  - 1 : Four input transfer
  - 0 : Input inhibited, Feedback from output to input(*no change*)

 

*Fig. 2-6 4-bit register*

## 2-4 Registers


- When the load input is 1, the data in the four inputs are transferred into the register with the next positive transition of a clock pulse
- When the load input is 0, the data inputs are inhibited and the D-output of flip flop are connected to their inputs.

 

*Fig. 2-7 4-bit register with parallel load*

## 2-5 Shift Registers

- Shift Register
  - ◆ A register capable of shifting its binary information in one or both directions
  - ◆ The logical configuration of a shift register consists of a chain of flip-flops in cascade
  - ◆ The simplest possible shift register uses only flip-flops : *Fig. 2-8*
  - ◆ The **serial input** determines what goes into the leftmost position during the shift
  - ◆ The **serial output** is taken from the output of the rightmost flip-flop

 

*Fig. 2-8 4-bit shift register*



- Data can be transferred to a register only when its load input is 1.

A) True

B) False

## 2-5 Shift Registers

- Bidirectional Shift Register with Parallel Load
  - ◆ A register capable of shifting in *one direction only* is called a **unidirectional shift register**
  - ◆ A register that can shift in *both directions* is called a **bidirectional shift register**
  - ◆ The most general shift register has all the capabilities listed below:
    - An input clock pulse to synchronize all operations
    - A shift-right /left (serial output/input)
    - A parallel load, n parallel output lines
    - The register unchanged even though clock pulses are applied continuously
  - ◆ 4-bit bidirectional shift register with parallel load :


*Fig. 2-9*

- 4 X 1 Mux = 4 , D F/F = 4

*Tab. 2-4 Function Table for Register of Fig. 2-9*

Mode		Operation
S1	S0	
0	0	No change
0	1	Shift right(down)
1	0	shift left(up)
1	1	Parallel load

## 2-5 Shift Registers

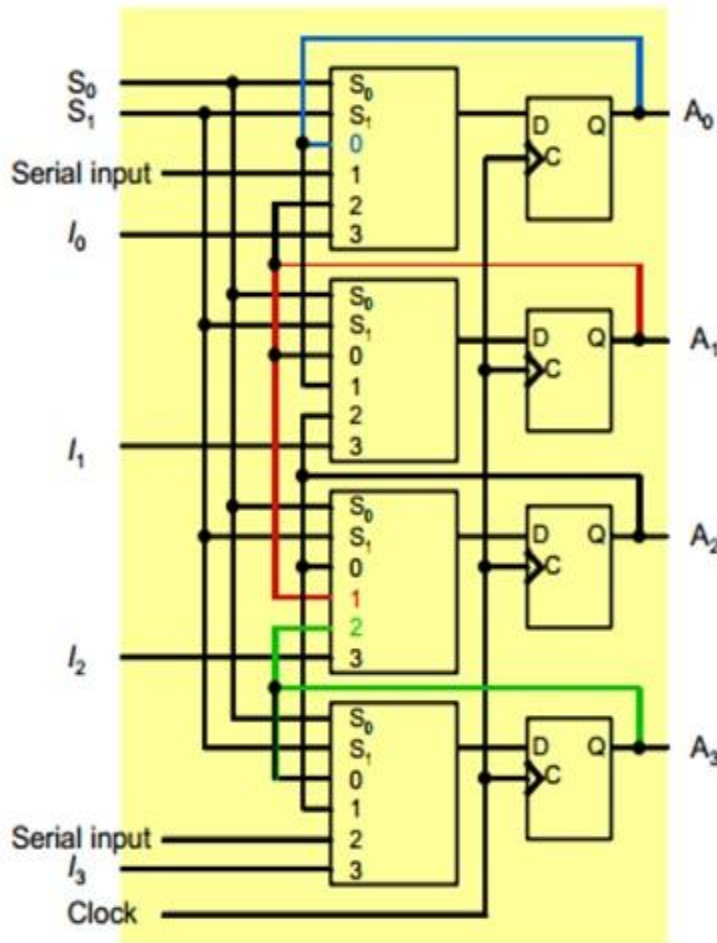

$S_1S_0 = 00$  :  $A_i \rightarrow A_i$  (No change)

$S_1S_0 = 01$  :  $A_{i-1} \rightarrow A_i$  (Shift)

$S_1S_0 = 10$  :  $A_{i+1} \rightarrow A_i$  (Shift)

$S_1S_0 = 11$  : Parallel load

### ■ Shift Register

Interface digital systems situated remotely from each other



Fig. 2-9 Bidirectional shift register

- Which of the following is not a type of a Register?
  - A) SISO
  - B) SIPO
  - C) PIPO
  - D) None of the above