

Unit 2 Problems

Tutorial 5

Example 1

An ac voltage is mathematically expressed as $v = 141.42\sin(157.08t + \pi/2)$ volts. Find its (a) effective value (b) frequency (c) periodic time.

An ac voltage is mathematically expressed as

$$v = 141.42 \sin(157.08t + \pi/2) \text{ Volts}$$

$$v = V_m \sin(\omega t + \phi)$$

$$\text{Effective value} = \frac{V_m}{\sqrt{2}} = \frac{141.42}{\sqrt{2}} = 100\text{V}$$

$$\omega = 157.08$$

$$2\pi f = 157.08$$

$$f = \frac{157.08}{2\pi} = \underline{25 \text{ Hz}}$$

$$T = \frac{1}{f} = \frac{1}{25} = \underline{0.04 \text{ Sec}}$$

Example 2 Polar Notation Problem

- An AC current denoted by a phasor in complex plane as $I = 4 + j3$ Amp. Is flowing through a resistor of 10 ohm . Determine the power consumed by the resistor.

$$r = \sqrt{a^2 + b^2} \quad \text{and} \quad \theta = \tan^{-1} \frac{b}{a}$$

Solution

Solution Let us first express the current \mathbf{I} in the polar form,

$$\mathbf{I} = I_r + jI_i = 4 + j3 = \sqrt{4^2 + 3^2} \angle \tan^{-1}(3/4) = 5 \angle 36.87^\circ \text{ A}$$

Thus, we find that the magnitude (the rms value) of the given current is 5 A. Therefore, the power consumed is

$$P = I^2 R = 5^2 \times 10 = \mathbf{250 \text{ W}}$$

Problem on Rectangular and Polar calculations

Two phasors A and B are given as $A = 3 + j1$, and $B = 4 + j3$. Calculate the values of (a) $A + B$; (b) $A - B$; (c) AB ; (d) A/B . Express the results in both polar and rectangular coordinates.

$$[\text{Ans. (a) } 7 + j4 = 8.06 \angle 29.7^\circ;$$

$$(b) -1 - j2 = 2.24 \angle -116.57^\circ;$$

$$(c) 15.8 \angle 55.3^\circ = 8.99 + j12.99;$$

$$(d) 0.632 \angle -18.44^\circ = 0.6 - j0.02]$$

Addition subtraction and Multiplication

$$A = 3 + j1 \quad B = 4 + j3$$

$$a) \quad A+B = 3+j1 + 4+j3 = 7+j4 = 8.06 \angle 29.7^\circ$$

$$b) \quad A-B = 3+j1 - 4-j3 = -1-j2 = 2.24 \angle -110.7^\circ$$

$$c) \quad AB = (3+j1)(4+j3) = 15.8 \angle 55.3^\circ = 8.99 + j12.99$$

$$d) \quad \frac{A}{B} = \frac{3+j1}{4+j3} = 0.632 \angle -18.44^\circ = 0.6 - j0.02$$

Addition subtraction and Multiplication

Addition, Subtraction and Multiplication For these operations, just use ordinary algebra plus two more rules: (1) keep real and imaginary parts separate, and (2) treat j^2 as -1 . For example, whenever we add complex numbers, we add the real parts and the imaginary parts separately:

$$\mathbf{z}_1 + \mathbf{z}_2 = (3 + j4) + (-7 - j3) = (3 - 7) + j(4 - 3) = -4 + j1$$

and similarly for subtraction. Thus, complex numbers are added and subtracted like vectors in a plane. This is one of the few properties common between complex numbers and vectors.

Similarly, multiplication of \mathbf{z}_1 and \mathbf{z}_2 is

$$\begin{aligned}\mathbf{z}_1 \mathbf{z}_2 &= (3 + j4)(-7 - j3) = 3(-7) + j4(-j3) + 3(-j3) + j4(-7) \\ &= -21 - j^2 12 - j9 - j28 = -21 + 12 - j9 - j28 = (-21 + 12) - j(9 + 28) \\ &= -9 - j37\end{aligned}$$

Division

Division and Conjugation Division requires a trick to get the results in standard form :

$$\begin{aligned}\frac{z_1}{z_2} &= \frac{3+j4}{-7-j3} = \frac{3+j4}{-7-j3} \times \frac{-7+j3}{-7+j3} \\ &= \frac{(3)(-7) + (j4)(j3) + (3)(j3) + (j4)(-7)}{(-7)^2 - (j3)^2} = \frac{-21 - 12 + j9 - j28}{49 + 9} \\ &= \frac{-33 - j19}{58} = -\frac{33}{58} - j\frac{19}{58}\end{aligned}$$

Problem on Representation of sin wave equations

Obtain the sum of the three voltages,

$$v_1 = 147.3 \cos(\omega t + 98.1^\circ) \text{ V}, \quad v_2 = 294.6 \cos(\omega t - 45^\circ) \text{ V} \quad \text{and} \quad v_3 = 88.4 \sin(\omega t + 135^\circ) \text{ V}$$

Solution We plot the above phasors in complex plane, in terms of their peak values. First, we write the voltages in terms of sine functions. Since, $\sin(90^\circ + \theta) = \cos \theta$, we can write

$$v_1 = 147.3 \sin(90^\circ + \omega t + 98.1^\circ) \text{ V} = 147.3 \sin(\omega t + 188.1^\circ) \text{ V}$$

$$v_2 = 294.6 \sin(90^\circ + \omega t - 45^\circ) \text{ V} = 294.6 \sin(\omega t + 45^\circ) \text{ V}$$

and

$$v_3 = 88.4 \sin(\omega t + 135^\circ) \text{ V}$$

Problem on XL and XC calculation

(a) What reactance will be offered (i) by an inductor of 0.2 H, (ii) by a capacitance of 10 μF , to an ac voltage source of 10V, 100 Hz? (b) What, if the frequency of the source is changed to 140 Hz?

Solution

$$(a) \quad (i) \quad X_L = 2\pi fL = 2\pi \times 100 \times 0.2 = \mathbf{125.66 \, \Omega}$$

$$(ii) \quad X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 100 \times 10 \times 10^{-6}} = \mathbf{159.15 \, \Omega}$$

$$(b) \quad (i) \quad X_L = 2\pi fL = 2\pi \times 140 \times 0.2 = \mathbf{175.9 \, \Omega}$$

$$(ii) \quad X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 140 \times 10 \times 10^{-6}} = \mathbf{113.7 \, \Omega}$$

Problem on Resonance Frequency


A coil having resistance 5Ω inductance of 32mH , respectively is connected in series with a 796-pF capacitor. Determine resonance frequency of the circuit

$$\begin{aligned} f_r &= \frac{1}{2\pi\sqrt{LC}} \\ &= \frac{1}{2\pi\sqrt{32 \times 10^{-3} \times 796 \times 10^{-12}}} \\ &= \underline{\underline{31.53\text{ kHz}}} \end{aligned}$$


Problem on Series RL circuit

For the series RL circuit shown in Fig. 10.2a,

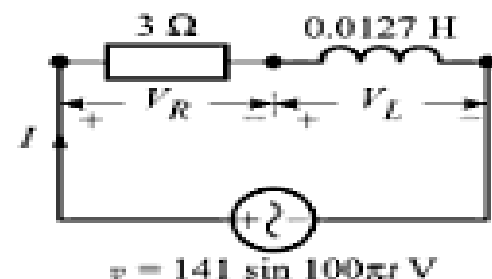
- (a) Calculate the rms value of the steady state current and the relative phase angle.
- (b) Write the expression for the instantaneous current.
- (c) Find the average power dissipated in the circuit.
- (d) Determine the power factor.
- (e) Draw the phasor diagram.



(a) The circuit.

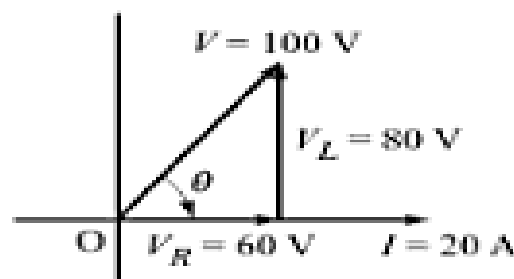

(b) Phasor diagram.

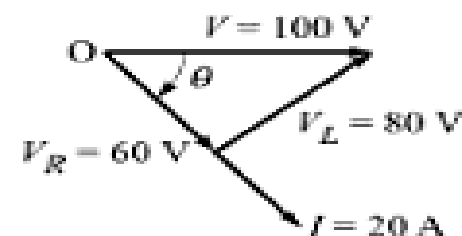

(c) Phasor diagram redrawn.

Fig. 10.2 A series *RL* circuit.

$$\mathbf{V} = V \angle 0^\circ = \frac{V_m}{\sqrt{2}} \angle 0^\circ = \frac{141}{\sqrt{2}} \angle 0^\circ = 100 \angle 0^\circ = 100 + j0 \text{ volts}$$

The impedance, $\mathbf{Z} = R + j\omega L = 3 + j100\pi \times 0.0127 = 3 + j4 = 5 \angle 53.1^\circ$ ohms

$$\therefore \text{Current, } \mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{100 \angle 0^\circ}{5 \angle 53.1^\circ} = 20 \angle -53.1^\circ \text{ A}$$

Thus, the rms value of the steady state current is 20 A, and the phase angle is 53.1° lagging.

(b) The expression for the instantaneous current can be written as

$$i = 20\sqrt{2} \sin(100\pi t - 53.1^\circ) = 28.28 \sin(100\pi t - 53.1^\circ) \text{ A}$$

(c) Average power, $P = VI \cos \theta = 100 \times 20 \times \cos 53.1^\circ = 1200 \text{ W}$

$$\text{Or, } P = I^2 R = (20)^2 3 = 1200 \text{ W}$$

(d) $pf = \cos \theta = \cos 53.1^\circ = 0.6$ lagging. Alternatively,

$$pf = \frac{\text{Average power}}{\text{Apparent power}} = \frac{P}{VI} = \frac{1200}{100 \times 20} = 0.6 \text{ lagging}$$

(e) Taking the current as reference, the phasor diagram is drawn in Fig. 10.2b, where

$$I = 20 \text{ A}; \quad V_R = IR = 20 \times 3 = 60 \text{ V}; \quad V_L = IX_L = 20 \times 4 = 80 \text{ V} \quad \text{and} \quad V = 100 \text{ V}$$

The same phasor diagram is redrawn in Fig. 10.2c, by rotating it clockwise by an angle 53.1° , so that the applied voltage becomes the reference phasor.

Problem on Power and RC circuit

A current of 0.9 A flows through a series combination of a resistor of $120\ \Omega$ and a capacitor of reactance $250\ \Omega$. Find the impedance, power factor, supply voltage, voltage across resistor, voltage across capacitor, apparent power, active power and reactive power.

Solution Taking current as the reference phasor, $\mathbf{I} = 0.9\angle 0^\circ\text{ A}$.

Impedance,	$\mathbf{Z} = 120 - j250 = 277.3\angle -64.4^\circ\ \Omega$
Power factor,	$pf = \cos \theta = \cos(-64.4^\circ) = 0.432\text{ leading}$
Supply voltage,	$\mathbf{V} = \mathbf{IZ} = (0.9\angle 0^\circ)(277.3\angle -64.4^\circ) = 249.6\angle -64.4^\circ\text{ V}$
Voltage across resistor,	$V_R = IR = (0.9\angle 0^\circ) \times 120 = 108\angle 0^\circ\text{ V}$
Voltage across capacitor,	$V_C = IX_C = (0.9\angle 0^\circ)(250\angle -90^\circ) = 225\angle -90^\circ\text{ V}$
Apparent power,	$P_{app} = VI = 249.6 \times 0.9 = 224.6\text{ VA}$
Actual power,	$P_a = VI \cos \theta = 249.6 \times 0.9 \times \cos 64.4^\circ = 97.06\text{ W}$
Reactive power,	$P_r = VI \sin \theta = 249.6 \times 0.9 \times \sin 64.4^\circ = 202.58\text{ VAR}$