

# Programmable Logic Array(PLA)

- It has programmable AND array and programmable OR array.
- Because **both arrays are programmable**, it is **flexible**.
- The PLA is similar in concept to the PROM, except that the PLA does not provide full decoding of the variables and does not generate all the minterms .



(a) Programmable read-only memory (PROM)




(b) Programmable array logic (PAL)



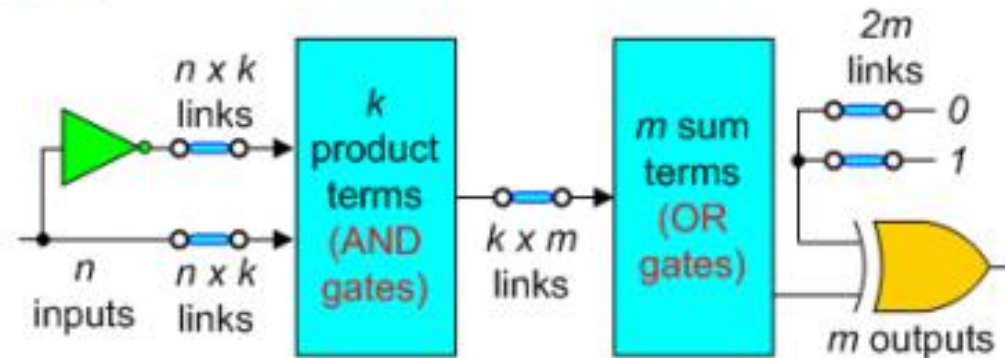(c) Programmable logic array (PLA)

- In PLAs, instead of using a decoder as in PROMs, a number ( $k$ ) of AND gates is used where  $k < 2^n$ , ( $n$  is the number of inputs).

A block diagram of the PLA is shown in the figure. It consists of  $n$  inputs,  $m$  outputs, and  $k$  product terms.



The product terms constitute a group of  $k$  AND gates each of  $2n$  inputs.

Links are inserted between all  $n$  inputs and their complement values to each of the AND gates.

- The output of the OR gate goes to an XOR gate, where the other input can be programmed to receive a signal equal to either logic 1 or logic 0.
- The output is inverted when the XOR input is connected to 1 (since  $x \text{ XOR } 1 = \bar{x}$ ).
- The output does not change when the XOR input is connected to 0 (since  $x \text{ XOR } 0 = x$ ).

# Example 1: Implement the following table using PLA.

A	B	C	F1	f2
0	0	0	1	1
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

Step 1: K-maps for simplification:

BC A		B			
		00	01	11	10
A	0	1	1	0	1
	1	1	0	0	0

$$F_1 = \overline{A}\overline{B} + \overline{A}\overline{C} + \overline{B}\overline{C}$$

$$\overline{F}_1 = AB + AC + BC$$

BC A		B			
		00	01	11	10
A	0	1	0	0	0
	1	0	1	1	1

$$F_2 = AB + AC + \overline{A}\overline{B}\overline{C}$$

$$\overline{F}_2 = \overline{A}\overline{C} + \overline{A}\overline{B} + \overline{A}\overline{B}\overline{C}$$

- Designing using a PLA, a careful investigation must be taken in order to **reduce the distinct product terms**.
- **Both the true and complement forms** of each function should be **simplified** to see which one can be expressed with **fewer product terms** and which one provides **product terms that are common** to other functions.

- K-maps for simplification:

		BC			
		00	01	11	10
A	0	1	1	0	1
	1	1	0	0	0

$$F_1 = \overline{A}\overline{B} + \overline{A}\overline{C} + \overline{B}\overline{C}$$

$$\overline{F}_1 = AB + AC + BC$$

		BC			
		00	01	11	10
A	0	1	0	0	0
	1	0	1	1	1

$$F_2 = AB + AC + \overline{A}\overline{B}\overline{C}$$

$$\overline{F}_2 = \overline{A}C + \overline{A}B + AB\overline{C}$$


The combination that gives a minimum number of product terms is:

$$F_1' = AB + AC + BC \text{ or } F_1 = (AB + AC + BC)'$$

$$F_2 = AB + AC + A'B'C'$$




This gives only 4 distinct product terms:  $AB$ ,  $AC$ ,  $BC$ , and  $A'B'C'$ .

## Step 2: Logic Design

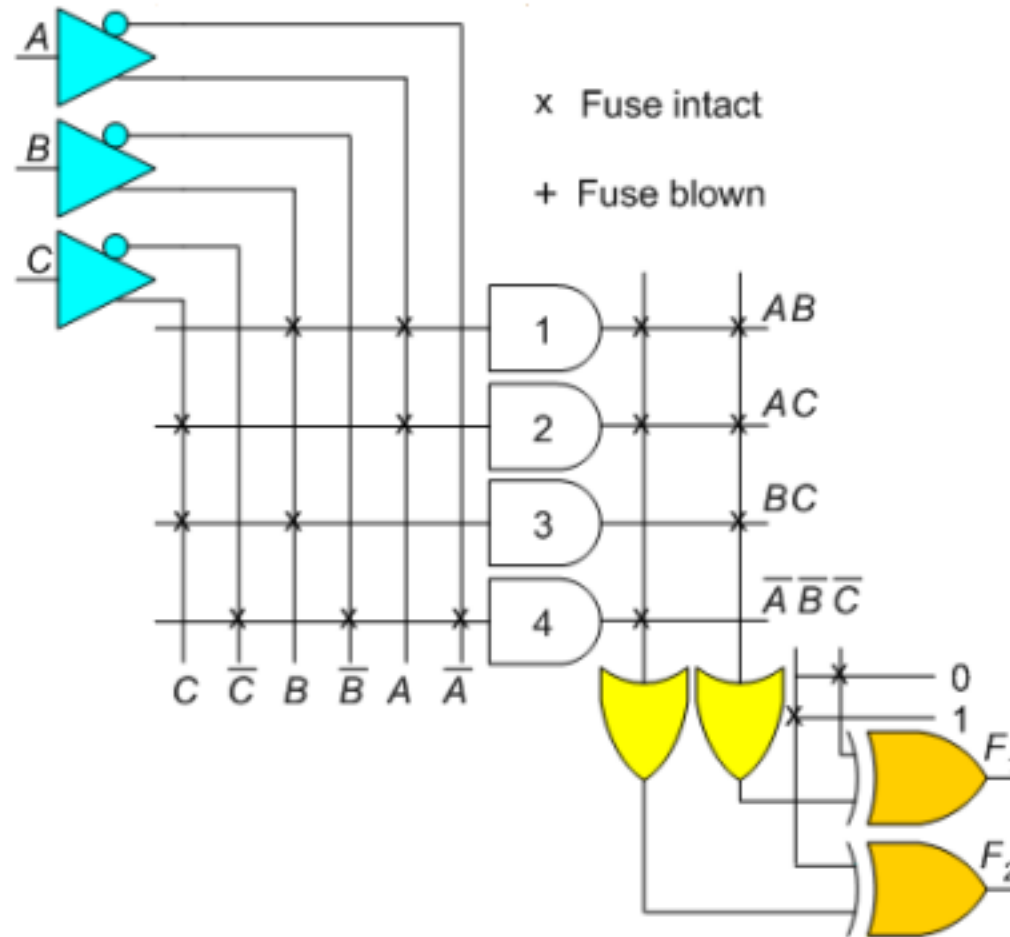

   
# Programmable Array Logic (PAL)


- It has programmable AND array and **fixed OR array**.
- Because **only the AND array is programmable**, it is **easier to use**
- However, it is not flexible as compared to Programmable Logic Array (PLA).




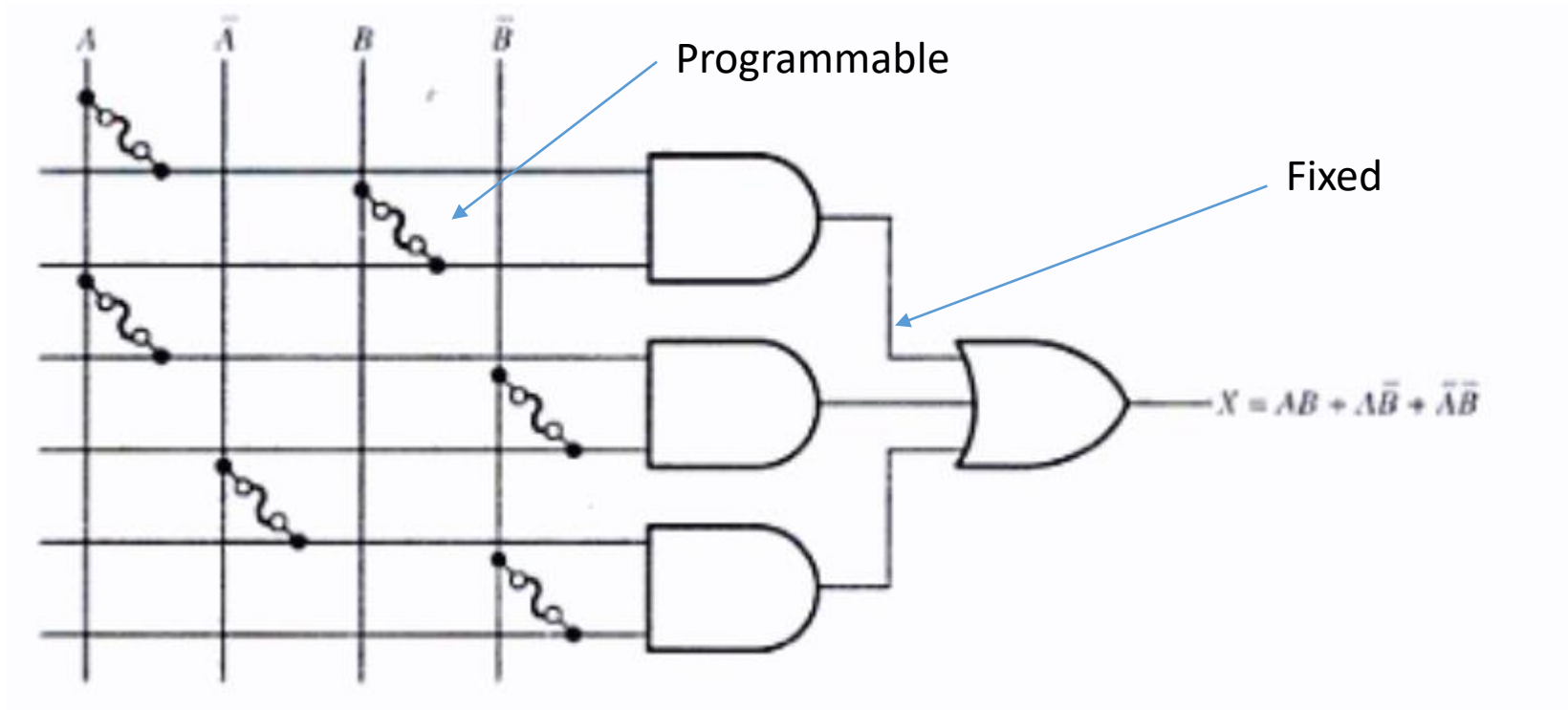
## Example 1: Implement $AB + A\bar{B} + \bar{A}\bar{B}$ using PAL?



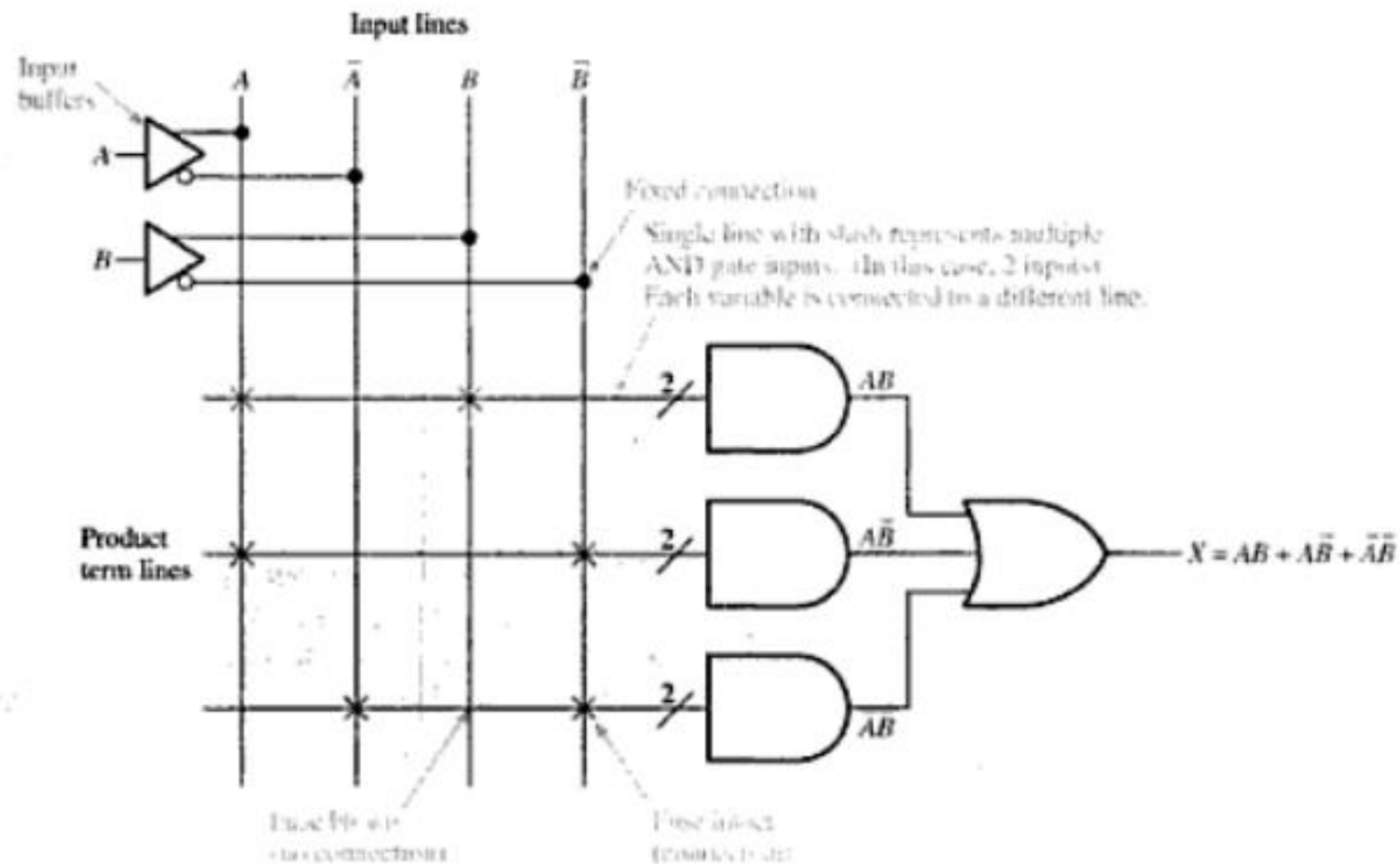

Simplified Diagram

## Example 2:

### Implement following function using PAL?

$$w(A, B, C, D) = \Sigma(2, 12, 13)$$

$$x(A, B, C, D) = \Sigma(7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$y(A, B, C, D) = \Sigma(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$

$$z(A, B, C, D) = \Sigma(1, 2, 8, 12, 13)$$

# Sol:

Use K-map for Simplification

$$w(A, B, C, D) = \sum(2, 12, 13)$$

$$x(A, B, C, D) = \sum(7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$y(A, B, C, D) = \sum(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$

$$z(A, B, C, D) = \sum(1, 2, 8, 12, 13)$$

Simplifying the four functions to a minimum number of terms results in the following Boolean functions:

$$w = ABC' + A'B'CD'$$


$$x = A + BCD$$

$$y = A'B + CD + B'D'$$

$$z = ABC' + A'B'CD' + AC'D' + A'B'C'D$$

$$= w + AC'D' + A'B'C'D$$

## LOGICAL DIAGRAM for PAL:

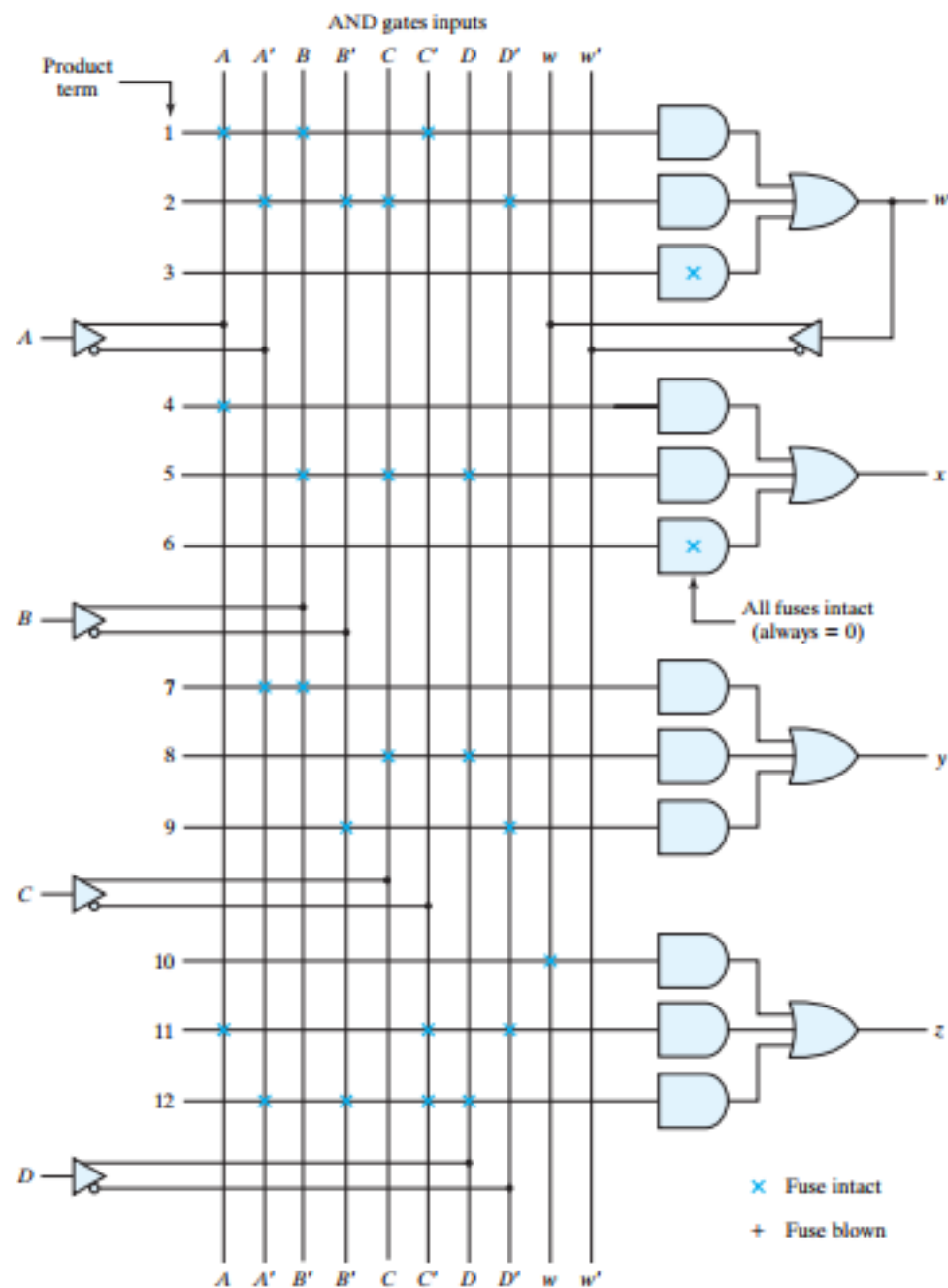

# PALs and PLAs

PLA is the most flexible

- One PLA can implement a huge range of logic functions
- BUT many pins; large package, higher cost

PALs are more restricted / you trade number of OR terms vs number of outputs

- Many device variations needed
- Each device is cheaper than a PLA

# Field Programmable Gate Arrays (FPGAs)

- FPGAs have much more logic than CPLDs
  - 2K to >10M equivalent gates
  - Requires different architecture
  - FPGAs can be RAM-based or Flash-based
    - RAM FPGAs must be programmed at power-on
      - External memory needed for programming data
      - May be dynamically reconfigured
    - Flash FPGAs store program data in non-volatile memory
      - Reprogramming is more difficult
      - Holds configuration when power is off


# FPGA Structure

- Typical organization in 2-D array
  - Configurable logic blocks (CLBs) contain functional logic (could be similar to PAL22V10)
    - Combinational functions plus FFs
    - Complexity varies by device
  - CLB interconnect is either local or long line
    - CLBs have connections to local neighbors
    - Horizontal and vertical channels use for long distance
    - Channel intersections have switch matrix
  - IOBs (I/O logic Blocks) connect to pins
    - Usually have some additional C.L./FF in block


 
# Field-Programmable Gate Arrays structure

- Logic blocks
  - To implement combinational and sequential logic
- Interconnect
  - Wires to connect inputs and outputs to logic blocks
- I/O blocks
  - Special logic blocks at periphery of device for external connections



# Quick Quiz

- The PLD which is more flexible
  - A. PLA
  - B. ROM
  - C. PAL
  - D. Fixed logic

# Quick Quiz

- The size of the PLA is specified by the
  - A. Number of product terms
  - B. Number of inputs
  - C. Number of the outputs
  - D. All of the above

# Quick Quiz

- PAL consists of following matrix
  - A. Fixed AND matrix and a programmable OR matrix
  - B. Programmable AND matrix and a fixed OR matrix
  - C. Both AND and OR matrix are fixed
  - D. Both AND and OR matrix are programmable