
UNIT-II

Combinational Logic System

Lecture 16
Prepared By:
Dr.Krishan Arora
Assistant Professor and Head


 $Z = \sum A, B, C(1,3,6,7)$

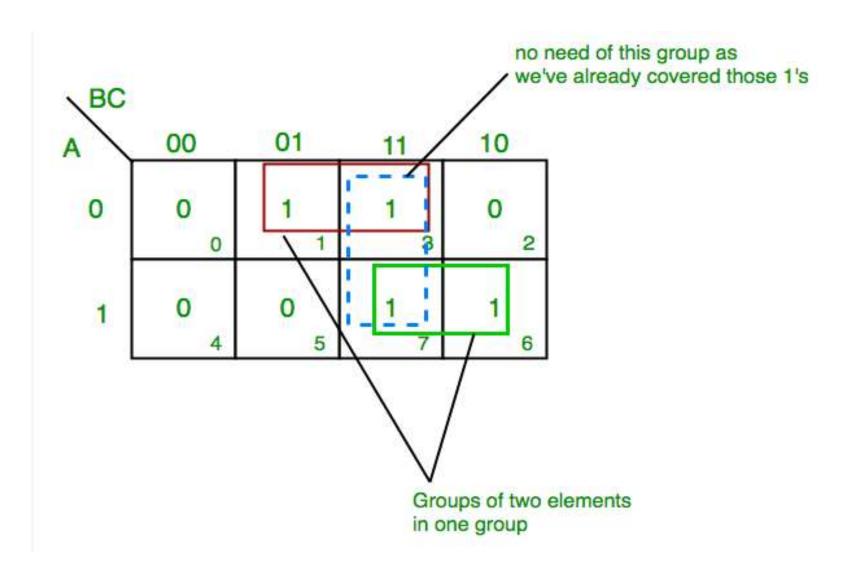

- From red group we get product term—
- A'C
- From green group we get product term—
- AB
- Summing these product terms we get- Final expression

(A'C+AB)


• $F(P,Q,R,S)=\sum(0,2,5,7,8,10,13,15)$

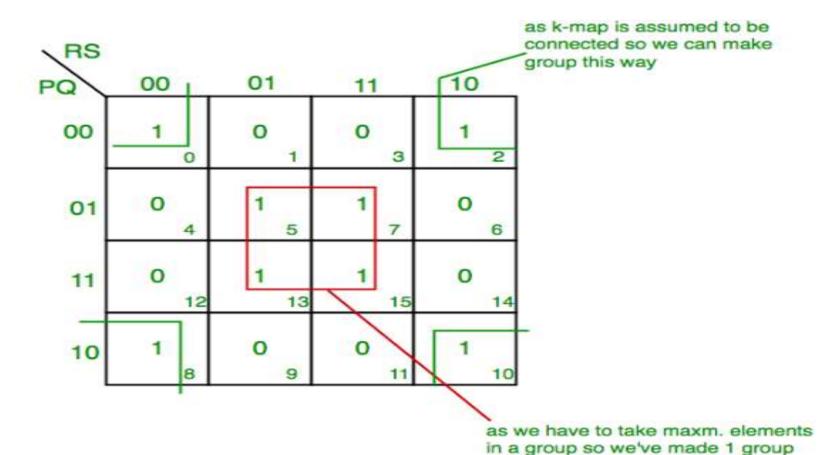

of 4 1's not 2 groups of 2 1's


- From red group we get product term—
- QS
- From green group we get product term—
- Q'S'
- Summing these product terms we get- Final expression (QS+Q'S')

• $F(A,B,C)=\pi(0,3,6,7)$

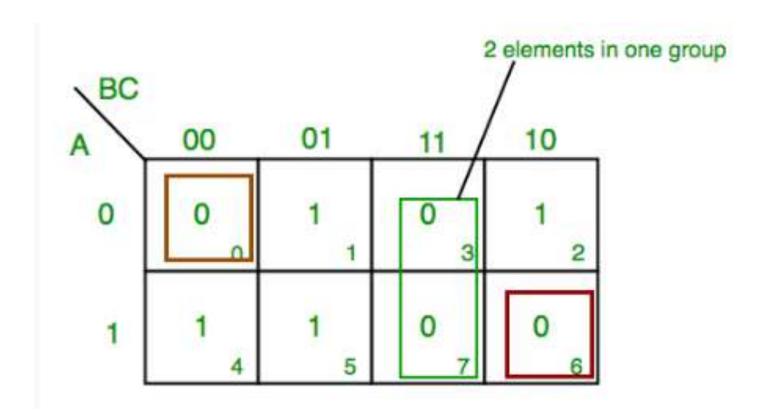

:Final expression (A' + B' + C) (B' + C') (A + B + C)


• $F(A,B,C,D)=\pi(3,5,7,8,10,11,12,13)$

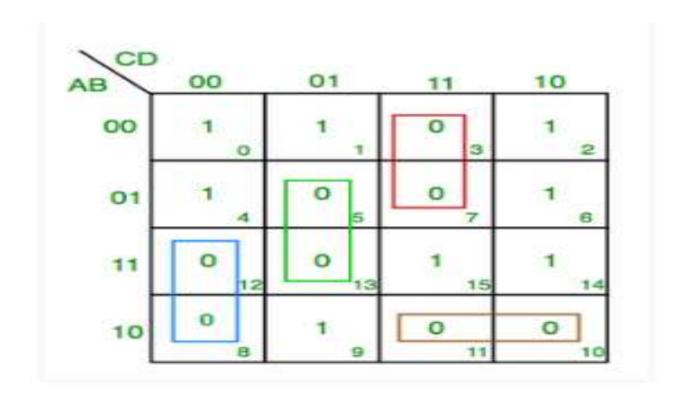

(C+D'+B').(C'+D'+A).(A'+C+D).(A'+B+C')

PoS Optimization from SoP

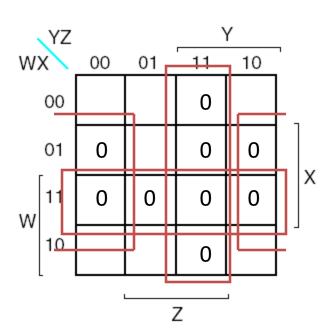 $F(W,X,Y,Z) = \Sigma m(0,1,2,5,8,9,10)$ $= \prod M(3,4,6,7,11,12,13,14,15)$



$$F(W,X,Y,Z) = (W' + X')(Y' + Z')(X' + Z)$$

Or,


$$F(W,X,Y,Z) = X'Y' + X'Z' + W'Y'Z$$

Which one is the minimal one?

SoP Optimization from PoS

 $F(W,X,Y,Z) = \prod M(0,2,3,4,5,6)$


= $\Sigma m(1,7,8,9,10,11,12,13,14,15)$

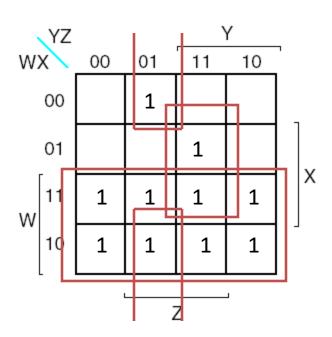

$$F(W,X,Y,Z) = W + XYZ + X'Y'Z$$


Writing the given expression in POS form:

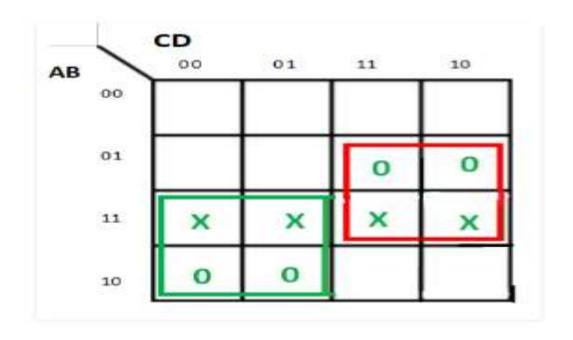• F(A, B, C, D) = M(6, 7, 8, 9) + d(12, 13, 14, 15)



Therefore, POS minimal is, F = (A'+C)(B'+C')

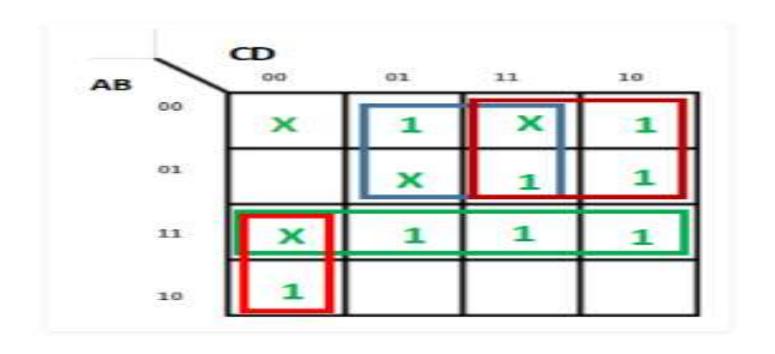Minimise the following function in SOP minimal form using K-Maps:
 F(A, B, C, D) = m(1, 2, 6, 7, 8, 13, 14, 15) + d(0, 3, 5, 12)



$$f = AC'D' + A'D + A'C + AB$$